

520.492: Mixed-Signal VLSI Systems



Homework # 2

Due 2/25/2005

Problem 1 (10 points):

Consider the APS (active pixel sensor) circuit implemented by the silicon structure shown in cross-section in Figure 1, and the corresponding timing diagram of the clock signals controlling the operation.

 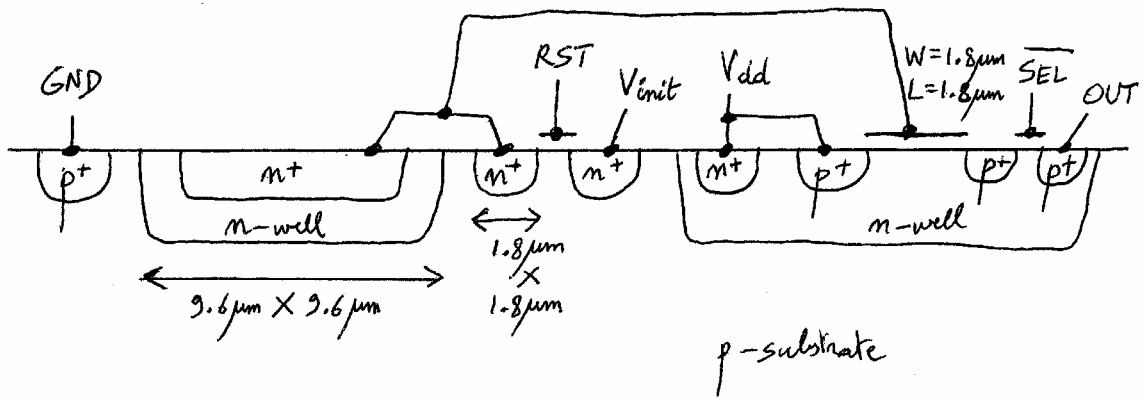- a. Draw the schematic of the implemented circuit. Label the devices and signal nodes consistent with Figure 1.
- b. Estimate the total parasitic capacitance on the APS integrating node. Use the device geometries given in Figure 1, and the MOSIS parametric data at <http://www.mosis.org/cgi-bin/cgiwrap/umosis/swp/params/ami-c5/t48x-params.txt>. Of the tabulated capacitance parameters, consider all area and fringe capacitances that apply except those involving metal lines.
- c. Estimate the photocurrent onto the integrating node, assuming a uniform flux of 1,000 photons per square micron and per second, and perfect quantum efficiency (i.e., each incident photon generates one electron-hole pair). Neglect the contribution from the drain junction at the reset nMOS transistor.
- d. At 30fps (frames per second), estimate the voltage excursion on the integrating node.
- e. The output current on the OUT node is measured just before and after activation of reset (RST). Assume that OUT is held at 100mV below the supply V_{dd} , and the reset voltage V_{init} is lower than a pMOS threshold V_{TP} below V_{dd} . Estimate the change in output current before and after reset. In general, what is this current difference as a function of photocurrent?
- f. *BONUS (for the adventurous)*: How would you implement the circuit at the periphery of the APS array to apply the voltage on the OUT line while registering the difference current? Draw a transistor-level schematic.



V_{init} : constant

Figure 1

Problem 2 (5 points):

Consider the following 4-input logic functions, OUT1 and OUT2:

A	B	C	D	OUT1	OUT2
0	0	0	0	0	1
0	0	0	1	0	1
0	0	1	0	0	1
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	1
0	1	1	0	1	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	1	1
1	0	1	0	1	1
1	0	1	1	1	0
1	1	0	0	1	1
1	1	0	1	1	0
1	1	1	0	1	0
1	1	1	1	1	0

- (a) Implement the functions each using a CMOS complementary logic gate.
- (b) Implement the functions using CMOS transmission gate logic.
- (c) Do you recognize these functions? Implement them as efficiently (least number of transistors) as you can.

No schematic entry, just draw the schematic.

Problem 3 (5 points):

Consider the CMOS inverting amplifier shown in Figure 2. Assume subthreshold operation with identical tail currents I_0 and identical device sizing W/L for nMOS and pMOS transistors.

 


Figure 2

- (a) Find the output voltage V_{out} as a function of input voltage V_{in} .
- (b) Find the output current I_{out} as a function of V_{in} . What does this do?