

## 520.492 Mixed-Signal VLSI Systems

*Week 3*

### **Memory and Arithmetic**

#### **References**

1. Geiger, Allen and Strader: pp. 821-866.
2. Weste and Eshraghian (2<sup>nd</sup> Ed.), Chapter 8.

# MEMORY AND ARITHMETIC

---

ref: Weste & Eshraghian, Chapter 8  
Geiger, Allen & Strader, pp 821-866



## MEMORIES (and the like)

- Registers
  - Shift registers
  - Stack registers
- Random Access Memories (RAM)
  - Static (SRAM)
  - Dynamic (DRAM)
- Read-Only Memories (ROM)
  - Hardwired
  - Programmable / Erasable (EPROM; E<sup>2</sup>PROM)
- Programmable Logical Arrays (PLA)


## ARITHMETIC

- Addition and Subtraction
  - Bit-Parallel Adders (carry look-ahead, Manchester, ...)
  - Bit-Serial Adders
- Multiplication
  - Array Multiplication (Booth recoding, ...)
  - Wallace Tree Multipliers
  - Serial Multipliers

# REGISTERS

 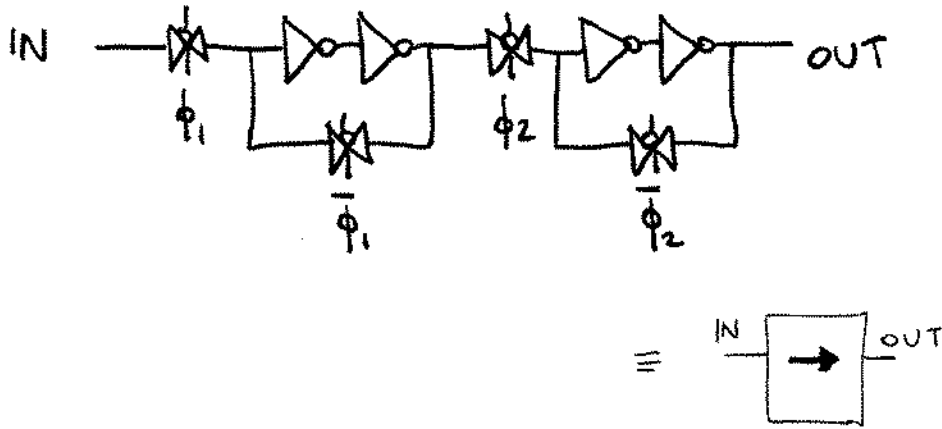


## • Shift Register:

 

- parallel in / serial out  
 - serial in / parallel out

## Bidirectional Shift Register Cell:


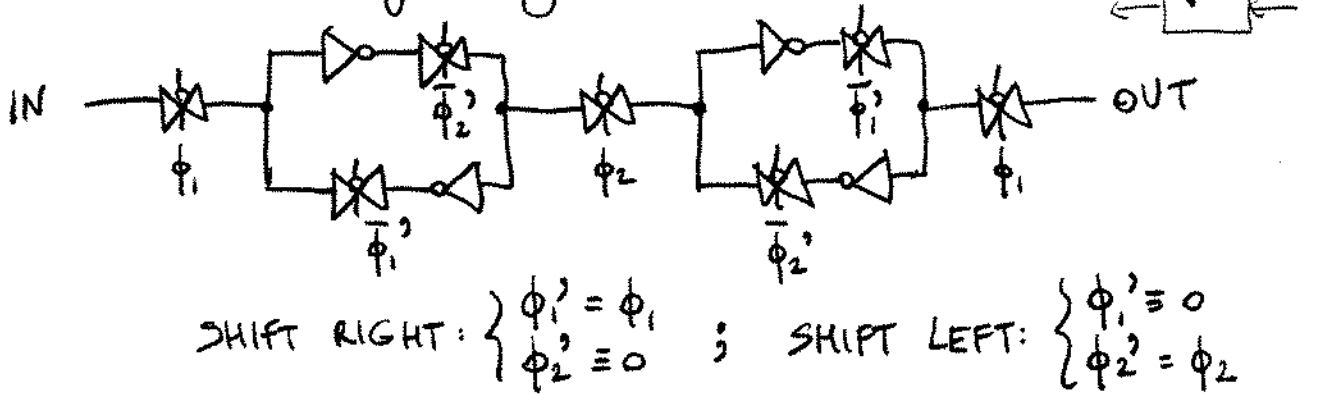


## • Stack Register:



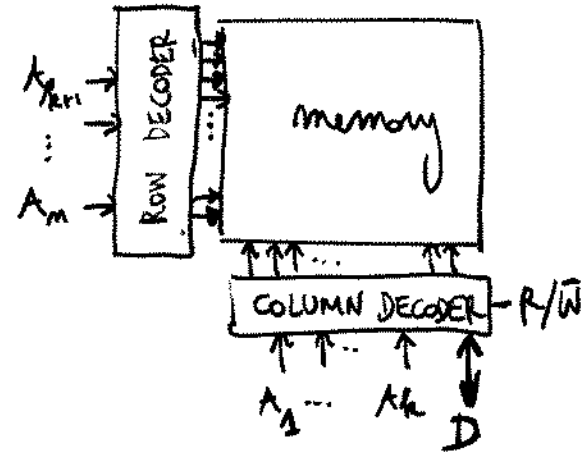 
# ADDRESS-ENCODED MEMORIES


Address  $\{A_j\} \rightarrow$  Data  $D(i)$



• row/column configuration in memory:

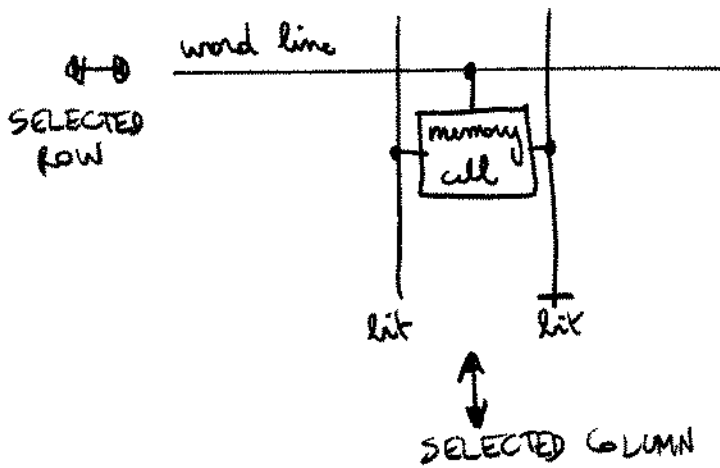


• decoder:

 



# 3T DRAM

 

# PROGRAMMABLE LOGICAL ARRAYS (PLA)

$$Y = f(X)$$

as a sum (canonical sum) of product combinations of  $x_j$  and  $\bar{x}_j$  terms


e.g.:

X		Y	
$x_1$	$x_2$	$y_1$	$y_2$
0	0	1	0
0	1	0	1
1	0	0	1
1	1	1	1

$\Rightarrow$

$$y_1 = \bar{x}_1 \cdot \bar{x}_2 + x_1 \cdot x_2$$
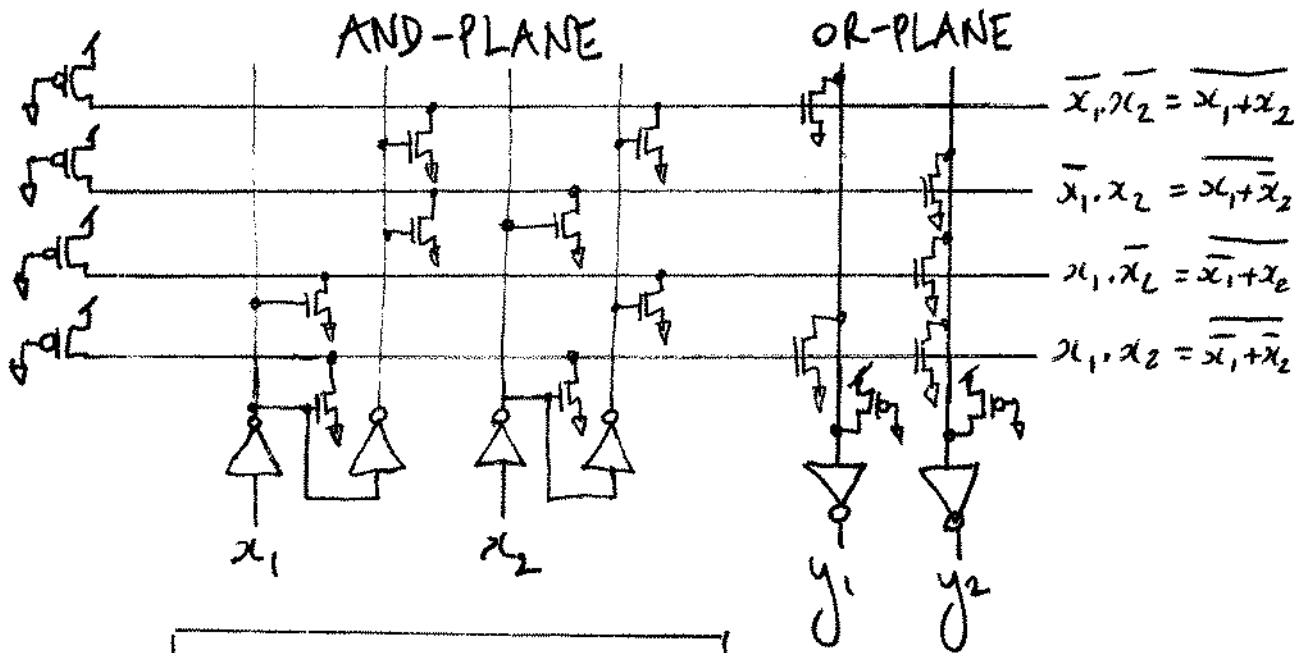
$$y_2 = \bar{x}_1 \cdot x_2 + x_1 \cdot \bar{x}_2 + x_1 \cdot x_2$$



Extensions:

$$Y_i = f(X_i, Y_{i-1})$$

sequential logic  
finite state machines

PROS: structured logic  
scalable, fast turnaround

CONS: efficiency low (size, power, ... vs. minimalist approach)

# ADDITION (unsigned)

$$\left. \begin{aligned} A &= \sum_{i=0}^{n-1} A_i 2^i \\ B &= \sum_{i=0}^{n-1} B_i 2^i \end{aligned} \right\} S = A + B = \sum_{i=0}^{n-1} (A_i + B_i) 2^i \\
 &= \sum_{i=0}^{n-1} S_i 2^i$$

- $S_i \neq A_i + B_i$  : problem  $\begin{cases} A_i = 1 \\ B_i = 1 \end{cases}$
- if bit-sum  $\geq 2 \Rightarrow$  subtract 2 and carry a 1 to the next bit level ( $i+1$ )

$$\begin{cases} S_i = (A_i + B_i + C_i) \bmod 2 \\ C_{i+1} = (A_i + B_i + C_i) \text{ div } 2 \end{cases} \quad (C_0 = 0)$$

(arithmetic)

$A_i$	$B_i$	$C_i$	$(A_i + B_i + C_i)$	$S_i$	$C_{i+1}$
0	0	0	0	0	0
0	0	1	1	1	0
0	1	0	1	1	0
0	1	1	2	0	1
1	0	0	1	1	0
1	0	1	2	0	1
1	1	0	2	0	1
1	1	1	3	1	1


$$S_i = A_i \oplus B_i \oplus C_i$$

$$C_{i+1} = A_i B_i + A_i C_i + B_i C_i$$

(logic)




FULL ADDER :

 


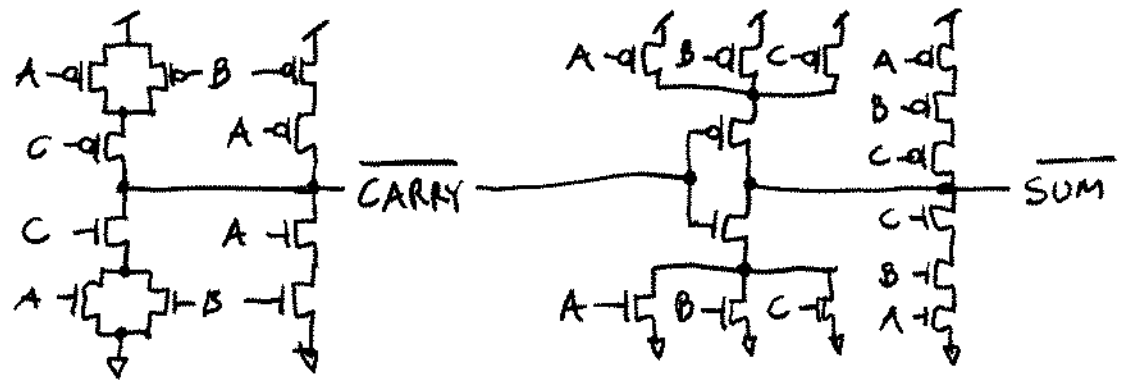(1)  $CARRY = \underbrace{A \cdot B}_{\text{generate (G)}} + C \cdot \underbrace{(A+B)}_{\text{propagate (P)}}$

$SUM = ABC + A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} = A \cdot B \cdot C + (A+B+C) \cdot \overline{CARRY}$



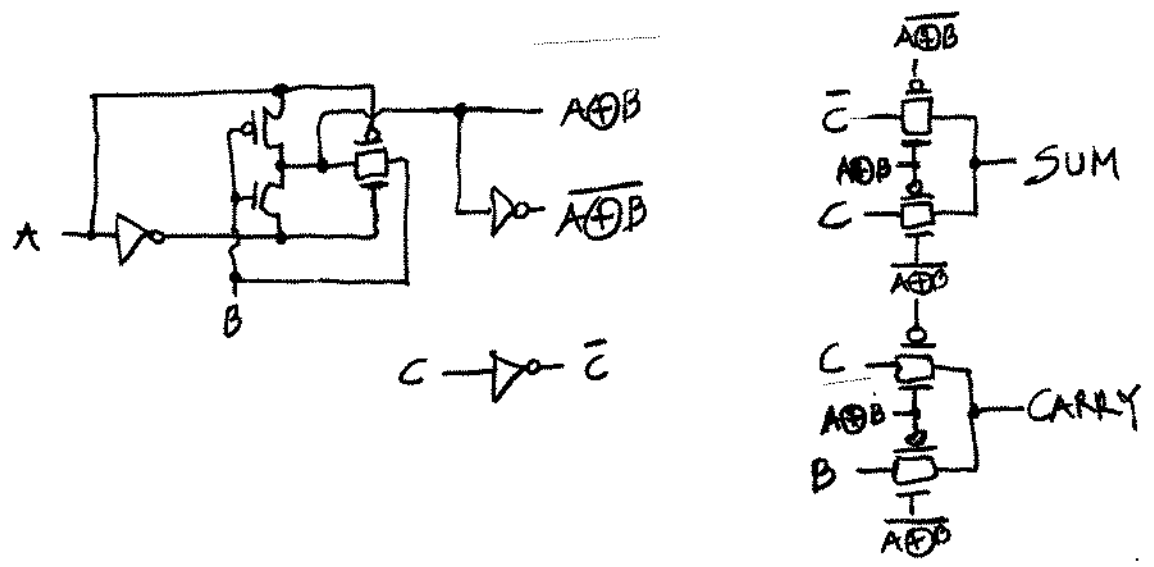
(2)  $CARRY = (A \oplus B) \cdot C + \overline{(A \oplus B)} \cdot B$   
 $SUM = (A \oplus B) \cdot \bar{C} + \overline{(A \oplus B)} \cdot C$   
 where  $A \oplus B \equiv A \cdot \bar{B} + \bar{A} \cdot B$




# CONFIGURATION

## Bit-Parallel:

- Ripple Carry

 


- Pipelined

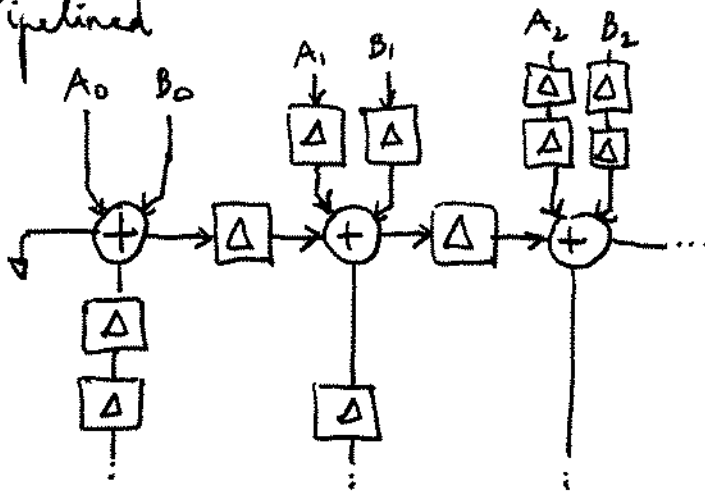

- Carry Look-Ahead (Mandeville); Carry Select; Conditional Sum ...  
→ techniques to reduce critical carry path propagation delay


## Bit-Serial:

 
 
# MULTIPLICATION

$$\begin{aligned}
 X &= \sum_{i=0}^{n-1} X_i 2^i \\
 Y &= \sum_{j=0}^{m-1} Y_j 2^j
 \end{aligned}
 \left. \vphantom{\begin{aligned} X \\ Y \end{aligned}} \right\} P = X \cdot Y = \sum_{i=0}^{n-1} X_i 2^i \cdot \sum_{j=0}^{m-1} Y_j 2^j = \\
 \sum_{i=0}^{n-1} \sum_{j=0}^{m-1} (X_i Y_j) 2^{i+j} = \sum_{k=0}^{n+m-2} P_k 2^k \quad (k=i+j)$$

Again,  $P_k = \sum_{j=0}^{m-1} (X_{k-j} \cdot Y_j)$




- Parallel Summation of  $(X_{k-j} \cdot Y_j)$  contributions:
  - Linear parallel implementation ( $O(n)$  depth)
    - array multiplier
    - Booth recoding multiplier
  - Tree structure implementation ( $O(\log_2 n)$  depth)
    - Wallace tree multiplier
- Serial Summation
  - Serial / Parallel multiplier

Parallel Summation of  $X_{k_j} \cdot Y_j$  product terms:

	$2^2$	$2^1$	$2^0$
...	$X_2 Y_0$	$X_1 Y_0$	$X_0 Y_0$
	$X_1 Y_1$	$X_0 Y_1$	
	$X_0 Y_2$		
...	$P_2$	$P_1$	$P_0$

• array:

 

(see Waker & Estimation, Fig. 8.37)

- Booth reading
- Tree structure (binary,  $\log_2(n)$  latency)


Serial Summation of  $X_{i-j} \cdot Y_j$  product terms:

$$\sum_i P_i 2^i = \sum_i \left( \sum_j X_{i-j} Y_j \right) 2^i$$

$\downarrow$  SHIFT       $\downarrow$  FIXED

	$2^2$	$2^1$	$2^0$	
...	$X_2 Y_0$	$X_1 Y_0$	$X_0 Y_0$	$\rightarrow i=0$
...	$X_1 Y_1$	$X_0 Y_1$		$\rightarrow i=1$
...	$X_0 Y_2$			$\rightarrow i=2$
...	$P_2$	$P_1$	$P_0$	

• Serial/Parallel Multiplier

 

• Serial/Parallel Pipelined Multiplier

