

Lecture 4

Other Sensors and Control Elements

References

Webster, Ch. 2 (Sec. 2.5-2.9).

http://en.wikipedia.org/wiki/Linear_variable_differential_transformer

http://en.wikipedia.org/wiki/Piezoelectric_sensor

<http://en.wikipedia.org/wiki/Switch>


<http://en.wikipedia.org/wiki/Relay>

<http://en.wikipedia.org/wiki/Potentiometer>

- Inductive sensors (displacement)

A bit antiquated, but inductors themselves (in particular mutual inductors) are widely and increasingly used in wireless measurement instrumentation.

- Coil

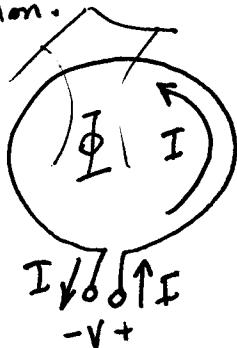


- current I generates magnetic flux Φ :

$$\Phi = L \cdot I$$

- derivative flux $\frac{d\Phi}{dt}$ induces voltage V

$$V = \frac{d\Phi}{dt} = L \cdot \frac{dI}{dt}$$

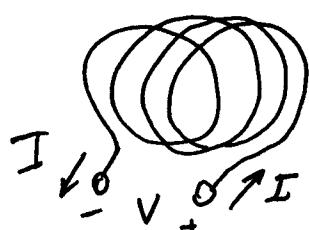
- Multiturn coil : n turns (windings) \Rightarrow



- n times larger flux for same current

- n times larger voltage for same derivative flux
 $\Rightarrow \times n^2$

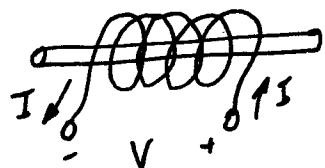- Coil with ferromagnetic core : permeability $\mu = \mu_0 \cdot \mu_r \Rightarrow$



- μ_r times larger flux for same current

- no change in voltage for given derivative flux
 $\Rightarrow \times \mu$

$$\Rightarrow V = L \frac{dI}{dt} \quad \text{with } L = n^2 \cdot G \cdot \mu$$


INDUCTANCE

\downarrow
NUMBER OF WINDINGS (TURNS)

\downarrow
GEOMETRY FACTOR

\downarrow
EFFECTIVE PERMEABILITY

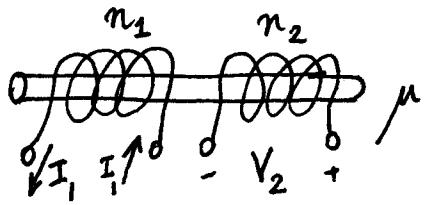- Mutual inductance between magnetically coupled coils:



- current I_1 generates magnetic flux ($\propto \mu n_1$)
- derivative flux induces voltage V_2 in second coil ($\propto n_2$)

$$\Rightarrow V_2 = M_{12} \cdot \frac{dI_1}{dt} \quad \text{with} \quad M_{12} = n_1 n_2 \cdot G \cdot \mu$$


MUTUAL
INDUCTANCE

This is the basis of a TRANSFORMER, and WIRELESS TELEMETRY

- Coil(s) with displaceable ferromagnetic core \Rightarrow INDUCTIVE SENSOR


Effective permeability μ changes with displacement of the core x .

- Self-inductance:

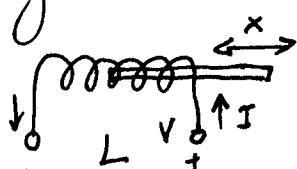


$$\Delta L \propto \Delta x \quad \text{for small } \Delta x$$

- Mutual inductance (transformer):

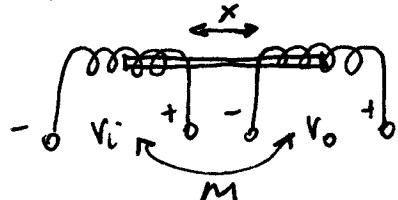

$$\Delta M \propto \Delta x \quad \text{for small } \Delta x$$

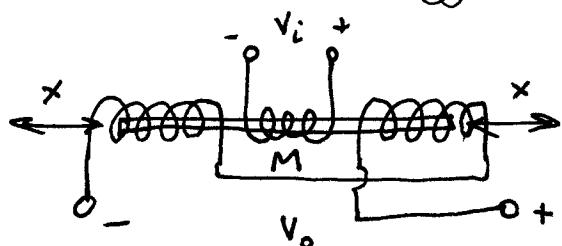
- Linear variable differential transformer (LVDT):



$$M \propto x \quad \text{for larger } x$$

- more linear, zero offset
- requires a diode-resistor bridge for decoding of phase

- Capacitive sensors (displacement) :

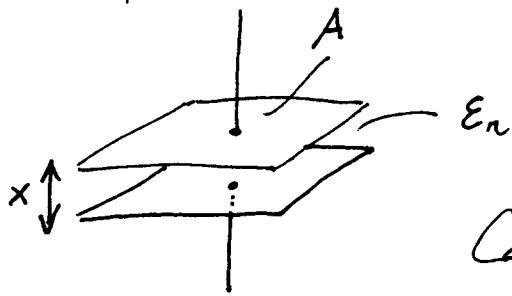


dielectric constant : $\epsilon = \epsilon_0 \cdot \epsilon_r$
(permittivity)

VACUUM RELATIVE
PERMITTIVITY

Capacitance between plates:

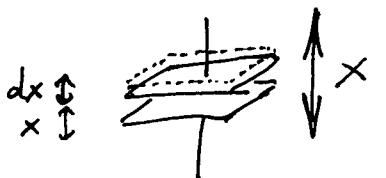
$$C = \epsilon \cdot \frac{A}{x} = \epsilon_0 \cdot \epsilon_r \cdot \frac{A}{x}$$



$$\Rightarrow \text{SENSITIVITY} : \frac{dC}{C} = -\frac{dx}{x}$$

Transversal
displacement
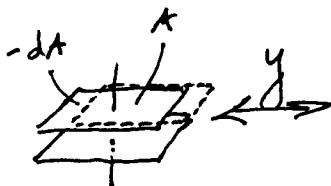
$$\text{or } \frac{dC}{dx} = -\frac{C}{x} = -\epsilon \frac{A}{x^2}$$




$$\Rightarrow \text{SENSITIVITY} : \frac{dC}{C} = +\frac{dA}{A} = -\frac{dy}{y}$$

Lateral
displacement

$$\text{or } \frac{dC}{dy} = -\frac{C}{y} = -\epsilon \frac{A}{xy}$$

Measurement of $\frac{dC}{C}$: e.g. (as in condenser microphone):
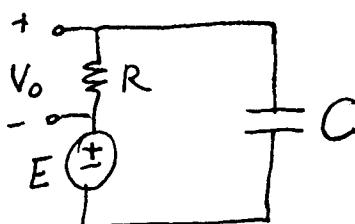
$$x \approx x_0 + \delta x(j\omega) \quad (\delta x \ll x_0)$$



$$\Rightarrow \frac{V_0(j\omega)}{\delta x(j\omega)} = \frac{E}{x_0} \cdot \frac{j\omega z}{1+j\omega z} ; \quad z = R C_0$$


constant ≈ 1 for $\omega > \frac{1}{z}$

$$\Rightarrow \delta x \approx \frac{x_0}{E} \cdot V_0 \quad \text{for } \omega > \frac{1}{z} \quad (\text{HIGHPASS})$$

Microphonics in Capacitive sensing:

- DC (static) charge on a capacitor:

$$Q = C \cdot V$$

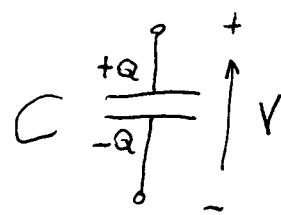


- AC charge flow (current) through the capacitor:

$$\begin{aligned} I &= \frac{dQ}{dt} = C \cdot \frac{dV}{dt} + \frac{dC}{dx} \cdot V \\ &= C \cdot \frac{dV}{dt} - C \frac{V}{x} \cdot \frac{dx}{dt} \end{aligned} \quad \rightarrow \quad \frac{dC}{dx} = -\frac{dx}{x}$$


↓ ↓
electronics microphonics

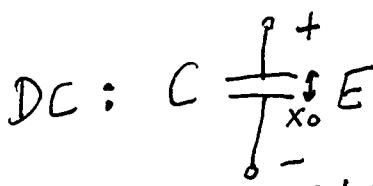\Rightarrow For small AC signals and large DC bias: $\left\{ \begin{array}{l} x = x_0 + \delta x, \delta x \ll x_0 \\ V = E + \delta V, \delta V \ll E \end{array} \right.$



DC: \downarrow
 δC

AC: \downarrow
 δV

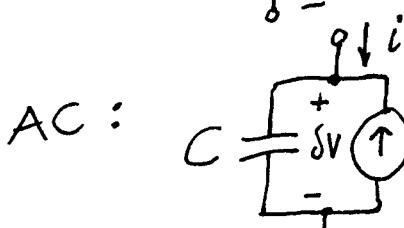

Norton equivalent:

$$i(j\omega) = j\omega C \delta V - C \frac{E}{x_0} j\omega \delta x$$


↓ ↓
electronics microphonics

admittance


Source

Example: condensor/electret microphone:

high input impedance
amplifier

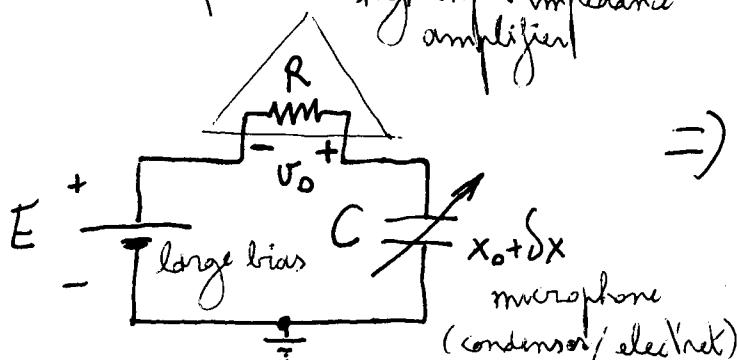
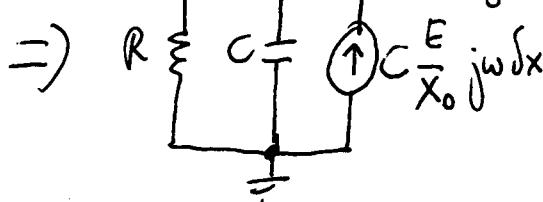
$$V_o = \frac{R \cdot \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} \cdot C \frac{E}{x_0} j\omega \delta x$$



- Piezoelectric sensors (displacement, and force) :

PIEZOELECTRIC CRYSTALS are electromechanical SENSORS and ACTUATORS:

- applied force (displacement) induces charge (voltage);
- applied voltage (charge) induces displacement (force).

$$\text{DISPLACEMENT} \longleftrightarrow \text{FORCE} \longleftrightarrow \text{CHARGE} \longleftrightarrow \text{VOLTAGE}$$


$$x \qquad E \qquad f \qquad k \qquad q \qquad C \qquad V$$

YOUNG'S MODULUS PIEZOELECTRIC CONSTANT CAPACITANCE

$$E = \frac{\sigma}{\epsilon} = \frac{f/A}{x/L} \qquad q = k \cdot f \qquad q = C \cdot V$$

Typical use :

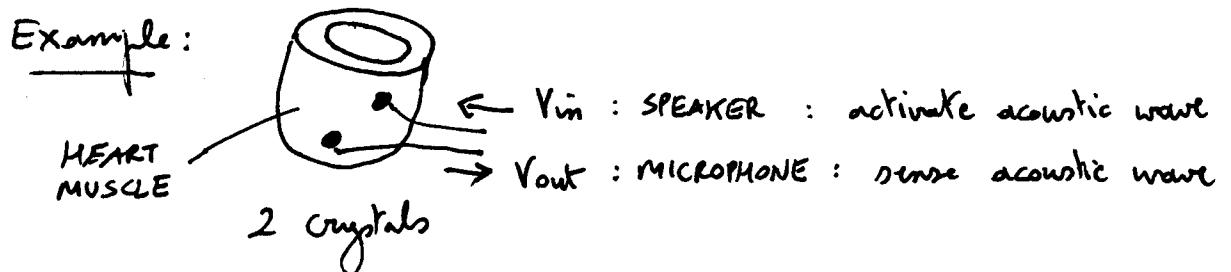- Micro-balance : sensitive, compact weight measurement
- Audio / ultrasonic : microphone AND speaker for active acoustics




Speaker-microphone pair allows to measure TRANSIT TIME which gives an indirect, sensitive measure of DISTANCE between two points on the cardiac muscle surface (assuming speed of sound does not change with muscle contraction.)

- Other sensors, e.g. TEMPERATURE : same principle
 - Thermocouple : junction of 2 different metals creates a voltage dependent on temperature
 - Common (K-type) : sensitivity $\approx 40 \mu\text{V}/^\circ\text{C}$
 - Need a temperature reference and a second, matched thermocouple to measure absolute rather than change in temperature.
 - Thermistor : ceramic material with resistance dependent on temperature
 - $\frac{\Delta R}{R} = \alpha \cdot \Delta T$ or $R = R_0(1 + \alpha \Delta T)$
where temperature coefficient α depends on the material ($\alpha > 0$, or $\alpha < 0$), and on temperature (nonlinear!).
 - Can be differentially embedded in a Wheatstone bridge for accurate T measurement.


BASIC CONTROL ELEMENTS

: switches, relays, turnpots

- Switches:

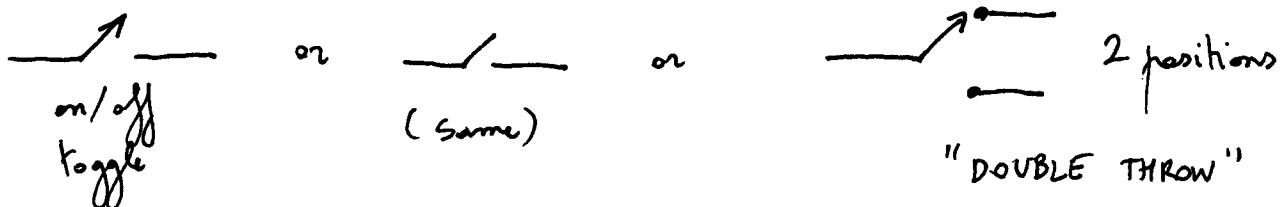


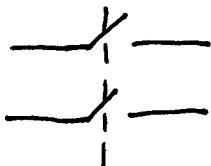Can join two switches with single control (both move together):




"DOUBLE POLE"

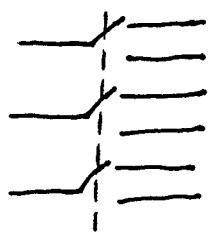Multi-throw, multi-throw combinations, e.g.:



"3P2T"

3 pole, 2 throw

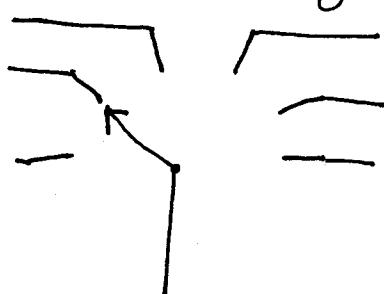

"1P6T"

1 pole, 6 throw

e.g.: 6 lead ECG
measurements,
selected by switch

Push buttons:



N.O.

"normally open"




N.C.

"normally closed"

(NOTE: "closed" means
conducting
connected;
"open" means
non-conducting,
disconnected)

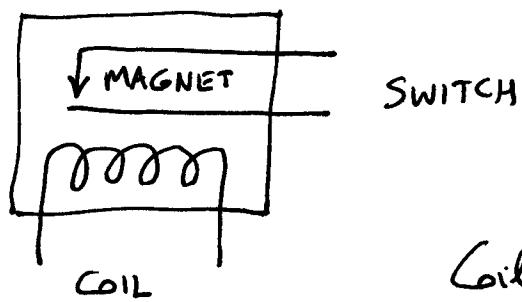- Relays : electrically (magnetically) activated switches




Coil closes (or opens) switch when a voltage is applied

Voltage \rightarrow current in coil \rightarrow magnetic field \rightarrow magnet pulling action \rightarrow switch closes or opens

Why needed ?

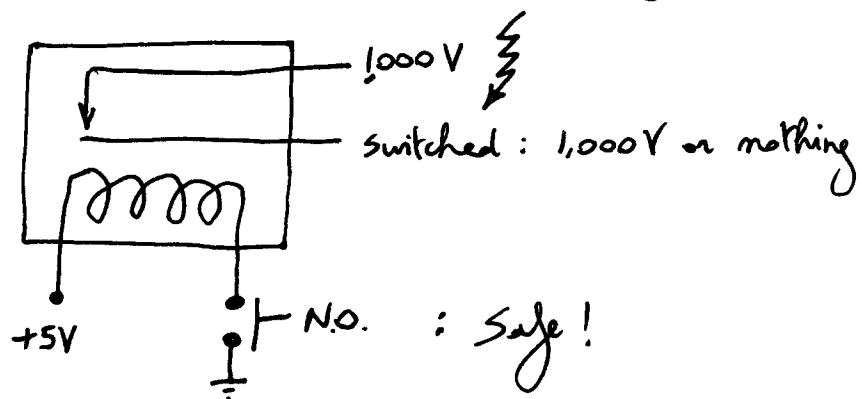
- \rightarrow electronic and software control of a switch , rather than mechanical (manual) input
- \rightarrow safety with high voltages , e.g. :




- Turn potentiometers (or TURNPOTS) :

analog control of circuit parameters with the turn of a knob.

- Threshold, offset, bias control:

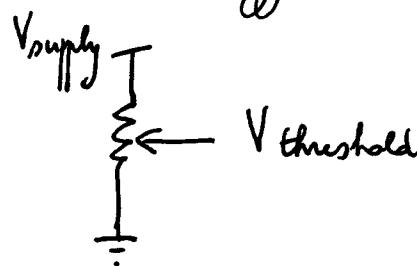


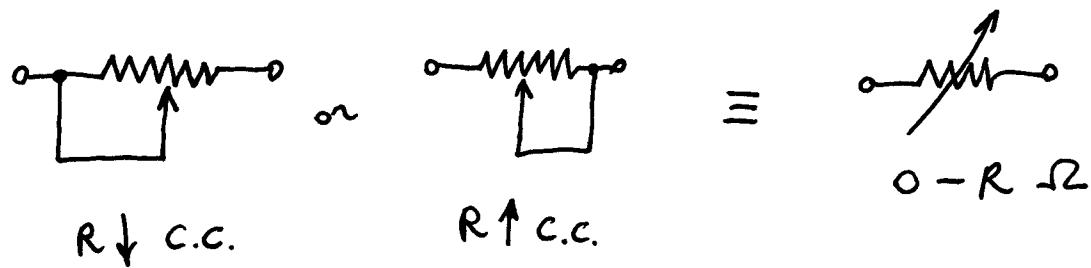- Variable resistor: trimpot with two terminals:




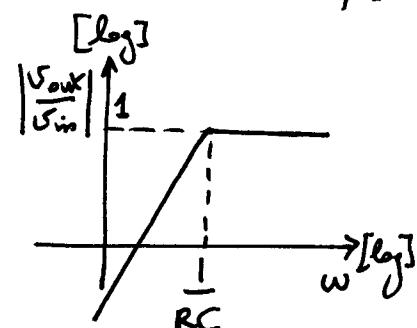Example: HIGHPASS FILTER with VARIABLE CUTOFF FREQUENCY:

$$\frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{R}{\frac{1}{j\omega C} + R} = \frac{j\omega RC}{1 + j\omega RC}$$



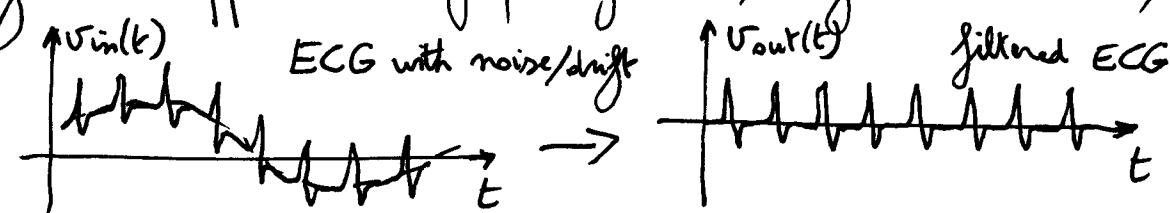Useful to suppress low-frequency noise/drift in the sensor/signal:



Turning the $R \nparallel$ knob trades noise/drift rejection vs. signal fidelity.