

Name: _____


BENG 186B Winter 2011

Final


- This exam is closed book, closed note, calculators are OK.
- Circle and put your final answers in the space provided; show your work only on the pages provided. Include units.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- Points for each problem are given in [brackets], 100 points total.

1	/10
2	/16
3	/8
4	/8
5	/8
6	/10
7	/10
8	/8
9	/10
10	/8
11	/4
Total	/100

Useful schematics and equations

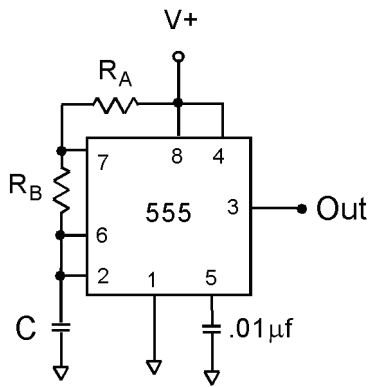

Oscillator

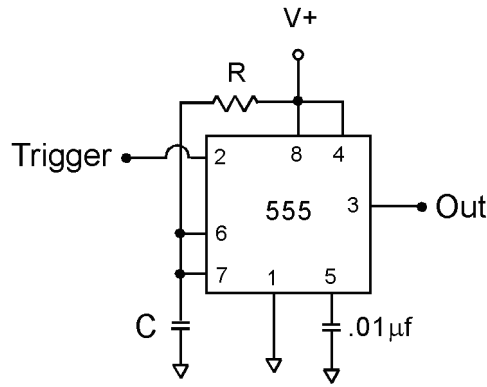

One-shot

Nernst Equation:

$$E = \frac{RT}{zF} \ln \frac{C_1}{C_2}$$

$R = 8.3 \text{ J}/(^{\circ}\text{K} \cdot \text{mol})$
 $T = \text{temperature } (^{\circ}\text{K})$
 $F = 96,500 \text{ C/mol}$
 $z = \text{valence (unitless)}$

Common mode gain and differential gain:

$$v_o = A_d v_d + A_c v_{cm}$$

$$v_d = v_a - v_b$$

$$v_{cm} = (v_a + v_b) / 2$$

1. Circle the letter of the best (one and only one) answer for each. [10 pts; 1 pt each]

A) Resolution of an instrument is:

- a) the difference between its true output and its measured value
- b) the standard deviation of its measured output
- c) the largest signal that it can measure without distortion
- d) the measure it takes in calibrating itself
- e) the smallest measurable increment in its output

B) The damping ratio of a second-order system should be:

- a) as small as possible to avoid an oscillatory system response
- b) as large as possible to produce a fast system response
- c) zero for a critically damped response
- d) one for a critically damped response
- e) negative for an overdamped response

C) Poisson's ratio for a strain gauge relates:

- a) change in resistance to change in diameter
- b) change in resistance to change in length
- c) change in diameter to change in length
- d) strain to change in length
- e) strain to resistance

D) A 2P3T (two-pole, three-throw) switch allows to connect: *(Hint: it helps to draw the switch)*

- a) three inputs to any of six outputs
- b) two inputs to any of six outputs
- c) three inputs to either of two sets of three outputs
- d) two inputs to either of three sets of two outputs
- e) neither of the above

E) At high frequencies the gain of an opamp is

- a) zero
- b) equal to the gain-bandwidth product
- c) the gain-bandwidth product divided by frequency
- d) increasing with frequency
- e) independent of frequency


F) A hysteretic comparator uses

- a) capacitive feedback
- b) negative feedback
- c) positive feedback
- d) unity-gain feedback
- e) neither of the above

- G) The concentration overpotential of an electrode depends on:
- a) temperature
 - b) valence of the cation
 - c) activity of the cation
 - d) all of the above
 - e) none of the above
- H) Compliance of the diaphragm and air bubbles in a catheter tube can be modeled electrically as:
- a) capacitance
 - b) inductance
 - c) inertance
 - d) resistance
 - e) constant current
- I) Pulse oxymetry directly measures:
- a) PO₂ with an electrochemical sensor
 - b) SO₂ with an electrochemical sensor
 - c) SO₂ with an optical sensor
 - d) PO₂ with an optical sensor
 - e) Neither of the above
- J) Macroshock is:
- a) A massive electrical shock with severe damage or fatality
 - b) An electrical shock where all current passes through the heart
 - c) An electrical shock caused by currents through a catheter
 - d) An electrical shock where part of the current passes through the heart
 - e) A massive disruption of electrical activity in the brain

2) Short answer, write your answer only in the space provided. [16 pts; 2 pts each]

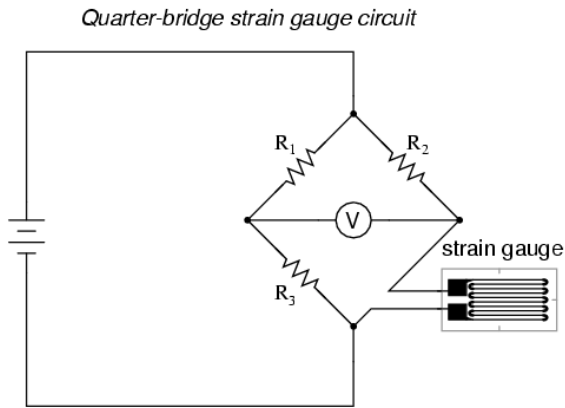(a) Find the precision of the voltage output in the following strain gauge circuit. All resistances are nominally $100\text{ k}\Omega$, but the strain gauge resistance is found to be $96\text{ k}\Omega$ at zero strain. The supply voltage is 5 V . [2 pts]



(b) List the parameters that describe non-ideal opamp characteristics. [2 pts]

(c) What is the difference between EEG and ECoG? [2 pts]

(d) What determines the voltage measured between two electrodes immersed in a uniform ionic solution? [2 pts]


(e) Sketch the Einthoven triangle with 6 ECG lead vectors in the frontal plane. [2 pts]

(f) What is the Doppler frequency shift for blood moving with velocity v towards the instrument containing both ultrasonic transmitter and receiver, with ultrasonic waves of frequency f and speed c ? [2 pts]


(g) What is SO_2 ? [2 pts]

(h) Why is it safer to operate an instrument with a grounded rather than an ungrounded plug? [2 pts]

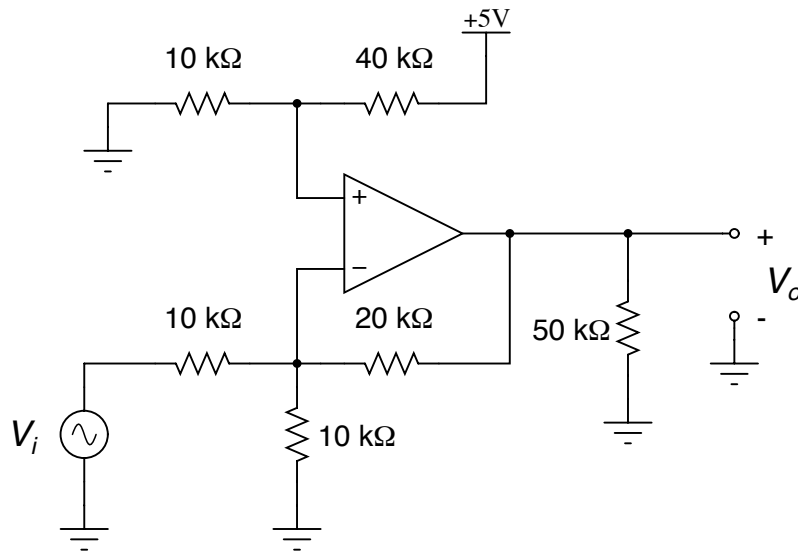3) Find the Thevenin equivalent at the V_o terminals in terms of the input voltage signal V_i [8 pts].



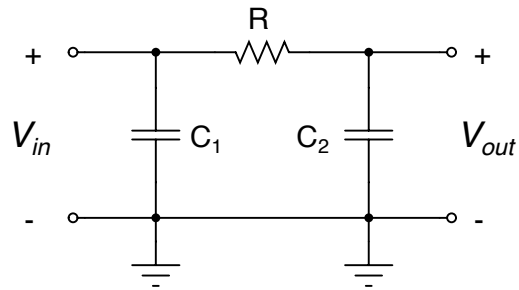
4a) Find the input impedance $Z_{in}(j\omega)$ as seen at the V_{in} terminal for the following filter circuit. [2 pts]



b) Find the output impedance $Z_{out}(j\omega)$ as seen at the V_{out} terminal. [2 pts]

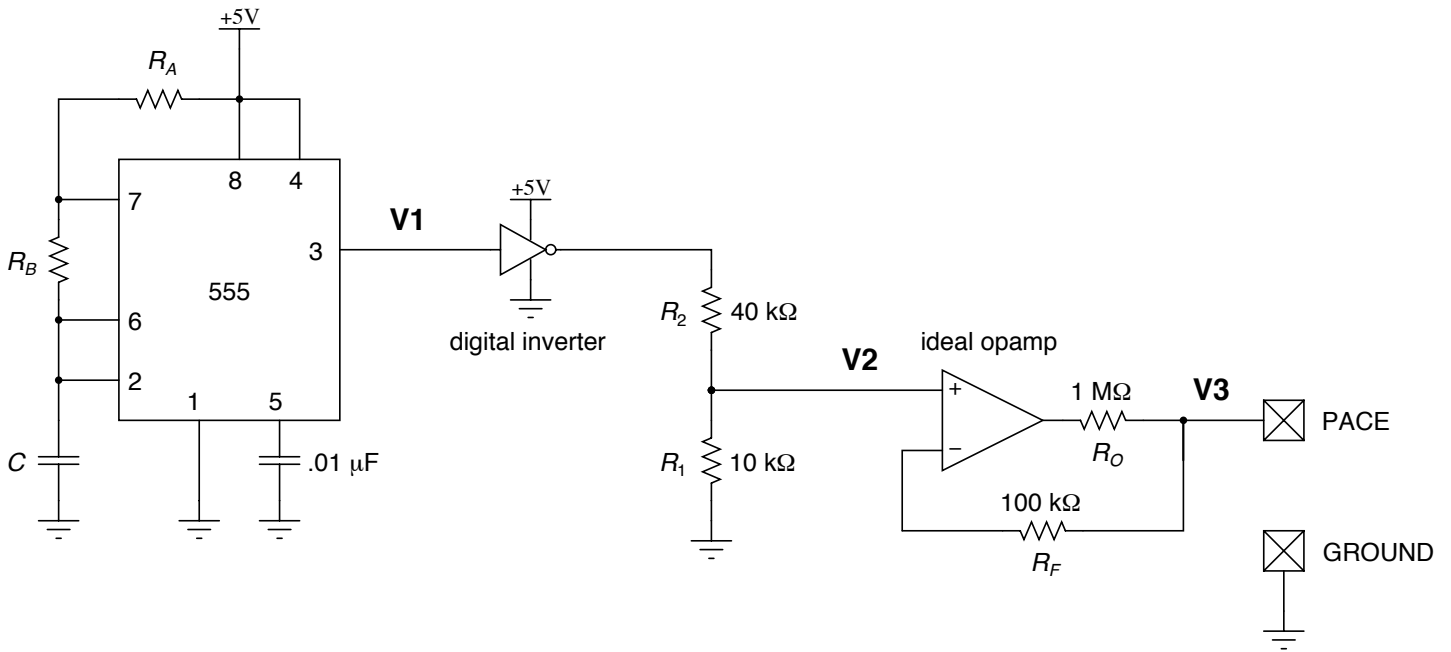c) Find the transfer function $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$. What type of filter is it? Sketch the magnitude of the transfer function, as function of frequency f , for $R = 100 \text{ k}\Omega$, $C_1 = 1.6 \text{ nF}$, and $C_2 = 16 \text{ nF}$. Indicate numerical values of the filter parameters. [4 pts]

5a) Sketch the voltage waveforms **V1**, **V2**, and **V3** over time for the pacemaker circuit shown below. Indicate the time and voltage scale on the waveforms. The equations for the 555 timer circuit are $T_{\text{low}} = 0.7 R_b C$, and $T_{\text{high}} = 0.7 (R_a + R_b) C$, where $R_a = 1.3 \text{ M}\Omega$, $R_b = 1.3 \text{ k}\Omega$, and $C = 1 \text{ }\mu\text{F}$. [6 pts]



V1

V2


V3

b) Explain the function of the R_O and R_F resistors in protecting the patient, and in protecting the circuit. [2 pts]

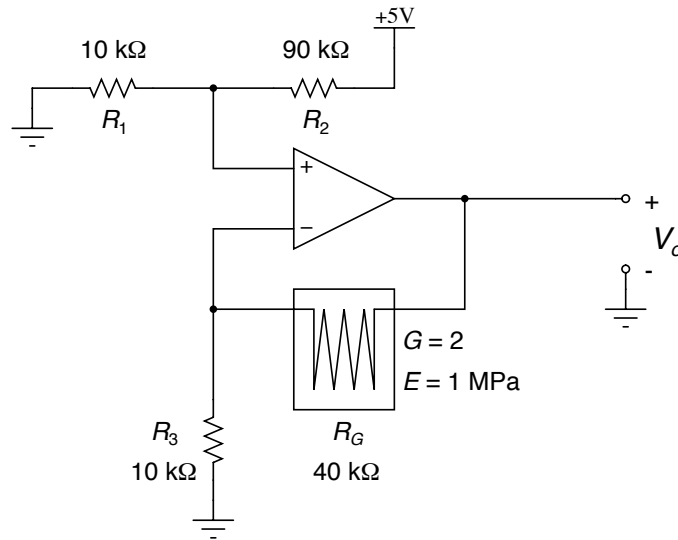c) *BONUS* (only do this after you have completed everything else):


Extend the pacemaker circuit so that the “PACE” output is only driven when no heartbeat is detected for at least five seconds. For this a third electrode “ECG” is connected to the heart and produces a voltage that is greater than 50mV during the QRS complex. Note: once your circuit starts pacing, it should not stop until a heartbeat is detected *outside* of the pace pulse. [extra 6 points, no partial credit!]

6a) Find the voltage V_o as a function of tensile stress σ for the following stress transducer circuit. R_G is the resistance of the strain gauge at zero strain, G is the gauge factor, and E is the Young's modulus of the strain gauge under tensile stress, as given below. [8 pts]




b) Find the sensitivity of the stress transducer, and indicate the units. [2 pts]

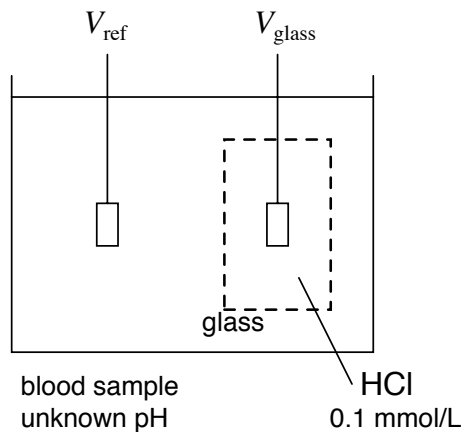7) A blood pH reader is shown below, with one Ag/AgCl electrode immersed in the blood sample at room temperature, and a second Ag/AgCl electrode inside a glass bulb containing a solution of 0.1 mmol/L HCl in water. The glass membrane is permeable to H^+ only. For each Ag/AgCl electrode, the half cell potential is $E_{hc} = 0.223$ V, and the impedance parameters are $R_d = 320$ k Ω , $C_d = 1$ pF, and $R_s = 1$ k Ω .



Each Ag/AgCl electrode:

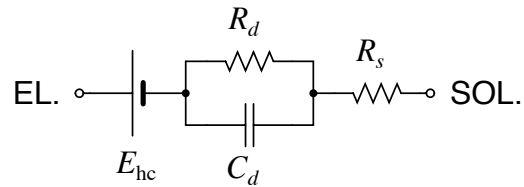

a) Find the pH of the HCl solution inside the glass bulb. [2 pts]


b) The voltage on the glass electrode relative to the reference electrode measures -186 mV. Find the pH of the blood sample. [4 pts]

c) Assuming that the electrical resistance between the solutions for transport of hydrogen through the thin glass membrane is $R_{mem} = 260$ k Ω , find the equivalent impedance between the two electrodes. Sketch the magnitude of the impedance as a function of frequency. On your graph denote and quantify the corner frequency f_c , and the value of effective resistance at zero and infinite frequencies. [4 pts]

8a) Sketch the time waveform of a typical ECG voltage signal measured across lead II in the frontal plane. Indicate P, Q, R, S, and T on the waveform, and indicate the time and voltage scales on the axes. [4 pts]

b) It is generally observed that the T wave is zero for the aVL lead, and is maximally positive for the II lead. Based on this, sketch a typical direction of the cardiac vector for the T wave in the frontal plane, in relation to the 6 lead vectors. *Hint:* You may assume that for each of the leads the corresponding ECG signal is $V_{\mathbf{a}} = \mathbf{M} \cdot \mathbf{a}$, where \mathbf{M} is the cardiac vector, and \mathbf{a} is the lead vector. [4 pts]

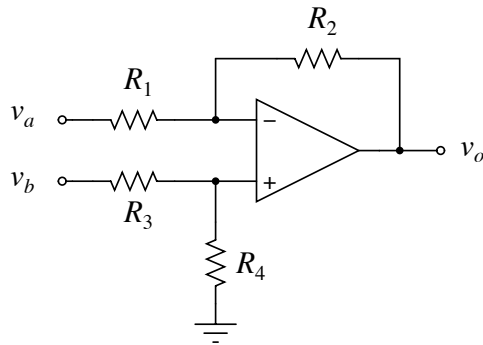9) Consider the differential biopotential amplifier below, with resistance values $R_1 = R_3 = 100 \text{ k}\Omega$, and $R_2 = R_4 = 10 \text{ M}\Omega$.




a) Find the input impedance on the v_a node to ground, the input impedance on the v_b node to ground, and the output impedance on the v_o node to ground. [3 pts]

b) Find the differential gain A_d , common gain A_c , and common mode rejection ratio CMRR of the bioamplifier. [3 pts]

c) The bioamplifier is now connected to the body through electrodes with impedance $R_a = 110 \text{ k}\Omega$ on the v_a terminal, and $R_b = 90 \text{ k}\Omega$ on the v_b terminal. Find the resulting changes in differential gain A_d , common gain A_c , and common mode rejection ratio CMRR. Explain what happened. [4 pts]

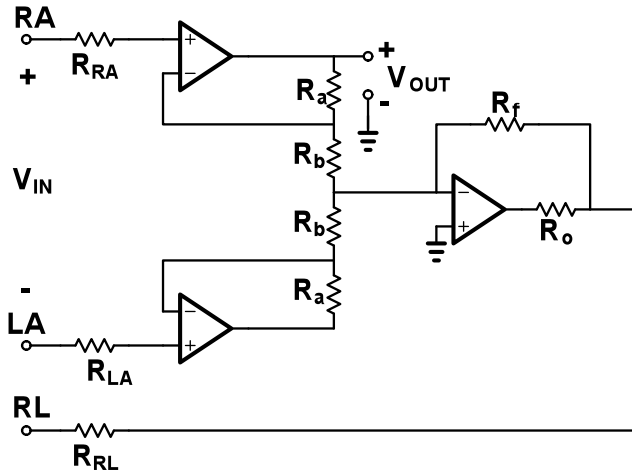10) Consider the DRL system below, with electrode resistances $R_{RA} = R_{LA} = R_{RL} = 130 \text{ k}\Omega$, and with circuit resistances $R_a = 1 \text{ M}\Omega$, $R_b = 1 \text{ k}\Omega$, and $R_f = 1 \text{ M}\Omega$.



a) Find the effective resistance between the RL terminal and ground. Assume the entire body is at common mode potential v_{cm} , and an external displacement current i_d enters the body. [5 pts]

b) Find the value of the resistance R_o such that no more than $10 \mu\text{A}$ can flow to or from the body through the RL terminal. You may assume the body is near ground potential, and the opamp is powered with +5 V and -5 V. [3 pts]

11) Questions from 2 guest lectures as promised. Please write answer only in the space provided.

Wireless Non-contact ECG and EEG [2 pts]

a) Why is it necessary for a non-contact capacitive electrode to have a build-in amplifier?

b) How does the impedance of a capacitive electrode depend on the distance from the skin? Does it matter what material is in between the skin and electrode?

Wireless and Global Health Care [2 pts]

a) Which country has the highest infant mortality rate in the developed world?

b) What does Dr. Saldivar mean by “reverse tropicalization”?