

Name (Last, First): \_\_\_\_\_

## BENG 186B Winter 2014

### Final

- This exam is closed book, closed notes. Calculators are OK.
- Circle and put your final answers in the space provided; show your work only on the pages provided. Include units.
- Do not attach separate sheets. If you need more space, use the back of the pages. This exam has 25 pages, including this page.
- Points for each problem are given in [brackets], 100 points total.

1	/16
2	/08
3	/10
4	/08
5	/12
6	/10
7	/12
8	/10
9	/10
10	/4
Total	/100

Useful schematics and equations:

The Goldman-Hodgkin-Katz (GHK) equation:


$$E = (60mV) \cdot \log_{10} \frac{P_K [K^+]_o + P_{Na} [Na^+]_o + P_{Cl} [Cl^-]_i}{P_K [K^+]_i + P_{Na} [Na^+]_i + P_{Cl} [Cl^-]_o}$$

Common mode gain and differential gain:

$$v_o = A_d v_d + A_c v_{cm}$$


$$v_d = v_a - v_b$$

$$v_{cm} = (v_a + v_b) / 2$$

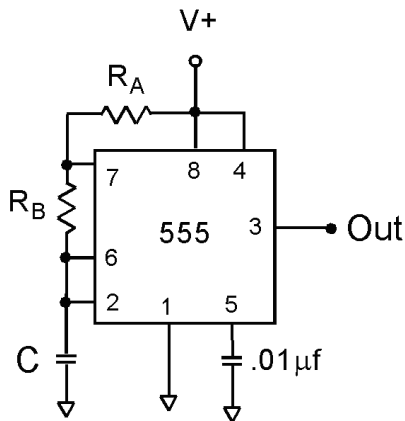

Oscillator
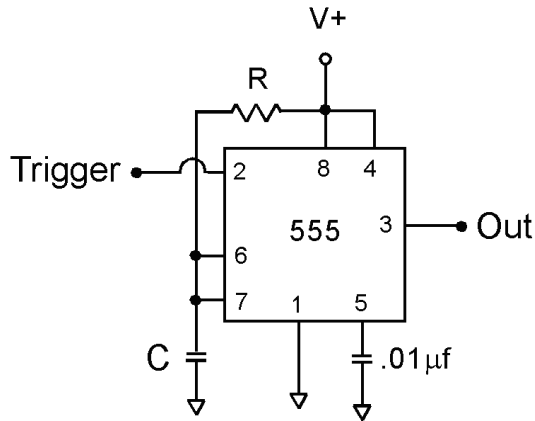
$$T_{High} = 0.7 (R_A + R_B) C ; T_{Low} = 0.7 R_B C$$



One-shot

$$T_{Pulse} = 1.1 R C$$

1) [16 pts] Indicate whether each of the following statements is true or false.

[ **TRUE / FALSE** ] One of the steps in the process of analog-to-digital signal conversion is sampling.

[ **TRUE / FALSE** ] The minimum sampling frequency is defined by the Nyquist criterion.

[ **TRUE / FALSE** ] Most sensors capture digital signals, which are then converted to analog for processing.

[ **TRUE / FALSE** ] A voltage divider is an example of a zeroth-order system.

[ **TRUE / FALSE** ] The average power dissipated by capacitors and inductors in a circuit is zero.

[ **TRUE / FALSE** ] A diode bridge rectifier is a useful way to rectify DC voltages to AC voltages

[ **TRUE / FALSE** ] The Nernst equation is a special case of the Goldman-Hodgkin-Katz equation.

[ **TRUE / FALSE** ] The ionic concentrations of cells are passively maintained by two processes: diffusion and ionic pump activation.

[ **TRUE / FALSE** ] Non-polarizable electrodes are preferred for bioinstrumentation measurements.

[ **TRUE / FALSE** ] A common-mode rejection ratio of 10 watts/watts can be expressed as 10 dB.

[ **TRUE / FALSE** ] The second-order dynamics of a fluid-filled catheter are due to the inertia and diffusivity of the fluid inside the tube.

[ **TRUE / FALSE** ] Range-gated (pulsed) Doppler imaging operates by measuring the delays in wave propagation and the frequency difference between the emitted and reflected signals.

[ **TRUE / FALSE** ] The Clark electrode presents a membrane permeable to O<sub>2</sub>, which allows it to measure the CO<sub>2</sub> concentration.

[ **TRUE / FALSE** ] A potentiostat can be used to measure the concentration of O<sub>2</sub> due to the linear relationship between concentration and electric current when a polarizing voltage is applied between Pt and Ag/AgCl electrodes in a salt buffer solution.

[ **TRUE / FALSE** ] The isosbestic wavelength defines where the maximum difference between the absorptivities of oxygenated hemoglobin and reduced hemoglobin occurs.


[ **TRUE / FALSE** ] Diodes can be an effective way of protecting your circuit from over-voltage.

2) **[8 pts]** Short answer, write your answer only in the space provided.


a) Draw a circuit that realizes a high-pass filter with 1 kHz cutoff frequency. Minimize the number of components, and label input and output. [2 pts]

b) For a signal with a range of 1.28 V and 4-bit representation, find the resolution of one least significant bit (1 LSB). [2 pts]

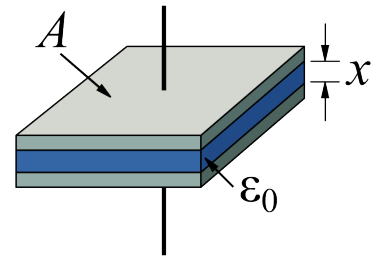c) For a capacitive sensor of transversal displacement as shown below, derive the sensitivity of the sensor as a function of  $\epsilon_0$ ,  $A$ , and  $x$ . [2 pts]



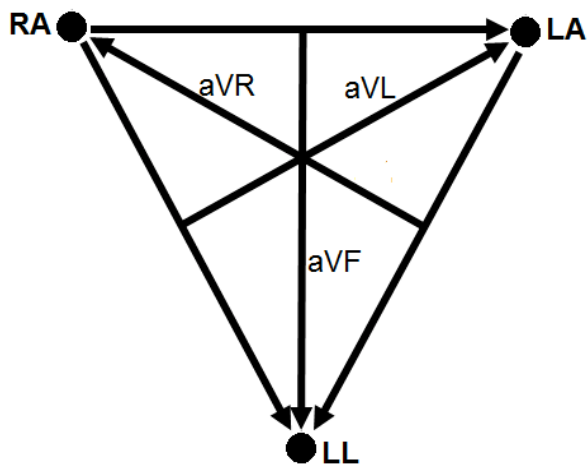d) Given the Einthoven's triangle, write the most simplified expression for the cardiac leads in terms of the potentials RA, LA, and LL. [2 pts]




aVR = \_\_\_\_\_

aVL = \_\_\_\_\_

aVF = \_\_\_\_\_

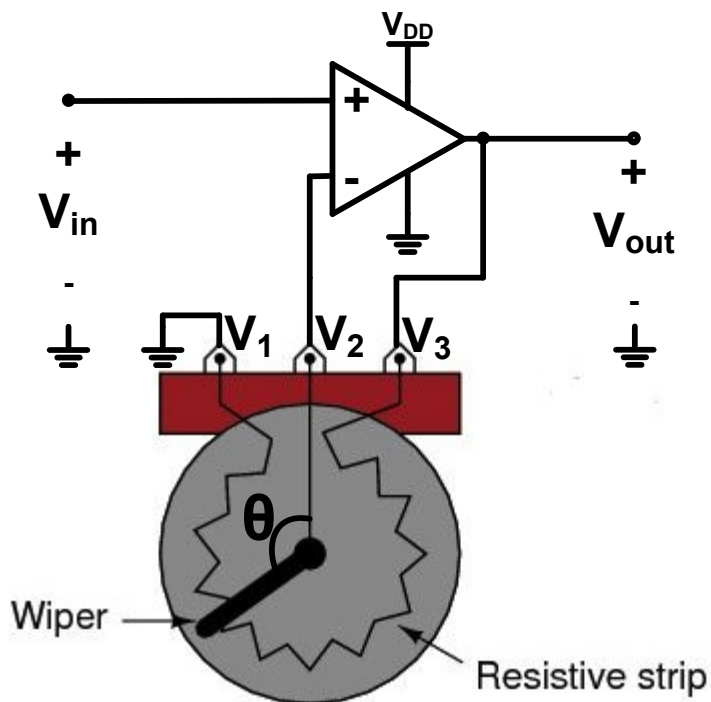3) [10 pts] Consider the following circuit. The potentiometer has a total resistance of  $10\text{ k}\Omega$  and its angle  $\theta$  ranges from  $10^\circ$  to  $350^\circ$ .



a) Find  $\theta$  for a gain ( $V_{out}/V_{in}$ ) of 4. [6 pts]

b) Find the minimum and maximum achievable gain of the circuit. Show how to change the circuit to limit the maximum gain to 10. [4 pts]

4) [8 pts] The resting potential of a cell separated from extracellular fluid by a membrane permeable to  $\text{Na}^+$ ,  $\text{K}^+$ , and  $\text{Cl}^-$  is measured at 37 °C. Refer to the table for individual ion concentrations found during the experiment.

<b>Ion</b>	<b>Intracellular concentration (mM)</b>	<b>Extracellular concentration (mM)</b>
<b><math>\text{Na}^+</math></b>	10	145
<b><math>\text{K}^+</math></b>	140	5
<b><math>\text{Cl}^-</math></b>	4	110

a) Find the Nernst potential for each ion type. [3 pts]




b) When we apply a pharmacological blocker that makes the membrane impermeable to  $K^+$ , the resting potential is found to be 30 mV. What is the permeability of  $Cl^-$  relative to that of  $Na^+$ ? [2 pts]

c) Now assume that the cell membrane is only permeable to  $K^+$  ions. How many  $K^+$  ions would have to cross the membrane to lower the membrane potential by 70 mV, and in which direction? Assume the membrane capacitance of the cell to be  $1 \mu F/m^2$  and that the cell is a sphere with diameter of 10  $\mu m$ . [3 pts]


5) [12 pts] A crack team of bioengineers developed a glucose meter for their senior design project. You will now get to analyze their basic circuit design to see how it behaves.

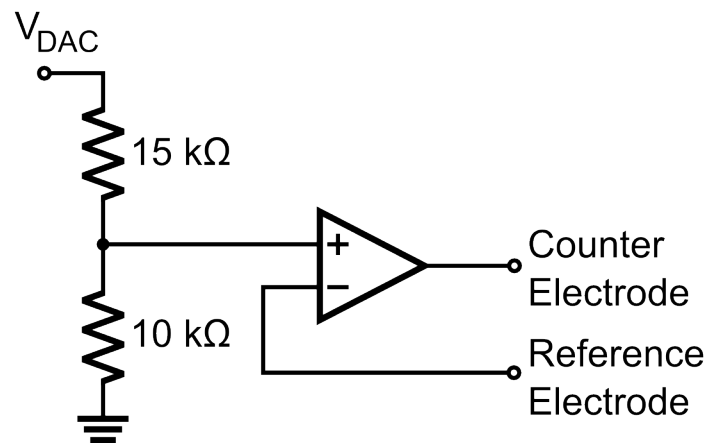- a) The glucose test strip needs a bias voltage applied to its counter electrode to work. The team used the following circuit:



The op-amp is ideal, and there is a feedback path through the test strip between the counter and reference electrode. If  $V_{DAC}$  is equal to 1 V, what is the voltage at the reference electrode? (*Hint*: what can you say about the two op-amp inputs?) [2 pts]

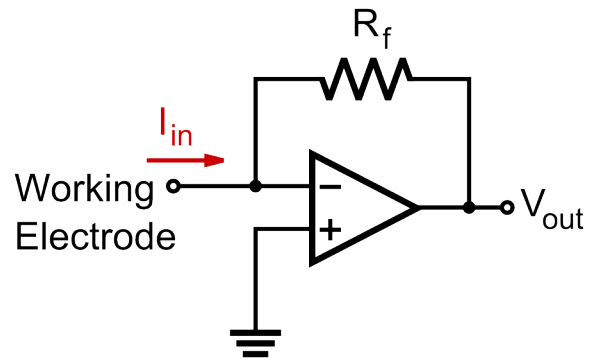
- b) When the bias voltage and a glucose sample are applied to the test strip, it produces a small amount of current through its working electrode. The transimpedance amplifier shown below converts this current to a voltage:



The op-amp is ideal. **Derive from first principles** the transfer function  $V_{out}/I_{in}$  for the above circuit. [2 pts]

- c) Why is this circuit better than a simple resistor? [2 pts]

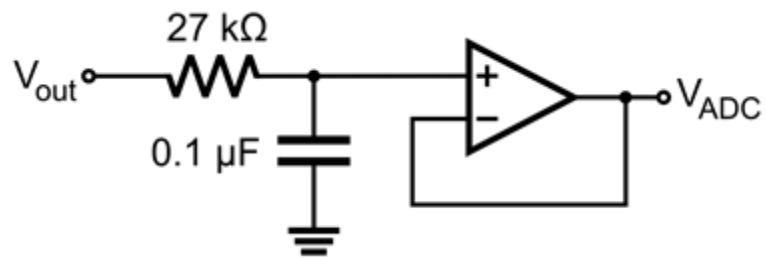d) The team also used the following circuit to filter the output of the transimpedance amplifier before it is read by the ADC:



The op-amp is ideal. **Derive from first principles** the transfer function for the above circuit. What kind of filter is this and what is the cutoff frequency? [4 pts]


e) **[BONUS 4 pts]** Show how to implement this function without this additional circuit by modifying the transimpedance amplifier.

f) The team calibrated their circuit against standard glucose solutions to obtain the following transfer function:

$$B_{\text{ADC}} = -53.05 \frac{\text{L}}{\text{mmol}} \times [\text{Glucose}] - 47.5$$

[Glucose] is the glucose concentration in mmol/L, while  $B_{\text{ADC}}$  is the output reading in arbitrary units. What is the sensitivity of the device? [2 pts]

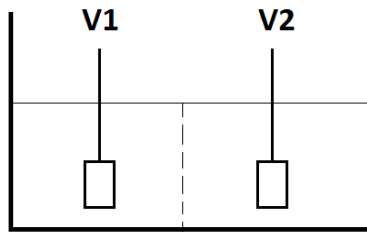6) [10 pts] The following set up is used to sense pH. The membrane separating chamber 1 and 2 is only permeable to  $H^+$ . Both chambers have Ag/AgCl electrodes with  $E_{hc} = 0.223$  V, series resistance of  $1\text{ k}\Omega$ , double layer resistance of  $100\text{ k}\Omega$ , and double layer capacitance of  $10\text{ pF}$ . The resistance of the  $H^+$ -permeable membrane is  $2\text{ M}\Omega$ .



a) What is the polarity of the voltage  $V1-V2$  measured by a voltmeter of infinite impedance when chamber 1 contains a strong acid and chamber 2 contains a weak base. [1 pt]


b) What is the expected  $V1-V2$  when chamber 1 contains  $10\text{ mmol/L KCl}$  solution and chamber 2 contains  $1\text{ mmol/L HCl}$  solution? [2 pts]

c) You now find out from the manufacturer of the electrodes that the two electrodes used are not identical and produce an open circuit voltage  $V_1 - V_2$  of 0.02 V when immersed in the same solution. How does this affect the expected voltage in part (b)? [1 pt]


d) Write the equivalent impedance between the electrodes as a function of radial frequency  $\omega$ . [3 pts]

- e) Plot the magnitude (in dB) and the phase (in degrees) of the impedance as a function of frequency  $f$  (in Hz) and specify the corner frequencies. [3 pts]

Magnitude

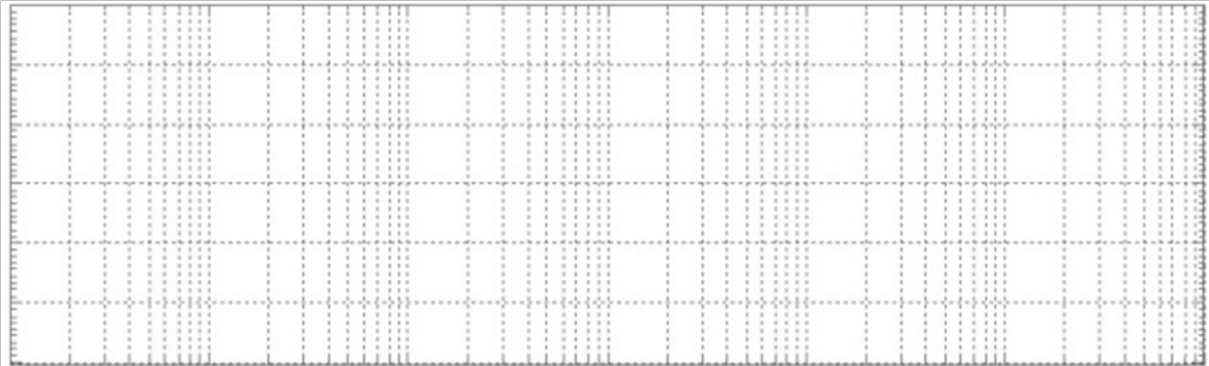


Phase

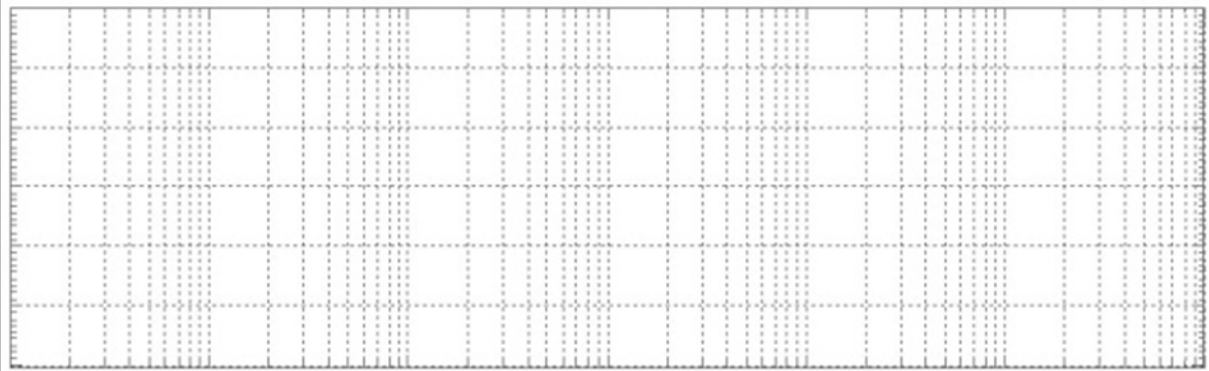



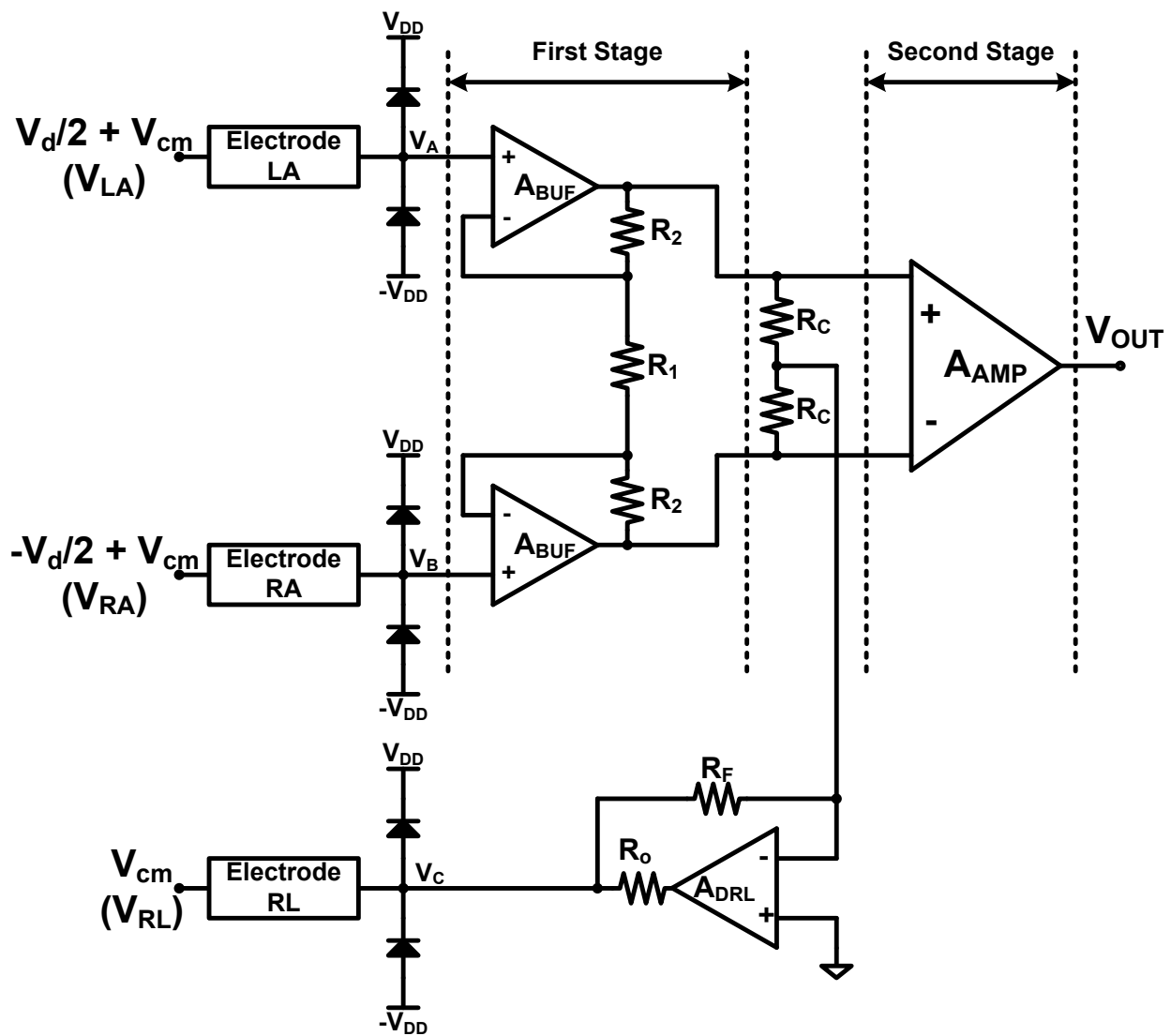7) [12 pts] An instrumentation amplifier (IA) with driven right leg active grounding common-mode suppression is shown below. The IA has resistances  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$ ,  $R_C = 20 \text{ k}\Omega$ ,  $R_F = 1 \text{ M}\Omega$ , and  $R_O = 1 \text{ M}\Omega$ . The IA second stage  $A_{AMP}$  has differential gain of 100 V/V and common-mode gain of 0 V/V. Assume the amplifiers  $A_{BUF}$  are ideal.



a) Assume the protection diodes are ideal with turn-on voltage of 0.7 V. Find the resulting voltage range at  $V_A$ ,  $V_B$ , and  $V_C$ . [2pts]


b) The body couples to a 60 Hz, 110 Vrms outlet with 1 pF capacitance. Find the rms amplitude of the displacement current entering the body. (*Hint*: for this part, you may assume the body is practically at ground potential) [2 pts]

c) Electrode RL connects to the body with an impedance of  $100\text{ k}\Omega$ . For a  $2\text{ mV}_{\text{rms}}$  differential input  $V_d$ , find the signal-to-noise ratio  $\text{SNR}_{\text{IN}}$  in dB at each of the input nodes  $V_A$  and  $V_B$  for the displacement current found in part (b). [2 pts]

d) Assume the electrode-body impedances of LA and RA are  $90\text{ k}\Omega$  and  $110\text{ k}\Omega$ , respectively. Find the common-mode rejection ratio CMRR and output signal-to-noise ratio  $\text{SNR}_{\text{OUT}}$  in dB. [2 pts]

e) Each protection diode has a parallel resistance of  $400 \text{ M}\Omega$ . Now find the resulting CMRR and  $\text{SNR}_{\text{OUT}}$  in dB. [4 pts]

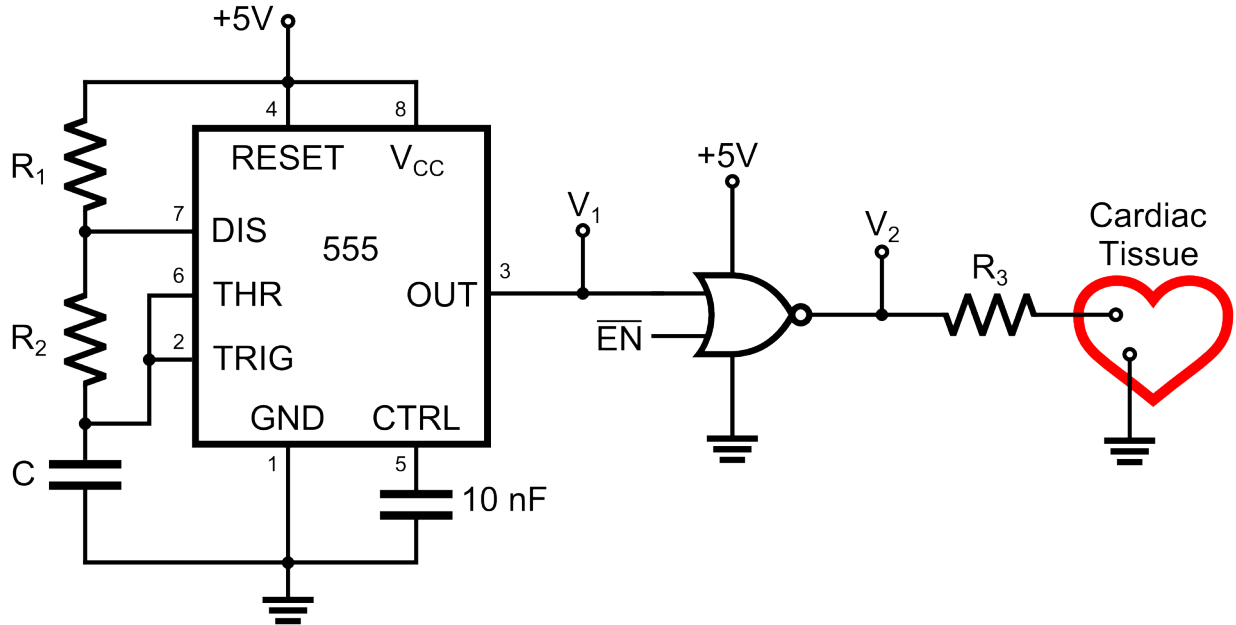8) [10 pts] The circuit below is used to generate a pacemaker drive signal. It is powered by a +5V battery, and has an “enable” input labeled  $\overline{EN}$ . The output of the circuit connects through an electrode to cardiac tissue. The values of the components are  $R_1 = 200 \text{ k}\Omega$ ,  $R_2 = 500 \text{ k}\Omega$ ,  $R_3 = 10 \text{ k}\Omega$ , and  $C = 1 \text{ }\mu\text{F}$ .



a) Plot the waveform seen at  $V_1$ . [4 pts]

b) What is  $V_2$  when  $\overline{EN} = 1$ ? [2 pts]

c) What is  $V_2$  when  $\overline{EN} = 0$ ? [2 pts]

d) What is the maximum current entering the body? [2 pt]

9) **[10 pts]** Congratulations! You just landed an internship at a major bioinstrumentation company. Your first assignment is to design an infant ECG device with the following specifications:

- Band-pass filtering between 0.1 Hz and 1 kHz corner frequencies.
- Amplification of the 1 mVpp ECG differential signal by 60 dB.
- Level-crossing detection with 20 mV hysteresis to produce a square wave output signal at the heartbeat frequency.

You have two electrodes, a single 2.5 V battery, ideal op-amps, and any required resistors and capacitors. Be sure to label all components, inputs, outputs, and needed values.





10) [4 pts] Questions from guest lectures. Please write your answer only in the space provided.

Wireless non-contact ECG and EEG

- a. Name two characteristics of the circuit that are compromised due to the extremely high impedance of the non-contact sensors. [1 pt]
  
  
  
  
  
  
  
  
  
  
- b. What kind of artifacts is still the major challenge for this type of electrode? [1 pt]

Wireless medical technology in global health

- a. Name two applications of wireless technology in health care. [1 pt]
  
  
  
  
  
  
  
  
  
  
- b. Which developed country presents the highest health expenditure per capita? [1 pt]