

BENG 186B Winter 2012

Quiz 2


February 15, 2012

NAME (Last, First):

- This quiz is closed book and closed note. You may use a calculator for algebra.
- Circle your final answers in the space provided; show your work only on the pages provided.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- Points for each problem are given in [brackets], 100 points total. The quiz is 50 minutes long.

1	/20
2	/30
3	/20
4	/30
Total	/100

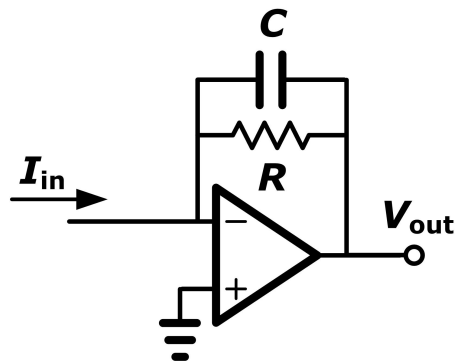1. [20 pts] Consider the following active filter circuit with current input I_{in} and voltage output V_{out} . You may assume that the op-amp is ideal.




- a. Derive the transfer function $H(j\omega) = V_{out}(j\omega)/I_{in}(j\omega)$ in terms of C and R . What are the units of the transfer function? What type of filter is this? [10 pts]




b. Derive the input impedance $Z_{in}(j\omega)$. [5 pts]

c. Derive the output impedance $Z_{out}(j\omega)$. [5 pts]

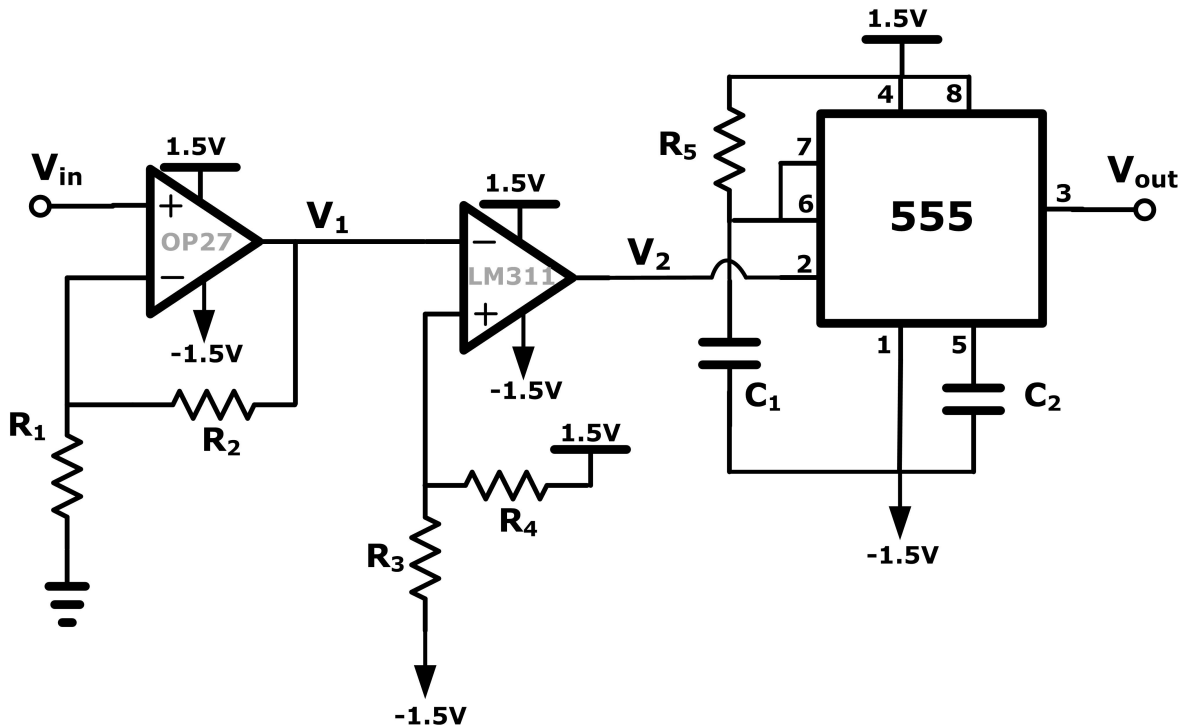2. [30 pts] The following circuit is driven by voltage input V_{in} and generates voltage output V_{out} as shown below. The components OP27, LM311, 555 are assumed ideal, each with positive supply 1.5 V and negative supply -1.5 V. Sketch the waveforms for the voltages V_1 , V_2 and V_{out} on the diagrams on the next page. Show your work below.




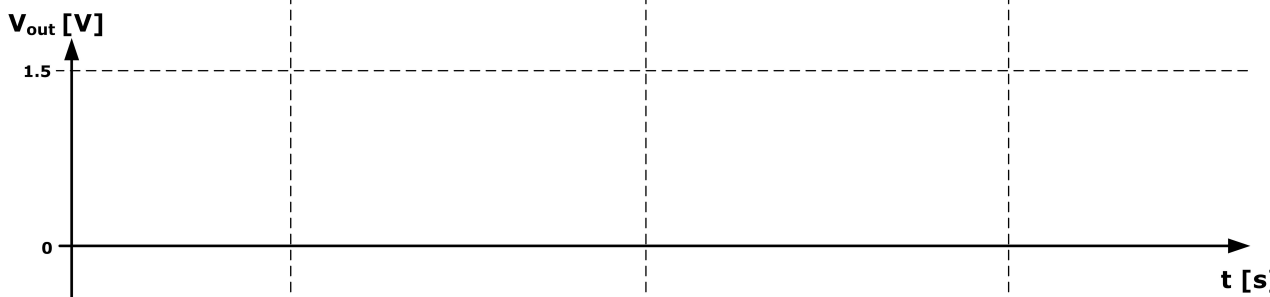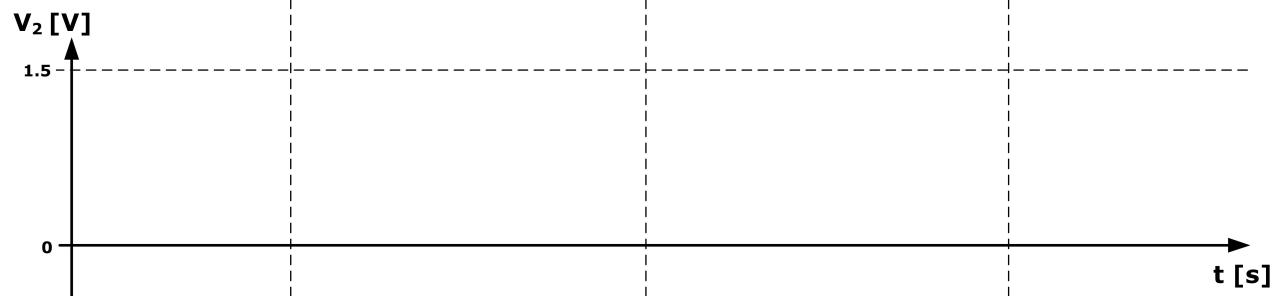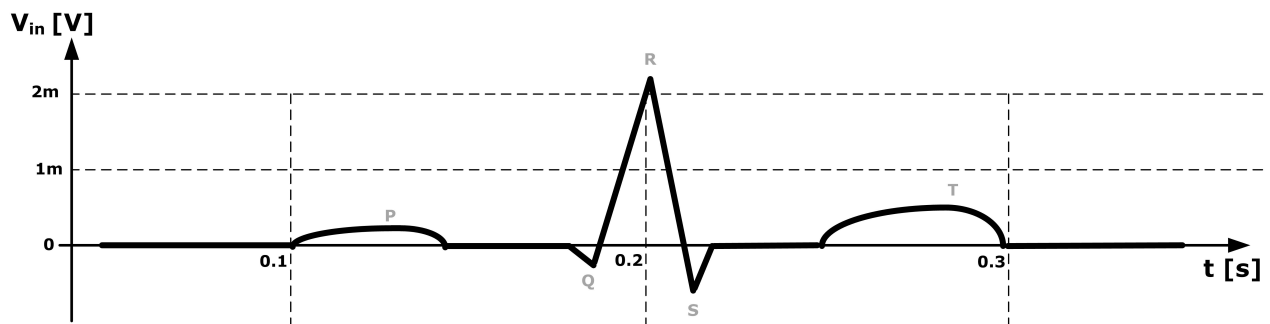$R_1 = 1 \text{ k}\Omega$, $R_2 = 999 \text{ k}\Omega$, $R_3 = 250 \text{ k}\Omega$, $R_4 = 50 \text{ k}\Omega$, $R_5 = 100 \text{ k}\Omega$
 $C_1 = 910 \text{ nF}$, $C_2 = 10 \text{ nF}$. The equation for the 555 is: $T = 1.1 R_5 C_1$.




3. [20 pts] Circle the best answer (circle only one letter for each question).

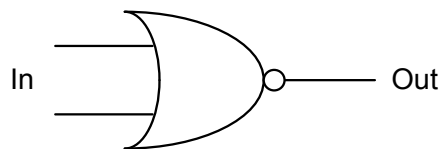- a. The Goldman-Hodgkin-Katz (GHK) equation:
- Solves for non-equilibrium membrane potentials
 - Yields zero membrane potential if impermeable
 - Yields a positive membrane potential for most excitable cells
 - Yields the inside minus outside potential at rest
 - Yields the outside minus inside potential at rest
- b. Axon myelination decreases:
- Membrane capacitance
 - Action potential propagation speed
 - Baseline membrane potential
 - QRS complex duration
 - Heart rate
- c. The highest frequency EEG wave is:
- Alpha, α
 - Beta, β
 - Gamma, γ
 - Delta, δ
 - Theta, θ
- d. In an ECG, the P wave:
- Represents ventricular repolarization
 - Is missing during atrial fibrillation
 - Increases during epilepsy
 - Detects eye movement/blinking
 - Represents depolarization after the AV node
- e. The following symbol represents which circuit component?




- AND Logic Gate
- NAND Logic Gate
- OR Logic Gate
- NOR Logic Gate
- Op-Amp

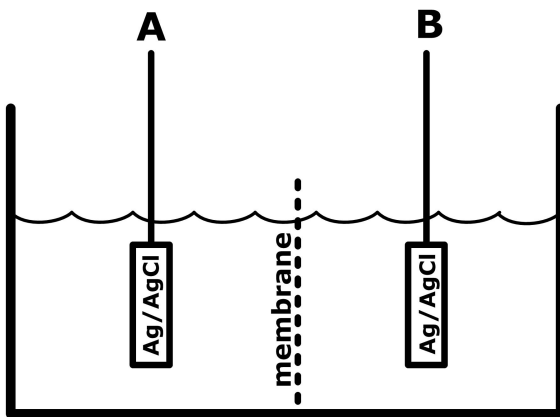4. [30 pts] A membrane separates a container into two compartments as shown below. The “inside” compartment (A) contains a solution of 100 mmol of NaCl and 10 mmol of KCl in 1 L of water. The “outside” compartment (B) contains a solution of 1 mmol of NaCl and 10 mmol of KCl in 1 L of water. Two identical Ag/AgCl electrodes are immersed, one in each compartment. For each Ag/AgCl electrode, the half cell potential E_{hc} is 0.223 V, and the impedance parameters are $R_d = 320 \text{ k}\Omega$, $C_d = 10 \text{ pF}$, and $R_s = 10 \text{ k}\Omega$. The membrane has equal permeabilities to all three ions.



Ag/AgCl electrode

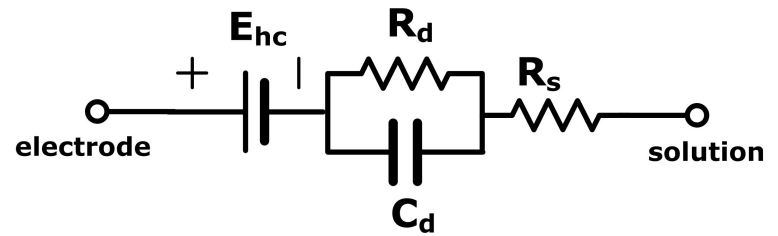

The Goldman-Hodgkin-Katz (GHK) equation:

$$E = (60mV) \cdot \log_{10} \frac{P_K [K^+]_o + P_{Na} [Na^+]_o + P_{Cl} [Cl^-]_i}{P_K [K^+]_i + P_{Na} [Na^+]_i + P_{Cl} [Cl^-]_o}$$

- a. Find the Nernst potential of Na^+ , K^+ and Cl^- . [5 pts]

b. Derive the voltage between nodes A and B at rest. [10 pts]

c. Derive and sketch the impedance $Z(j\omega)$ between nodes A and B as a function of ω . You may assume that the resistance for ion transport across the membrane R_{mem} is $1 \text{ M}\Omega$. [15 pts]

