

# **BENG 186B Winter 2014**

## **Quiz 2**

February 12, 2014


**NAME (Last, First):**

---

- This quiz is closed book and closed notes. You may use a calculator for algebra.
- Circle your final answers in the space provided; show your work only on the pages provided.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- There are 5 problems. Points for each problem are given in [brackets]. There are 100 points total. You have 50 minutes to complete this quiz.

1	/ 20
2	/ 25
3	/ 20
4	/ 20
5	/ 15
Total	/ 100

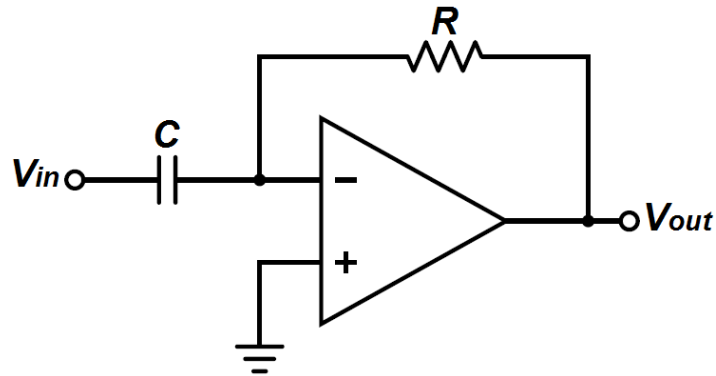1. [20 pts] Consider the following active circuit with voltage input  $V_{in}$  and voltage output  $V_{out}$ . You may assume that the op-amp is ideal.



- a) [10 pts] Derive the transfer function  $H(j\omega) = V_{out}(j\omega)/V_{in}(j\omega)$ . Which function does this circuit perform?

b) [5 pts] Derive the input impedance  $Z_{in}(j\omega)$ .


c) [5 pts] Derive the output impedance  $Z_{out}(j\omega)$ .

2. [25 pts] Consider the following circuit, with ideal components OP27, LM311, and 555.

The dynamics of the leftmost 555 system is governed by equations  $T_{high} \cong 0.7(R_1 + R_2)C_2$  and  $T_{low} \cong 0.7R_2C_2$ .

The dynamics of the rightmost 555 system is governed by equation  $T \cong 1.1R_3C_3$ .

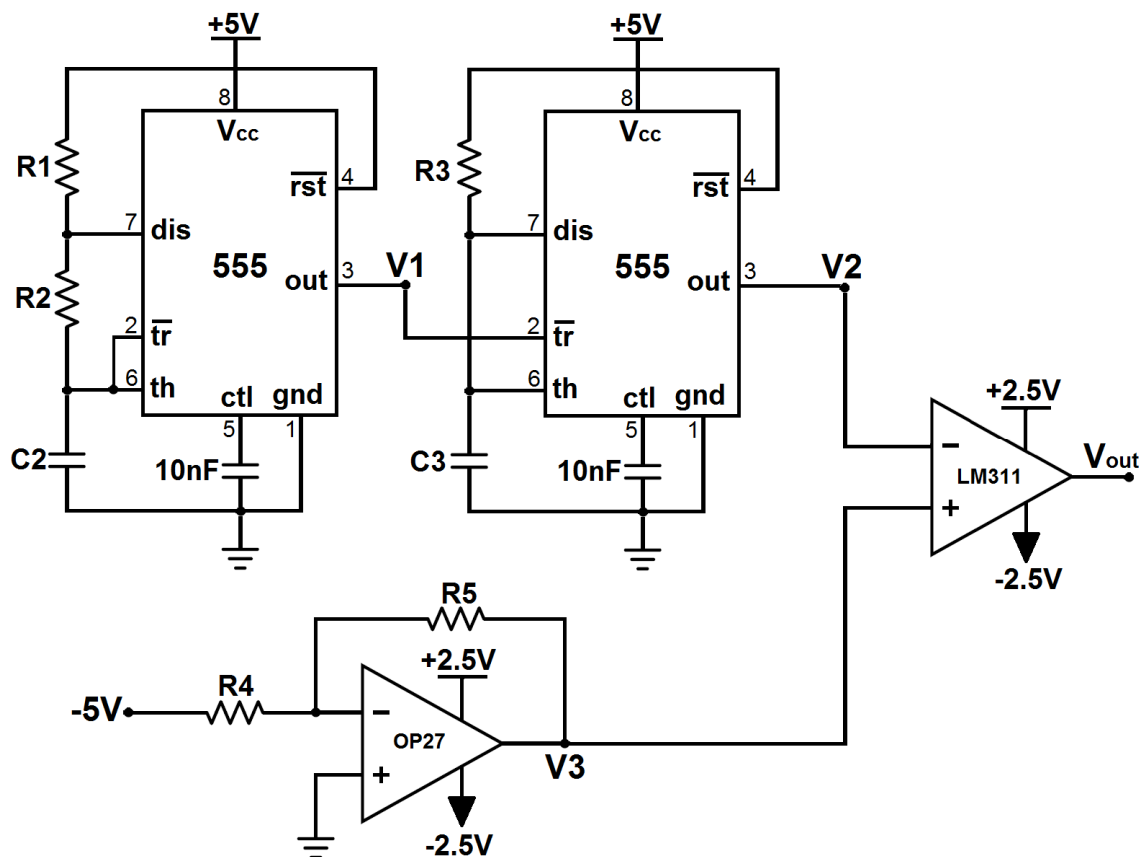(Hint: Try to approximate your solutions to facilitate the calculations.)



$$\begin{aligned}
 R1 &= 100\text{k}\Omega & R3 &= 9\text{k}\Omega & R4 &= 47\text{k}\Omega \\
 R2 &= 100\text{k}\Omega & C3 &= 0.5\mu\text{F} & R5 &= 47\text{k}\Omega \\
 C2 &= 0.5\mu\text{F}
 \end{aligned}$$


Sketch the waveforms for  $V_1$ ,  $V_2$ ,  $V_3$ , and  $V_{out}$  on the diagrams on next page, clearly indicating the voltage levels and time intervals of the transitions in the waveforms. Show your work below.



3. [20 pts] Circle the best answer (only one answer per question):


a) [6 pts] The following inverting hysteretic comparator transitions from -2V to +2V and from +2V to -2V when  $V_{in}$  crosses respectively:

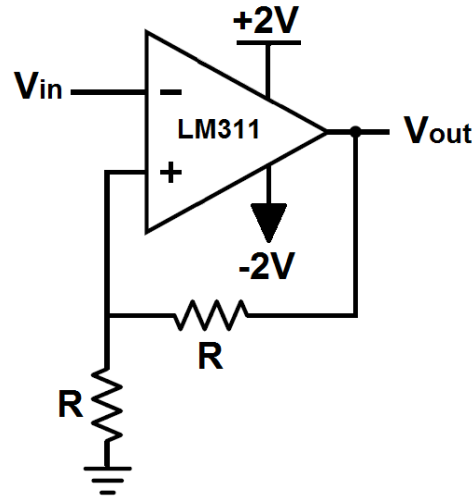- i. -0.1V and +0.1V
- ii. +1.0V and -1.0V
- iii. -0.5V and +0.5V
- iv. +2.0V and -2.0V
- v. None of the above



b) [6 pts] The output  $C$  in the digital circuit can be represented as:

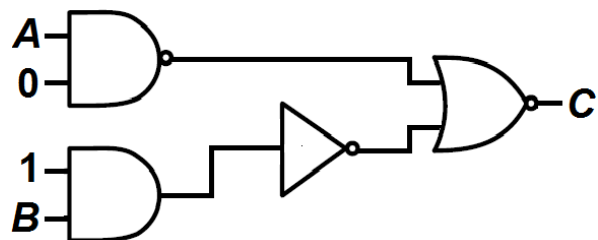- i.  $AND(A,B)$
- ii.  $A$
- iii.  $B$
- iv.  $0$
- v.  $1$



c) [8 pts] Indicate whether each of the following statements is true or false:

[ **TRUE / FALSE** ] The Nernst potential can only be measured across a membrane when it is permeable to the specific ion type being analyzed.

[ **TRUE / FALSE** ] The typical resting potential of excitable cells in the human body is positive.

[ **TRUE / FALSE** ] The permeability of the ion affects its Nernst potential.

[ **TRUE / FALSE** ] The action potential and synaptic potential are actually special cases of the membrane potential.

[ **TRUE / FALSE** ] The action potential in neurons is usually triggered by the influx of  $\text{Na}^+$  ions and propagates down the axon.


[ **TRUE / FALSE** ] Atrial repolarization is normally not observed in ECGs due to the ventricular repolarization.

[ **TRUE / FALSE** ] Despite being non-invasive, electroencephalography has higher temporal resolution than electrocorticography.

[ **TRUE / FALSE** ] The half-cell potential of electrodes is simply a function of the electrode material.



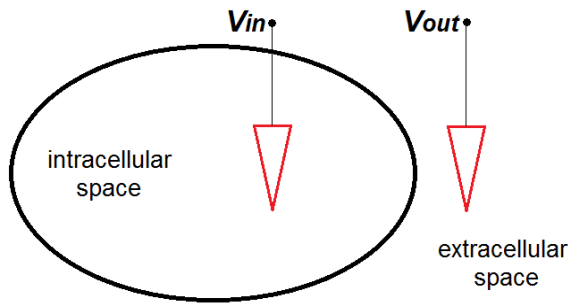4. [20 pts] Two identical electrodes are inserted in the intracellular and extracellular media of a cell, with the cell membrane separating both media. The concentrations are given in the table. At rest, the membrane permeability to  $\text{Cl}^-$  is twice that of the permeability to  $\text{Na}^+$  and  $\text{K}^+$ .



Solution	Intra (mM)	Extra (mM)
NaCl	10	100
KCl	110	20


The Goldman-Hodgkin-Katz (GHK) equation is given by:

$$E = (60mV) \log_{10} \frac{P_K[K^+]_o + P_{Na}[Na^+]_o + P_{Cl}[Cl^-]_i}{P_K[K^+]_i + P_{Na}[Na^+]_i + P_{Cl}[Cl^-]_o}$$

a) [10 pts] Find the Nernst potentials for  $\text{Na}^+$  and  $\text{Cl}^-$ .

b) [10 pts] Find the value of the equilibrium rest potential of the cell.

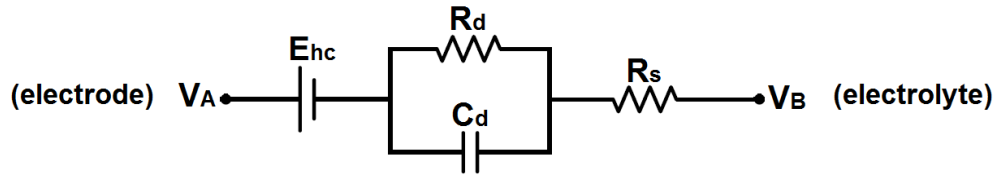5. [15 pts] The circuit model for a non-polarizable electrode is shown below.



a) [10 pts] Write the impedance between the electrode and electrolyte as a function of radial frequency  $\omega$ , and in the two limiting cases of very low frequency and very high frequency.

b) [5 pts] Two identical electrodes are immersed in the same solution. Find the open-circuit voltage, and closed-loop current, between the electrodes.