

# BENG 186B Winter 2015


## Quiz 2

Wednesday, February 11, 2015

*Last Name, First Name:* \_\_\_\_\_

- This quiz is closed book and closed notes. You may use a calculator for algebra and arithmetic.
- This quiz has 10 pages, including this cover sheet. Do not attach separate sheets. If you need more space, use the back of the pages.
- Circle or box your final answers and show your work on the pages provided.
- There are 4 problems. Points for each problem are given in **[brackets]**. There are 100 points total.
- You have 50 minutes to complete this quiz.

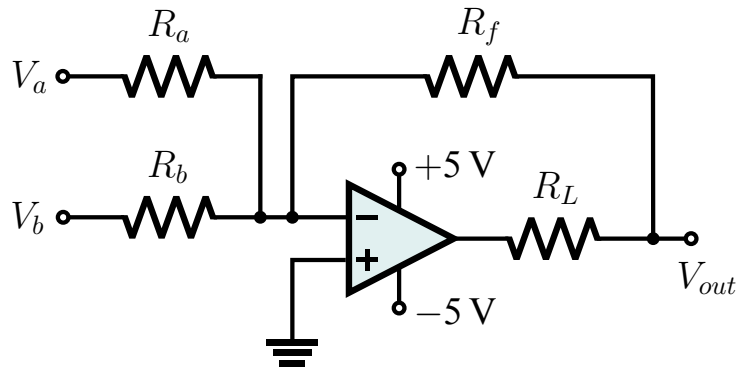1. [30 pts] Consider the following circuit:




(a) Assume the operational amplifier is ideal and unsaturated. Derive **from first principles** an expression for  $V_{out}$  in terms of  $V_a$  and  $V_b$ .

- (b) Does the  $V_{out}$  expression from part (a) depend on  $R_L$ ?
- (c) What is the maximum current drawn from the operational amplifier during a short circuit at the output,  $V_{out} = 0$ ? What function does  $R_L$  serve? *Hint*: Consider the voltage supplies of the operational amplifier.
- (d) What are the input impedances of the two inputs?
- (e) You can use the above circuit to produce an inverted average of the inputs:

$$V_{out} = -\frac{V_a + V_b}{2}$$

Based on the  $V_{out}$  expression from part (a), what values for  $R_a$ ,  $R_b$ , and  $R_f$  could you use to achieve this?

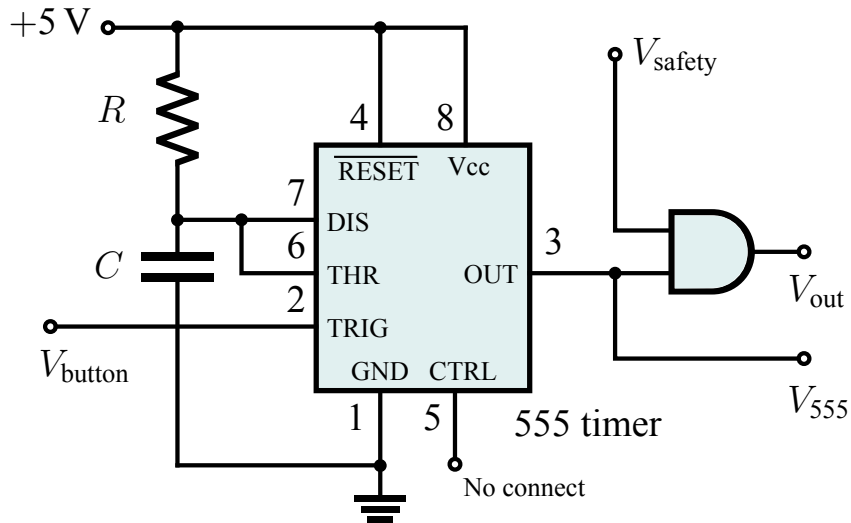2. [25 pts] The circuit shown below controls an automatic syringe pump. It is designed to deliver a fixed amount of fluid in response to each press of a button. The pump motor is controlled via  $V_{out}$  and can deliver 1 mL of fluid per second. The pump includes a “dead-man’s” switch for safety purposes.





You may find these equations useful ( $\ln(3) \approx 1.1$  and  $\ln(2) \approx 0.7$ ):

$$T = \ln(3) \times RC \quad T_{lo} = \ln(2) \times R_2C \quad T_{hi} = \ln(2) \times (R_1 + R_2)C$$

- (a) What numerical values for  $R$  and  $C$  could you use so that the syringe pump delivers 2 mL of fluid per button press?

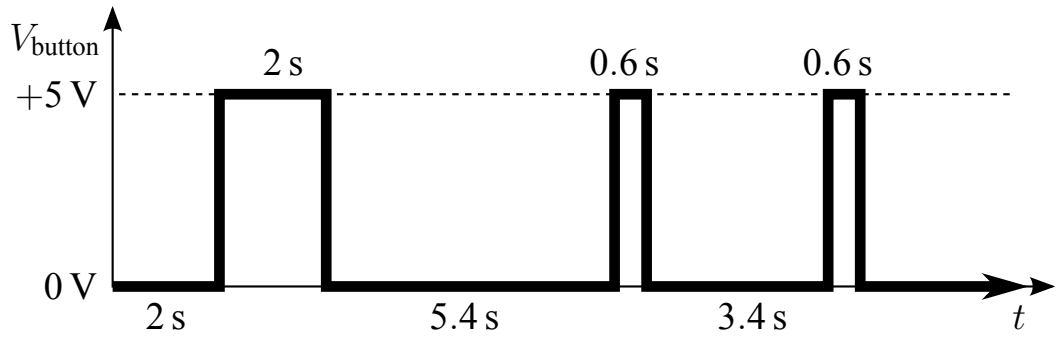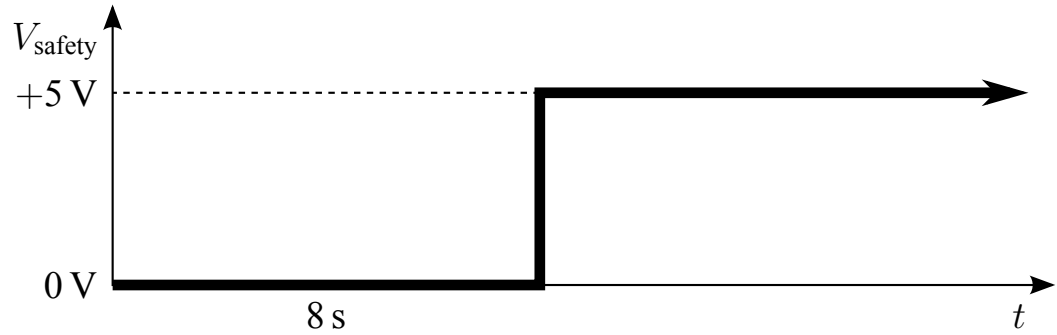
(b) Shown below are waveforms for  $V_{\text{button}}$  and  $V_{\text{safety}}$ . Given these inputs, draw **and fully label** the output waveforms for  $V_{555}$  and  $V_{\text{out}}$ .



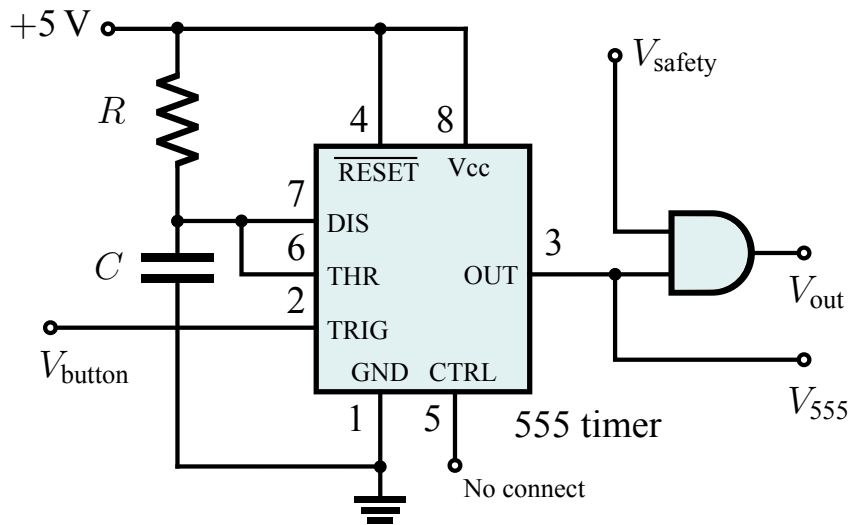(c) The syringe itself contains a sensor with a voltage output that varies linearly with respect to fluid volume. In particular, the sensor outputs:

- 0 V when the syringe is completely empty; and
- 5 V when the syringe is completely full.


Modify the circuit, copied below, so that the pump is disabled when the syringe is less than 10% full. **Be sure to label all components and their values, if applicable.** You may directly annotate changes on the copy below.



3. [20 pts] Circle the **best answer** (only one answer per question):


(a) [4 pts] The logic circuit shown on the right is equivalent to:

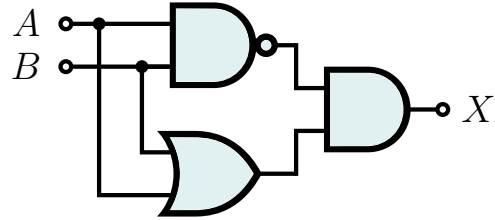- i.  $X = \text{AND}(A, B)$
- ii.  $X = \text{OR}(A, B)$
- iii.  $X = \text{XOR}(A, B)$
- iv.  $X = \text{NAND}(A, B)$
- v. none of the above



(b) [4 pts] The circuit shown on the right implements what function?

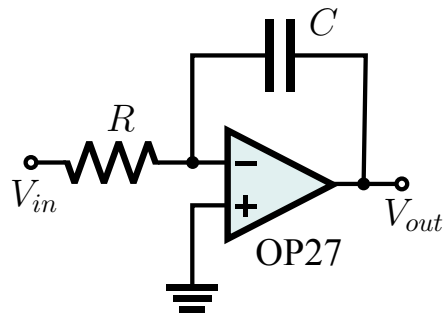- i. non-inverting low-pass filter
- ii. inverting high-pass filter
- iii. inverting integrator
- iv. non-inverting differentiator
- v. none of the above



(c) [4 pts] The following takes place at the electrode-electrolyte interface for electrochemical transduction:

- i. negative basic molecules react non-reversibly with positive acidic molecules on the electrode
- ii. anions from the electrolytes switch places with the cations on the electrode
- iii. water cleaves electrons off the electrode and reacts with the resulting cations
- iv. cations flow across the electrode-electrolyte interface while electrons flow in the electrode in the opposite direction
- v. none of the above

(d) [8 pts] Indicate for each statement below whether it is true or false:

- i. **TRUE / FALSE:** During depolarization the net charge inside the cell shifts from negative to positive.
- ii. **TRUE / FALSE:** The SA node depolarizes the right atrium which in turn triggers the AV node to depolarize the ventricles.
- iii. **TRUE / FALSE:** The T wave represents ventricular depolarization.
- iv. **TRUE / FALSE:** Skin impedance and noise from skeletal muscles are significant issues when non-invasively measuring signals farther inside the body.
- v. **TRUE / FALSE:** Electroretinograms (ERG) involve a series of high-contrast images shown to patients to help measure their retinal response.
- vi. **TRUE / FALSE:** An Ag electrode injecting a positive current into chlorine electrolyte causes deposition of an AgCl layer.
- vii. **TRUE / FALSE:** Cell permeability to an ion is relevant when using the GHK equation, but the individual Nernst can be determined even if the cell is not permeable to the ion type.
- viii. **TRUE / FALSE:** Ion pumps in the membrane are constantly keeping the Nernst potential fixed at the resting state.



4. [25 pts] A typical mammalian cell contains the following ion concentrations:

Ionic species	Concentration (mM)	
	Intracellular	Extracellular
$K^+$	400	20
$Na^+$	50	400
$Cl^-$	40	550
$Ca^{2+}$	0.0001	5

(a) What is the Nernst potential for each ionic species?

(b) Given these relative permeabilities and the GHK equation:

$$P_K = 1 \quad P_{Na} = 0.01 \quad P_{Cl} = 2 \quad P_{Ca} = 0$$
$$V_m = 60 \text{ mV} \times \log \left( \frac{P_{Na}[\text{Na}^+]_o + P_K[\text{K}^+]_o + P_{Cl}[\text{Cl}^-]_i}{P_{Na}[\text{Na}^+]_i + P_K[\text{K}^+]_i + P_{Cl}[\text{Cl}^-]_o} \right)$$

What is the equilibrium membrane potential  $V_m$  of the cell?

(c) Assume the capacitance of the cell membrane is  $1 \mu\text{F}/\text{cm}^2$ , and that you have a spherical cell  $10 \mu\text{m}$  in diameter. Calculate how many  $\text{K}^+$  ions must cross the membrane to change its potential by  $10 \text{ mV}$ . *Hint:* The charge of a proton is  $1.6 \times 10^{-19} \text{ C}$ .