

BENG 186B Winter 2018

Quiz 1

Friday, January 26, 2018

Name (Last, First): _____

- This quiz is closed book and closed notes. You may use a calculator for algebra and arithmetic.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- Circle or box your final answers and show your work on the pages provided.
- There are 4 problems. Points for each problem are given in **[brackets]**. There are 100 points total.
- You have 50 minutes to complete this quiz.

1. [10 pts] Circle the **best answer (only one answer per question)**:

(a) [2.5 pts] Indirect physiological measurements are typically:

- i. higher bandwidth.
- ii. more accurate.
- iii. more expensive.
- iv. less invasive.

(b) [2.5 pts] The transfer function of a critically damped second-order low-pass filter has:

- i. two complex conjugate poles.
- ii. two identical real poles.
- iii. one real zero and one real pole.
- iv. one real zero and one imaginary pole.


(c) [2.5 pts] The gauge factor of a strain gauge is independent of:

- i. piezo-resistive effect.
- ii. Poisson's ratio.
- iii. Young's modulus.
- iv. temperature.

(d) [2.5 pts] A linear variable differential transformer is a type of inductive sensor that offers:

- i. zero offset.
- ii. greater linearity.
- iii. greater noise suppression.
- iv. all of the above.

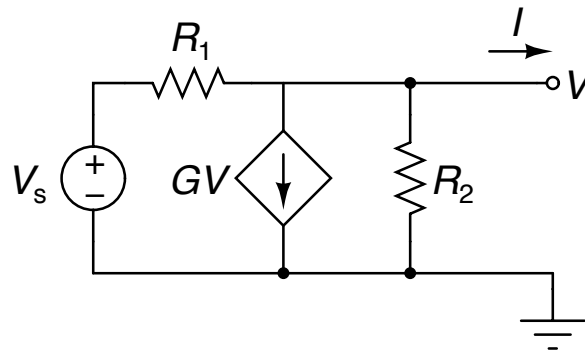2. [25 pts] Derive the Thévenin equivalent at node V in the circuit below:




(a) [10 pts] Find the Thévenin equivalent open-circuit voltage V_{oc} .

(b) [10 pts] Find the Thévenin equivalent impedance Z_{th} .

(c) [5 pts] Draw the Thévenin equivalent diagram.

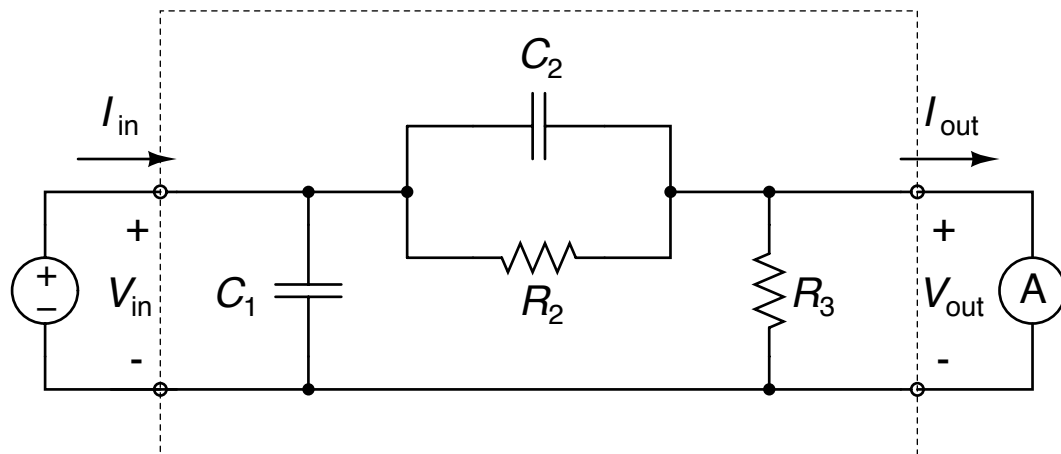3. [35 pts] Consider the voltage-input, current-output filter circuit below.




(a) [10 pts] Find the input impedance $Z_{in}(j\omega)$.

(b) [10 pts] Find the output impedance $Z_{out}(j\omega)$.


(c) [5 pts] Find the transfer function $H(j\omega) = I_{out}(j\omega) / V_{in}(j\omega)$.

(d) [10 pts] Sketch the Bode plot of the transfer function $H(j\omega)$ for $C_1 = 100$ nF, $C_2 = 10$ μ F, $R_2 = 1$ k Ω , and $R_3 = 100$ k Ω . Be sure to label the axes and indicate the units (rad/s, dB Ω^{-1} , and degrees).


$H(j\omega)$ Magnitude

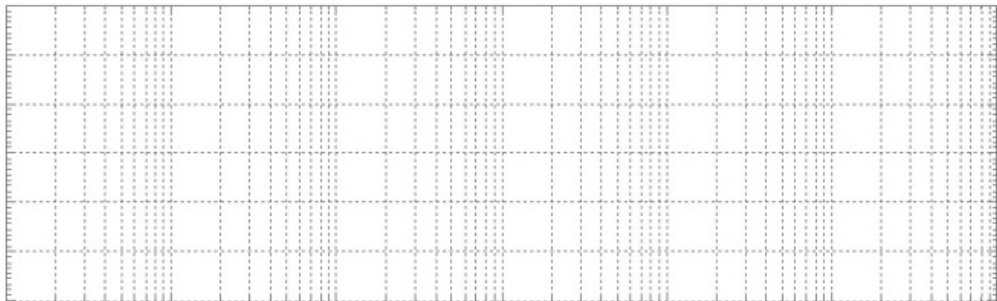

$H(j\omega)$ Phase

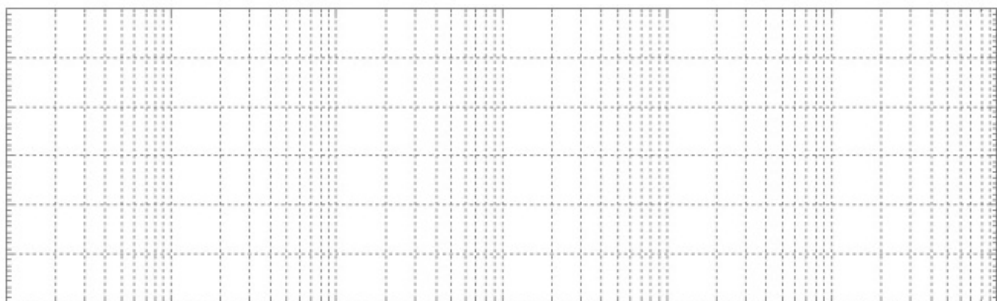

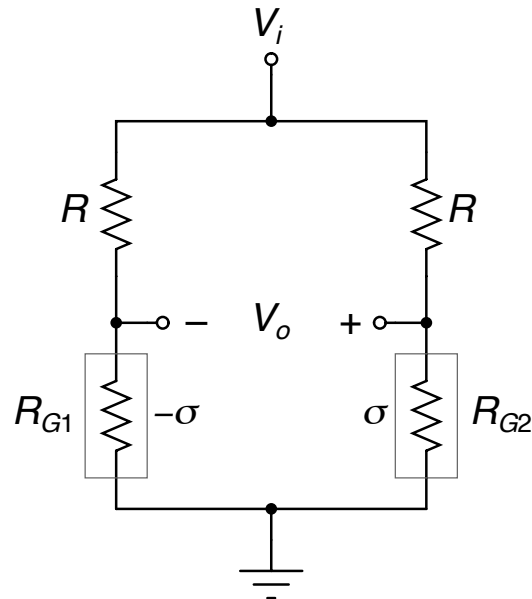4. **[30 pts]** Consider the stress transducer below, with constant supply voltage $V_i = 3 \text{ V}$, two constant resistors each with resistance $R = 100 \text{ k}\Omega$, and two strain gauges R_{G1} and R_{G2} with identical nominal resistance R_{nom} and gauge factor $G = -100$ that are differentially activated by complementary strain due to complementary stress σ and $-\sigma$ as shown. Both strain gauges have the same Young's modulus $E = 100 \text{ kPa}$.



$$\begin{aligned}
 R_{G1} &= R_{nom} (1 - G\epsilon) \\
 R_{G2} &= R_{nom} (1 + G\epsilon) \\
 \sigma &= E \epsilon
 \end{aligned}$$

- (a) [10 pts] Find the output voltage V_o as a function of stress σ .

(b) [10 pts] Find the value of R_{nom} that maximizes the sensitivity of the stress transducer, for low levels of stress $\sigma \approx 0$.

- (c) [10 pts] A 10-bit analog-to-digital converter (ADC) is used to digitize the voltage output V_o for a digital reading of stress σ . The full-scale voltage range of the ADC is from 1 V to 2 V. Find the accuracy of the stress reading for low levels of stress $\sigma \approx 0$.