

## 520.492 Mixed-Signal VLSI Systems


*Week 10*

### **Low Power Techniques**


#### **References**

1. Franca and Tsividis: Chapter 3.
2. C. Mead and L. Conway, *Introduction to VLSI Systems*, Addison-Wesley, 1980.
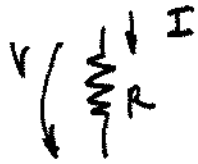
# ENERGY CONSUMPTION AND POWER DISSIPATION


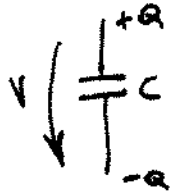
$$P_{\text{diss.}} = I \cdot V = R I^2 = \frac{V^2}{R}$$




$$\left\{ \begin{aligned} E_{\text{pot.}} &= \frac{C V^2}{2} = \frac{Q V}{2} = \frac{Q^2}{2C} && \text{ELECTROSTATIC ENERGY} \\ P_{\text{transient}} &= \frac{dE_{\text{pot.}}}{dt} = C V \frac{dV}{dt} = V \frac{dQ}{dt} = V \cdot I \end{aligned} \right.$$



$$\left\{ \begin{aligned} E_{\text{pot.}} &= \frac{L I^2}{2} = \frac{\Phi \cdot I}{2} = \frac{\Phi^2}{2L} && \text{MAGNETOSTATIC ENERGY} \\ P_{\text{transient}} &= \frac{dE_{\text{pot.}}}{dt} = L \cdot I \frac{dI}{dt} = V \cdot I \end{aligned} \right.$$

In general:

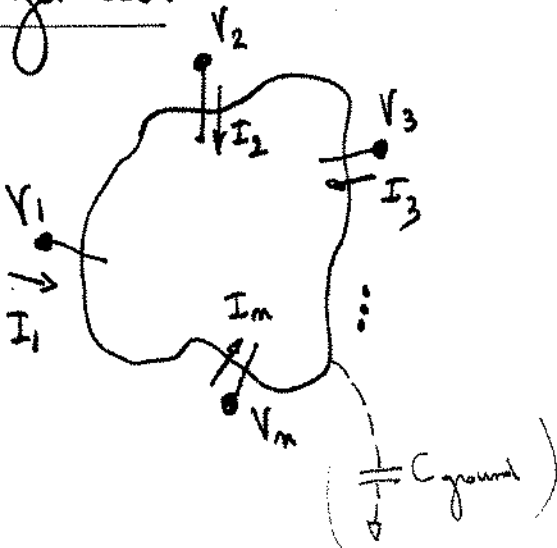

$$P_{\text{injected}} = \sum_{i=1}^m I_i V_i$$

$$= P_{\text{diss.}} + P_{\text{transient}}$$

$\downarrow$  resistive                       $\downarrow$  behind transient


$$\Rightarrow P_{\text{diss.}} = \langle P_{\text{injected}} \rangle = \left\langle \sum_{i=1}^m I_i V_i \right\rangle$$

$$\langle P_{\text{transient}} \rangle \equiv 0$$


$$n: \int_{\text{state 1}}^{\text{state 2}} P_{\text{transient}}(t) dt = 0$$

where state<sub>2</sub> and state<sub>1</sub> equal but different times

Current: DYNAMIC POWER DISSIPATION

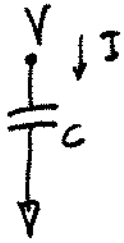
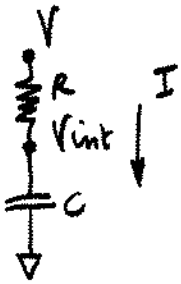
$$I = C \frac{dV}{dt} \Rightarrow P_{\text{injected}} = \frac{d}{dt} \left( \frac{C V^2}{2} \right) \Rightarrow P_{\text{diss.}} = \langle P_{\text{injected}} \rangle = \underline{\underline{0}}$$



$$I = C \frac{dV_{\text{int}}}{dt} \text{ and } V = V_{\text{int}} + R \cdot I$$

$$\Rightarrow P_{\text{injected}} = I \cdot V = R \cdot I^2 + \frac{d}{dt} \left( \frac{C V_{\text{int}}^2}{2} \right)$$

$$\Rightarrow P_{\text{diss.}} = \langle P_{\text{injected}} \rangle = \underline{\underline{R \cdot \langle I^2 \rangle \neq 0}}$$

Fourier domain:  $I = j\omega C V_{\text{int}} = j\omega C (V - R I)$

$$\Rightarrow I(\omega) = \frac{j\omega C}{1 + j\omega z} V(\omega) \text{ with } z = RC$$

Parseval:  $\langle I^2 \rangle = \frac{1}{2} \int_{-\infty}^{+\infty} |I(\omega)|^2 d\omega$  (Wiener-Khinchine special case)

$$\Rightarrow P_{\text{diss.}} = R \cdot \frac{1}{2} \int_{-\infty}^{+\infty} \frac{C^2 \omega^2}{1 + z^2 \omega^2} |V(\omega)|^2 d\omega$$

$$= C \cdot \frac{1}{2} \cdot \left( \frac{1}{z} \int_{-\infty}^{+\infty} \frac{\omega'^2}{1 + \omega'^2} \cdot |V(\omega')|^2 d\omega' \right)$$


change of variable  
 $\omega' = z \cdot \omega$   
 normalized frequency

depends on RELATIVE  
 FREQUENCY CONTENT  
 of V signal

example 1:

1:

V = harmonic

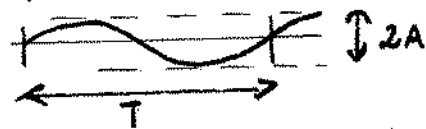

$$V(\omega) = A \cdot \delta\left(2\pi \frac{\omega}{T}\right)$$

↙ amplitude

$$\Rightarrow P_{\text{diss.}} = C \cdot \frac{1}{Z} \cdot \frac{\omega^2}{1 + \omega^2} \cdot \underbrace{\frac{1}{2} A^2}_{V_{\text{rms}}^2}$$


$$T \gg \tau \Rightarrow P_{\text{diss.}} \approx C V_{\text{rms}}^2 \cdot \frac{4\pi^2 \tau}{T^2}$$

$$\propto \boxed{C V_{\text{pp}}^2 \cdot \underline{f^2}}$$


example 2:

2:

V = square wave

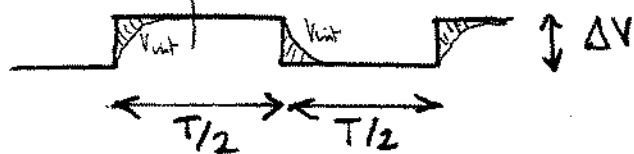
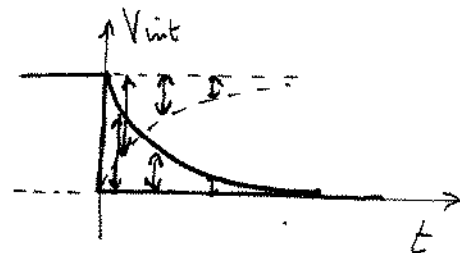
$$I = \frac{V - V_{\text{int}}}{R} = \pm \frac{1}{R} \Delta V \cdot e^{-\frac{t}{\tau}}$$





$$P = \langle RI^2 \rangle = \frac{2}{T} \frac{1}{R} \Delta V^2 \int_0^{\tau/2} e^{-\frac{2t}{\tau}} dt = \frac{2}{T} \frac{1}{R} \Delta V^2 \frac{RC}{2} = C \Delta V^2 \cdot \frac{1}{T}$$

$$\propto \boxed{C V_{\text{pp}}^2 \cdot \underline{f}}$$



(Why the difference?)

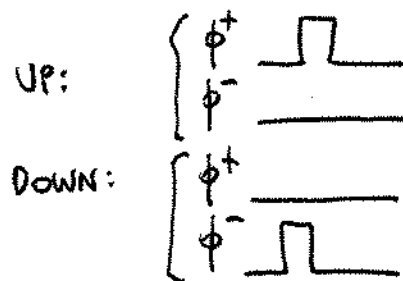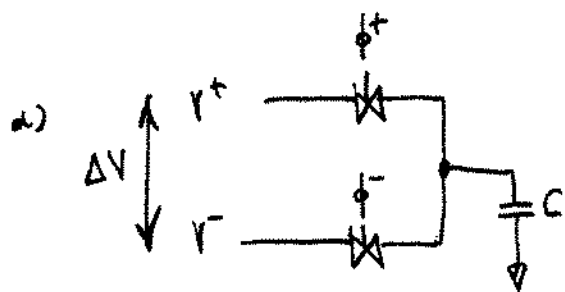example 3: cyclic charging of a large load capacitance:



Dissipated energy per UP or DOWN charging:
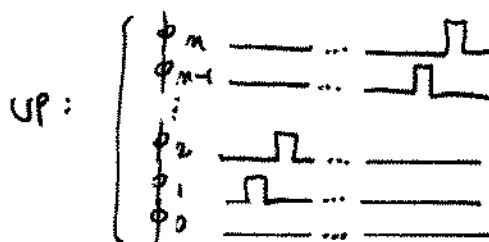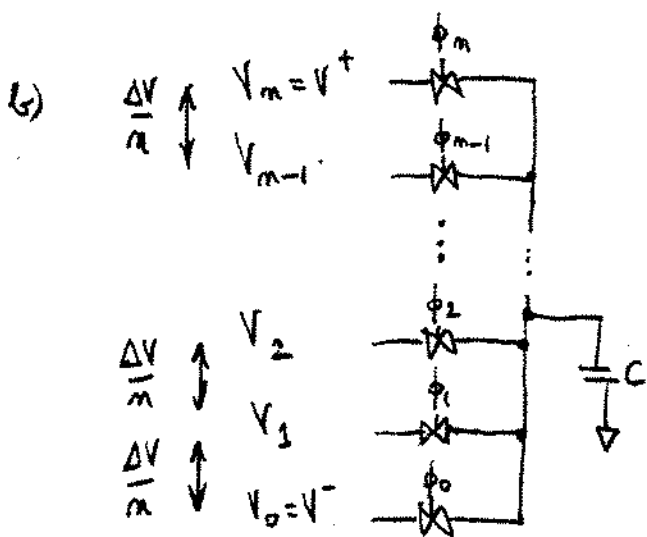
$$P_{\text{diss}}^{\text{UP}} = P_{\text{diss}}^{\text{DOWN}} = \frac{1}{2} C (V^+ - V^-)^2 = \frac{1}{2} C \Delta V^2$$




Dissipated energy per complete UP or DOWN charging:

$$P_{\text{diss}}^{\text{UP}} = P_{\text{diss}}^{\text{DOWN}} = \sum_{i=1}^m \frac{1}{2} C (V_i - V_{i-1})^2 = m \frac{1}{2} C \left(\frac{\Delta V}{m}\right)^2 = \frac{1}{2m} C \Delta V^2$$

which is supplied by  $V_m (V^+)$  and  $V_0 (V^-)$  only, on average.

# LOW POWER TECHNIQUES FOR DIGITAL CMOS

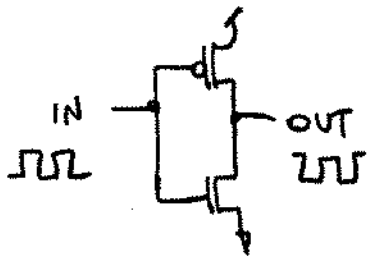

$$P_{diss.} = P_{static} + P_{transient}$$


LEAKAGE

junctions + bulk current  
leakage MOS

DYNAMIC + SHOOT-THROUGH

- $P_{static} = I_{leak} \cdot V_{dd}$


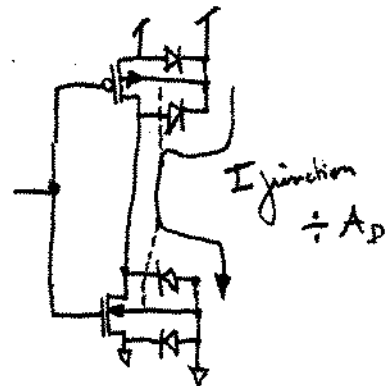
with  $I_{leak} = I_{junction} + I_{bulkcurrent}$



$$I_{bulkcurrent} \approx I_0 \cdot e^{-\frac{V_{th}}{V_T}}$$

- $P_{transient} = 2 \alpha f \cdot (E_{shoot-thru} + E_{dyn.})$

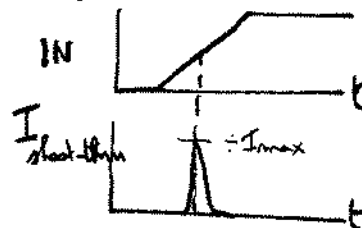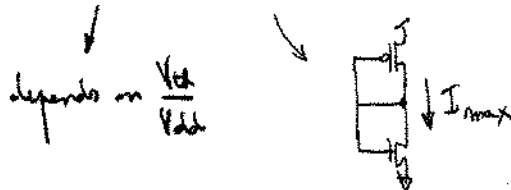with  $E_{shoot-thru} \approx I_{max} \cdot V_{dd} \cdot t_{rise}$



and  $E_{dyn} = \frac{1}{2} C V^2$


and  $\alpha =$  activity (average # of transitions per rising or falling clock edge)

and  $f =$  clock frequency



# Decentralization of the computational task

## PARALLEL (DISTRIBUTED) COMPUTING :

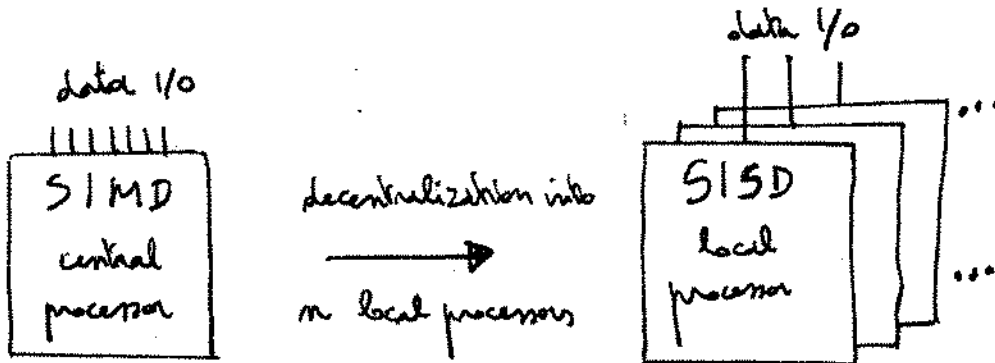

$\alpha f$   
 $V_{dd}$   
 $V_{th}$

$\alpha f/m$   
 $V_{dd}/m$   
 $V_{th}/m$

$$\tau_{prop} \propto \frac{V_{dd}}{(kV_{dd} - V_{th})^2}$$

$$P_{dyn} = \alpha f C V_{dd}^2 \quad \rightarrow \quad P_{dyn} = m \times \frac{\alpha f}{m} C \left(\frac{V_{dd}}{m}\right)^2$$

$$= \frac{\alpha f C V_{dd}^2}{m^2}$$

$$area = A \quad \rightarrow \quad area = A \times m$$

### limits: STATIC POWER DISSIPATION :

$$P_{stat} = (I_{junction} + I_0 e^{-\frac{V_{th}}{V_T}}) V_{dd} \quad \rightarrow \quad P_{stat} = \alpha (I_{junction} + I_0 e^{-\frac{V_{th}}{mV_T}}) \frac{V_{dd}}{m}$$

$e^{-\frac{V_{th}}{mV_T}} \uparrow \uparrow$




# Substrate modulation for external adjustment of $V_{th}$ :

(Stanford Ultra Low Power CMOS)

$V_{th}$  is not adjustable after fabrication, but can effectively be modulated through the body effect, by the  $V_{bulk}$  voltage:

$$V_g \text{ --- } \downarrow I \quad I = f(kV_g - V_{th}) \quad \rightarrow \quad V_g \text{ --- } \downarrow I \quad I = f(kV_g + \underbrace{(1-k)V_{bulk}}_{-V_{th}^{eff}} - V_{th})$$
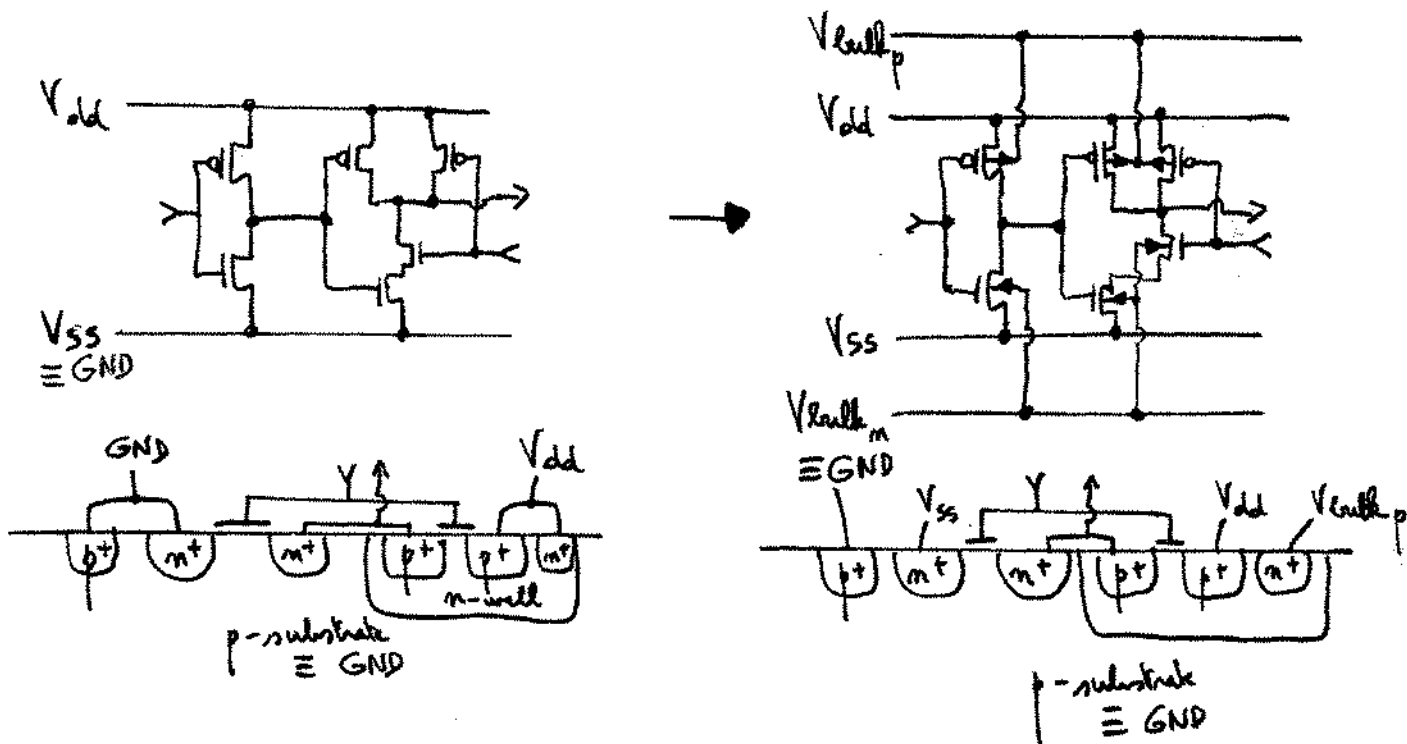
$$\Rightarrow \underline{V_{th}^{eff} = V_{th} - (1-k)V_{bulk}}$$




NOTE: •  $V_{bulk\_p} > V_{dd}$  and  $V_{bulk\_m} < V_{ss}$ , but

$V_{bulk\_m}$  and  $V_{bulk\_p}$  dissipate little dynamic power (no)

•  $V_{bulk\_m} \equiv GND$  identical for all gates  $\Rightarrow$  local adjustment is not possible, unless in a twin-tub process.


# LOW-POWER TECHNIQUES FOR ANALOG CMOS

Basic function of MOS transistor:

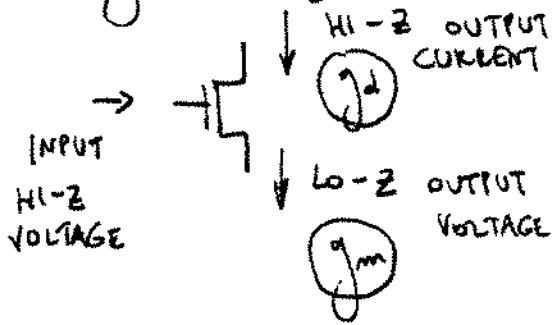

- TRANSCONDUCTANCE ( $g_m$ )
- VOLTAGE GAIN ( $A_v = \frac{g_m}{g_d}$ )

example: follower

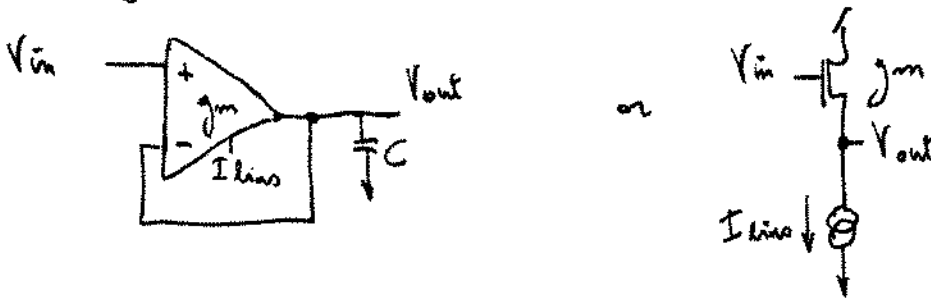

$$I_{out} = g_m (V_{in} - V_{out}) - g_d V_{out} = C \frac{dV_{out}}{dt}$$

time constant :  $\tau = C / (g_m + g_d) \approx C / g_m$

power :  $P = I_{bias} \cdot V_{dd}$

power-delay product : (typical)

$$P \cdot \tau = \frac{I_{bias}}{g_m} \cdot C V_{dd}$$

⇒ • increase  $\frac{g_m}{I_{bias}}$

• decrease  $V_{dd}$  and  $C$

1) lower  $C$  and  $V_{dd}$


limit:  $SNR : \frac{range}{SNR} \gg \sqrt{\frac{kT}{C}}$  and  $V_{dd} \gg range$   
 ↑  
 how much depends on circuit techniques

2) increase  $g_m / I$  : relative transconductance (units  $V^{-1}$ )




• operational:

sub-threshold:  $I \approx I_0 e^{kV_g/V_T} \Rightarrow g_m = I_0 \frac{k}{V_T} e^{kV_g/V_T} \Rightarrow \frac{g_m}{I} = \frac{k}{V_T}$

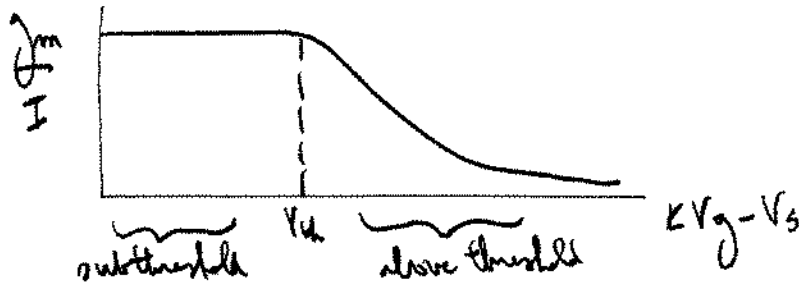above threshold:  $I \approx \frac{\beta}{2} (kV_g - V_s - V_{th})^2 \Rightarrow g_m = \beta k (kV_g - V_s - V_{th}) \Rightarrow \frac{g_m}{I} = \frac{k}{kV_g - V_s - V_{th}}$



• topological:

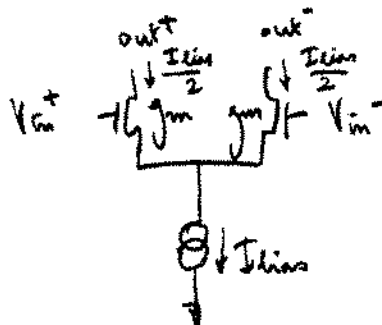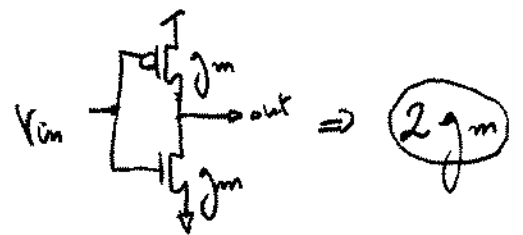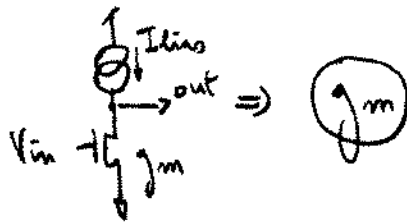


$\Rightarrow \frac{1}{2} g_m$

# Low-voltage techniques

( a few of them )

- low-voltage cascode:

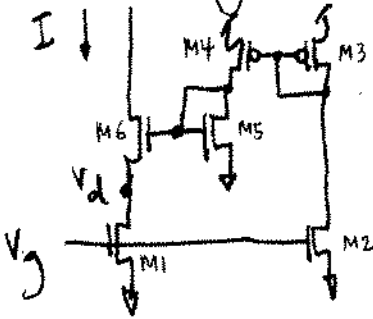


$$V_d = V_T \log \left( \frac{M_2 \cdot M_4 \cdot M_6}{M_1 \cdot M_3 \cdot M_5} \right)$$

$> 5 V_T$  for saturation of M1


$$\Rightarrow \frac{M_2 M_4 M_6}{M_1 M_3 M_5} \approx 100$$

- low-voltage differential ramp:



→ Combine n- and p-type diff pairs:

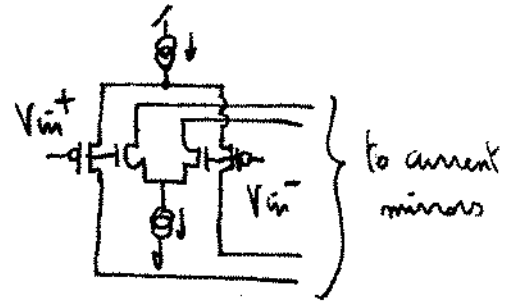

→ OR: dynamic:



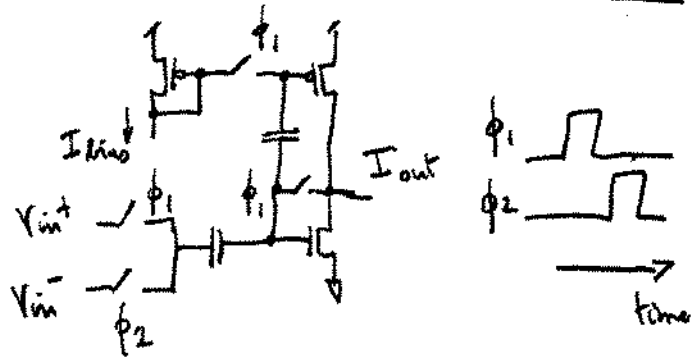


- low-voltage active switch:

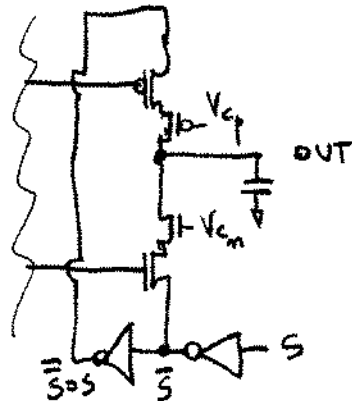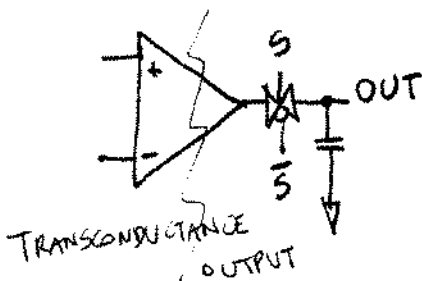
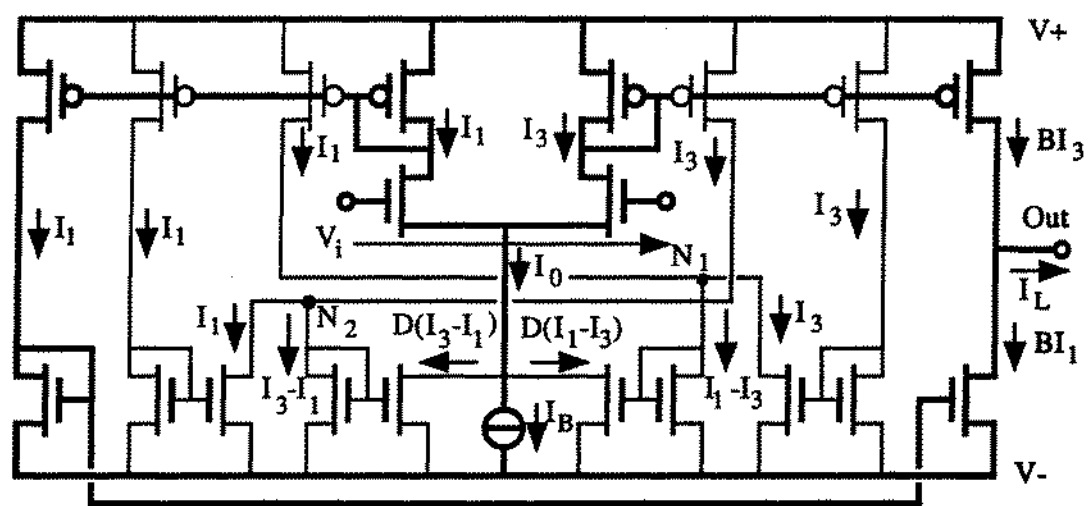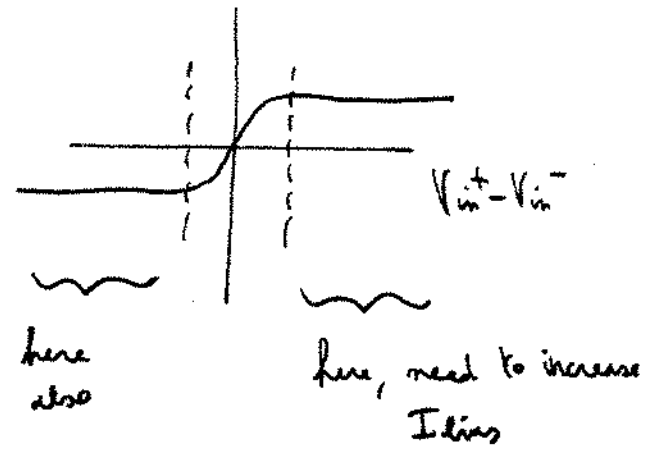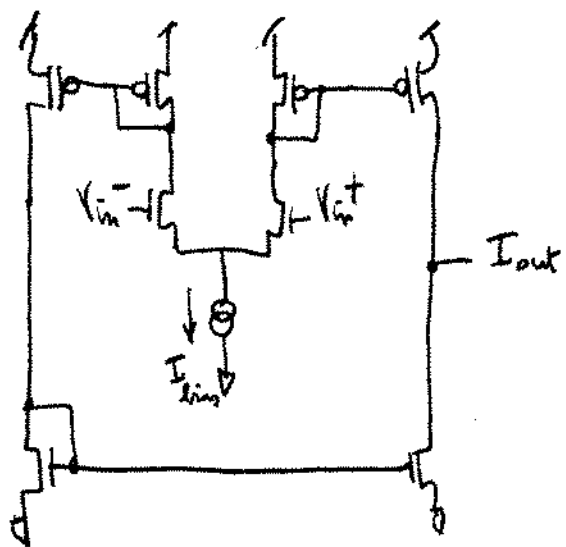
# DYNAMIC BIASING TECHNIQUE :

adjust  $I_{bias}$  to the needs of the load



$$-I_L = B (I_1 - I_3) = BI_B \frac{\tanh(V_i / 2nU_T)}{1 - D |\tanh(V_i / 2nU_T)|}$$

