

520.492 Mixed-Signal VLSI Systems

Week 11

Analog Dynamic Techniques

References



1. Franca and Tsividis: Chapter 4.
2. R. Gregorian and G.C. Temes, *Analog MOS Integrated Circuits for Signal Processing*, Wiley, 1986.

DYNAMIC ANALOG TECHNIQUES

ref: Franca and Tsividis, Chapter 4
(E.A. Vittoz)

- Sampling: $X(t) \rightarrow X_k = X(t_0 + k \cdot T)$

typical:

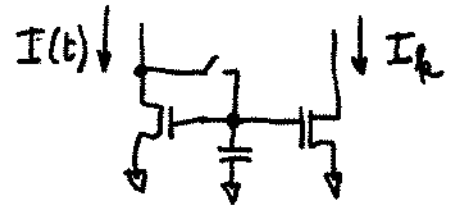
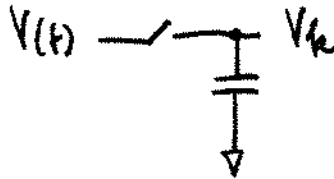


applications:

short-term analog memory ("register")

- Auto-Zeroing: $X(t) \rightarrow X(t) - X_k$

typical:

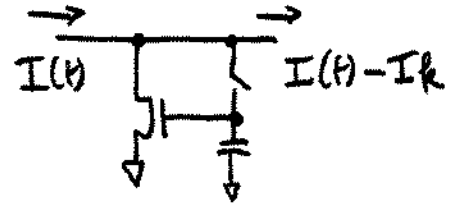
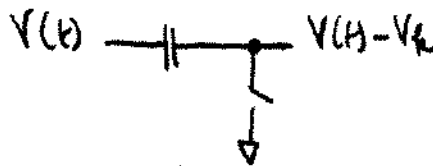


applications:

cancellation of DC noise and offsets
(1/f noise; MOS mismatch; supply...)

- Finite-State Automata: $X_{k-1} \rightarrow X_k = F(X_{k-1}; Y_k)$




typical:

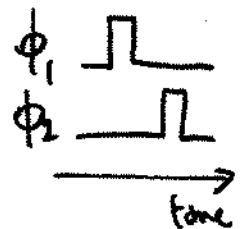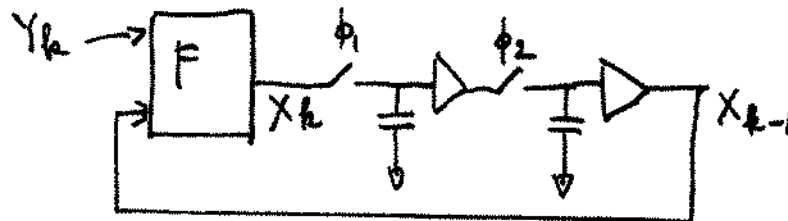

examples:

- discrete-time filters
- algorithmic D/A and A/D converters
- delta-sigma modulators
- etc...

SWITCH CHARGE INJECTION

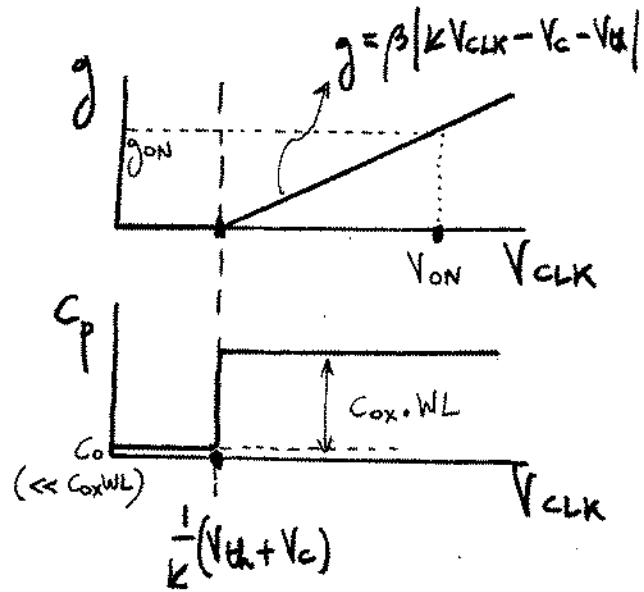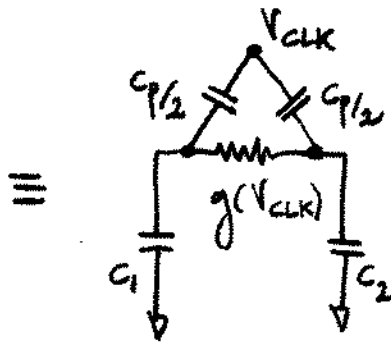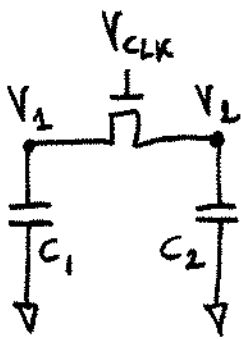

ON
↓
OFF

a) $V_{CLK} = V_{ON} > \frac{1}{2}(V_{th} + V_c)$ and $V_1 = V_2 \equiv V_c$

b) $V_{CLK} \downarrow \Rightarrow \frac{1}{2} C_p \cdot \frac{dV_{CLK}}{dt}$ current injected in C_1 and C_2


c) $V_{CLK} = V_{off} < \frac{1}{2}(V_{th} + V_c)$

$$\Rightarrow \begin{cases} V_1 = V_c + \Delta V_1 \\ V_2 = V_c + \Delta V_2 \end{cases}$$

and $C_1 \Delta V_1 + C_2 \Delta V_2 = \Delta Q_s$
 with $\Delta Q_s = -C_p [V_{ON} - \frac{1}{2}(V_{th} + V_c)]$
 (shared among C_1 and C_2)


- $C_1 = C_2 \Rightarrow C_1 \Delta V_1 = C_2 \Delta V_2$ symmetrical charge injection
- $C_1 \neq C_2 \Rightarrow \begin{cases} C_1 \Delta V_1 \approx C_2 \Delta V_2 \text{ for } \left| \frac{d}{dt} V_{CLK} \right| > 10 \frac{g_{on}}{\min(C_1, C_2)} \\ \Delta V_1 \approx \Delta V_2 \text{ for } \left| \frac{d}{dt} V_{CLK} \right| \ll \frac{g_{on}}{\max(C_1, C_2)} \end{cases}$

Typical situation:

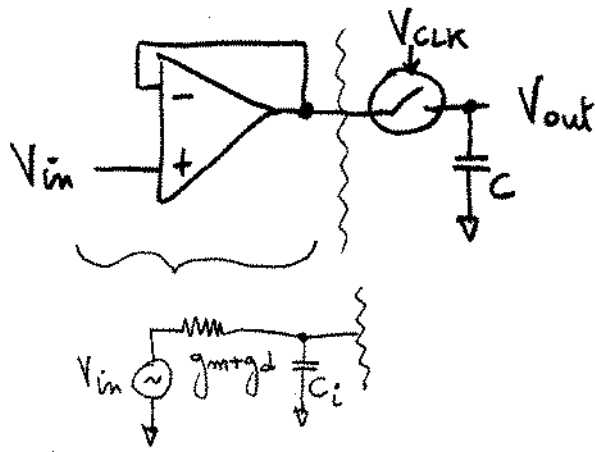


remedy:

①

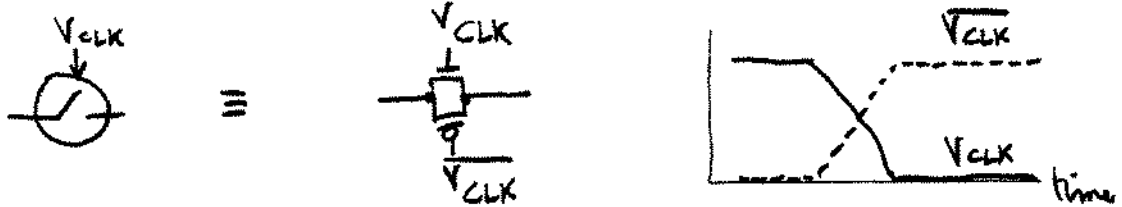


only works partially, since $|V_{on} - \frac{1}{2}(V_{th} + V_c)|$ is different for both

②

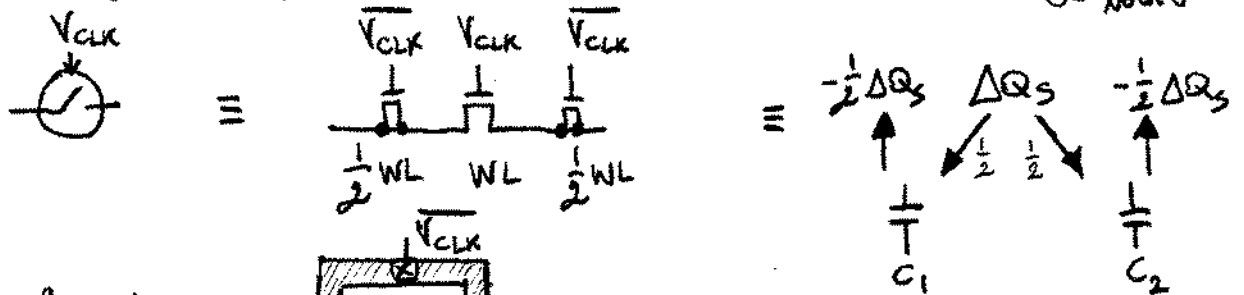


layout:

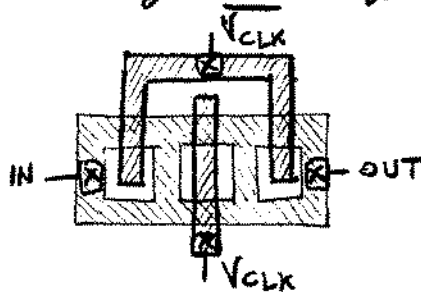

works fine as long as $|\frac{d}{dt} V_{CLK}| > 10 \cdot g_{on} / \min(C, C_i)$

③ = ① + ② works better than ②, also because $g_{on} = \text{higher}$


④

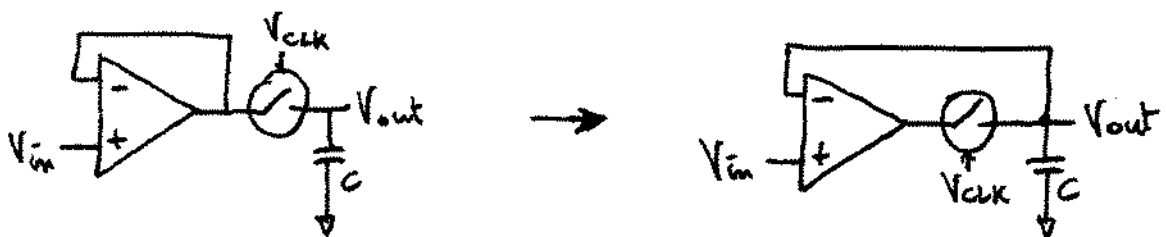

works satisfactorily only for $|\frac{d}{dt} V_{CLK}| \ll \frac{\min(g_{on}, g_{m+gd})}{\max(C, C_i)}$ and without ② or ③

DYNAMIC AUTO-ZEROING TECHNIQUES



→ offset and drift cancellation

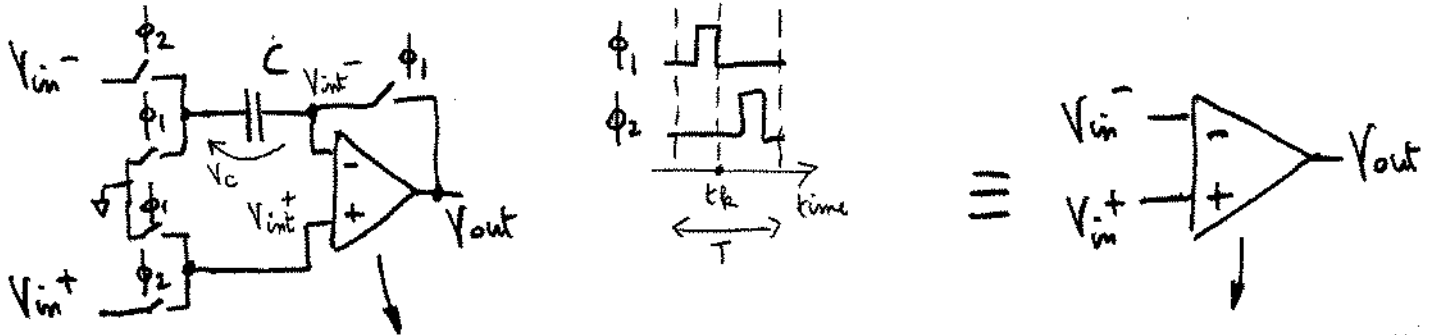

$$V_{out} = A (V_{int+} - V_{int-} - V_{off}(t)) \rightarrow V_{out} = A (V_{in+} - V_{in-} - \underline{\underline{V_{off}^{eff}(t)}})$$

• ϕ_1 : auto-zero: $V_{int-} \equiv V_{out}$
 $V_{int+} \equiv 0 \Rightarrow V_{out_k} = V_{c_k} = -\frac{A}{A+1} V_{off_k}$
 (sampled @ $t_k = t_0 + kT$)

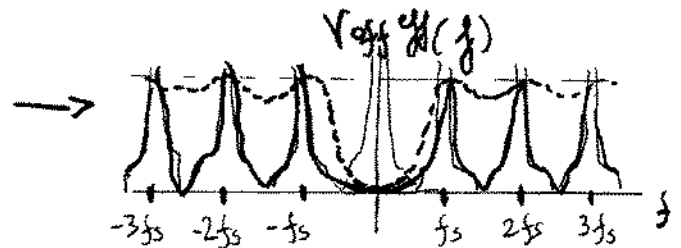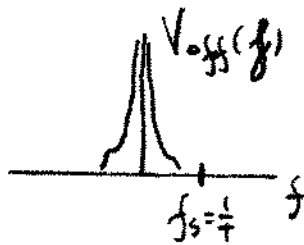• ϕ_2 : amplify: $V_{out} = A (V_{in+} - (V_{in-} - \frac{A}{A+1} V_{off_k}) + V_{off}(t))$
 $A \rightarrow \infty \Rightarrow V_{out} \approx A (V_{in+} - V_{in-} - \underbrace{(V_{off}(t) - V_{off_k})}_{V_{off}^{eff}(t)})$



⇒ Low-frequency components of $V_{off}(f)$ are virtually eliminated:


- offsets
- $1/f$ noise
- power supply variations
- etc...

except: \neq switch charge injection


Improvements:

Reduce switch charge injection

① Balanced input:

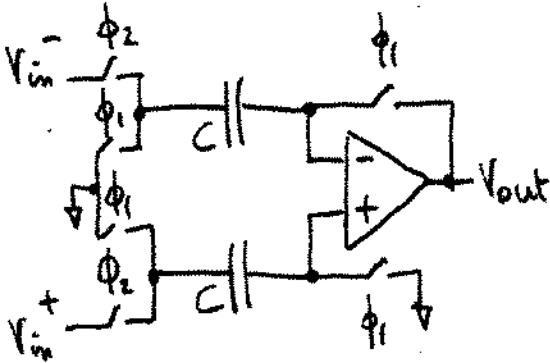


OR:

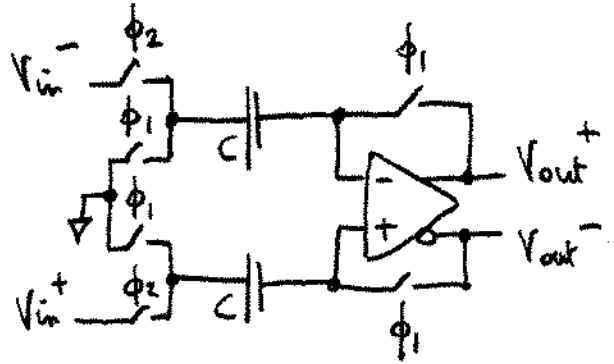

also reduces effect of parasitic C at the amplifier input node

② Weak secondary input:

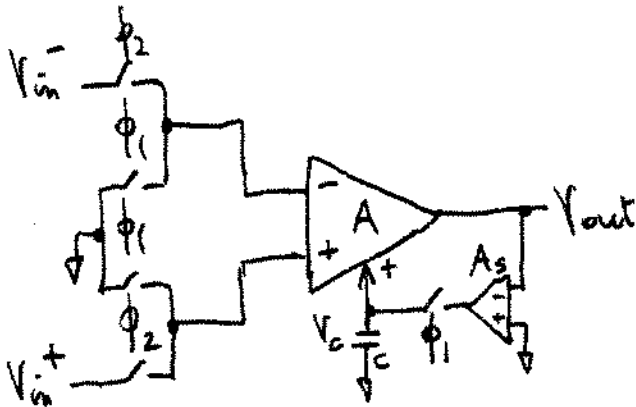

$$V_{out} = A(V_{in}^+ - V_{in}^- - V_{off}) + A_s V_c$$

- ϕ_1 : $V_{in}^+ - V_{in}^- \equiv 0$; $V_{out} = 0$
 $\Rightarrow V_{c_k} = -\frac{A}{A_s} V_{off_k} + \underbrace{C \Delta Q_s}_{\text{CHARGE INJECTION}}$

- ϕ_2 : $V_{out} = A(V_{in}^+ - V_{in}^- - V_{off}^{eff}(t))$

$$\Rightarrow V_{off}^{eff}(t) = (V_{off}(t) - V_{off_k}) - \frac{A_s}{A} C \Delta Q_s$$


$V_{off}^{eff}(t)$
w/o switch
injection

CHARGE INJECTION
SCALED BY A_s/A



charge injection is optimally reduced for $A_s \ll A$

DYNAMIC SAMPLING TECHNIQUES



a) Voltage-mode S/H

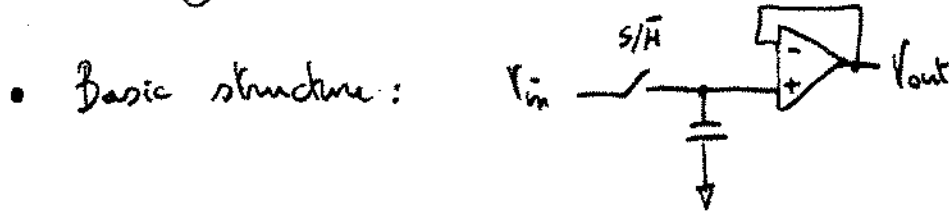

- Offset-compensated S/H:

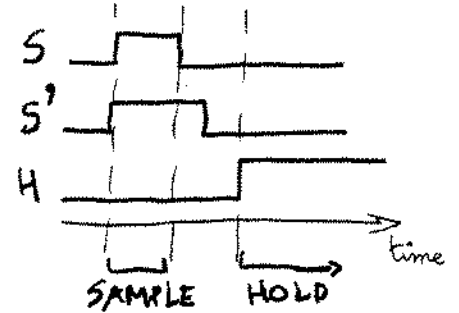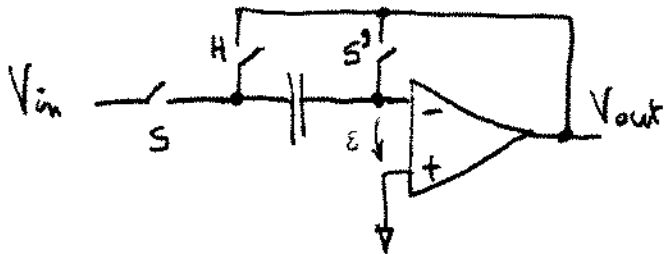

- Leakage-reduced S/H:

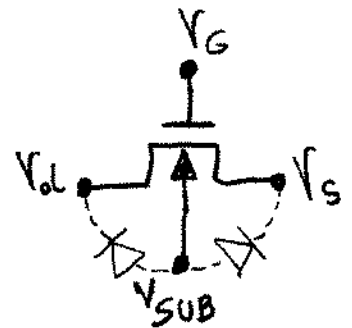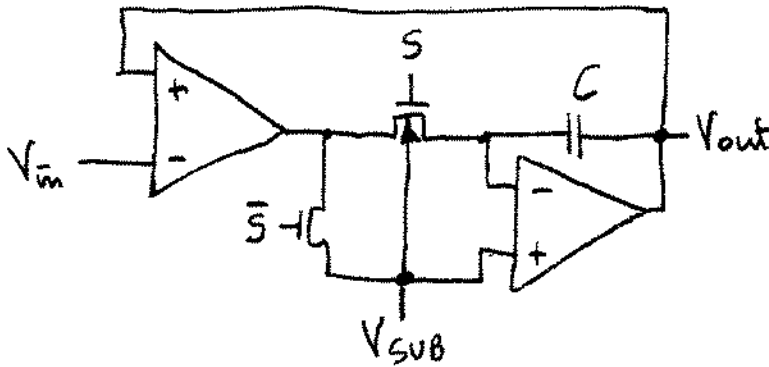



$$V_d, V_s \equiv V_{SUB} \Rightarrow I_s \approx 0$$

(diode leakage)

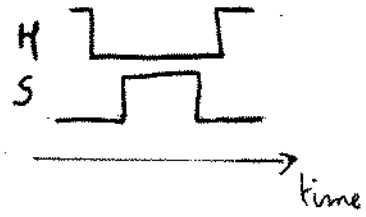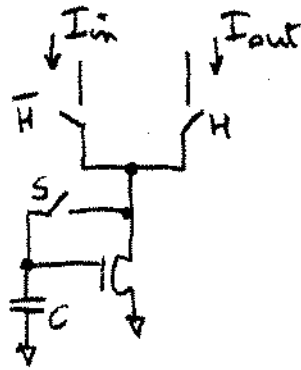b) Current-mode S/H


- Basic structure:

$$\left(\text{---} \equiv \frac{1}{s} \right)$$




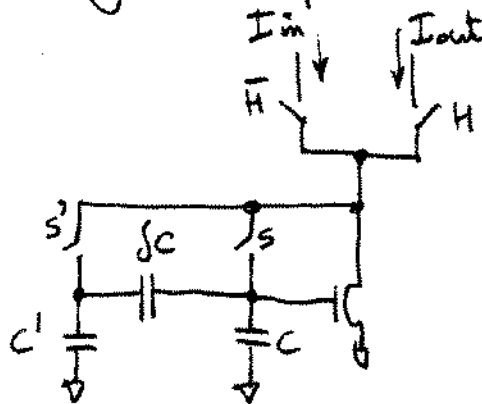- problems:
- charge injection is amplified by g_m
 - output is not available in sample mode

- Switch injection compensation by low-sensitivity auxiliary input:



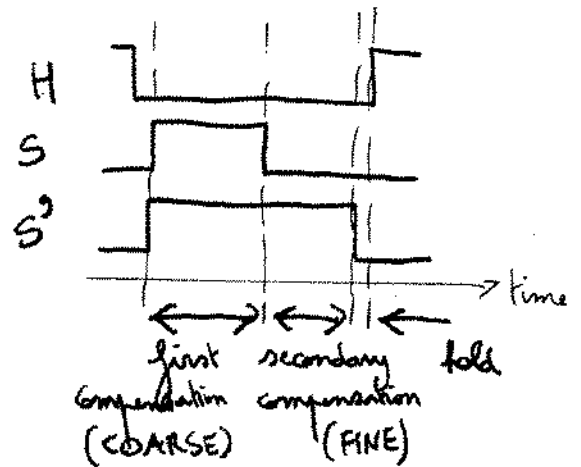$C_c \ll C, C' \Rightarrow$ more effective



- Uninterrupted output:

