520.492 Mixed-Signal VLSI Systems

Week 9

Structured and Testable Design

References

- 1. Geiger, Allen and Strader: Chapters 6 and 7.
- 2. C. Mead and L. Conway, *Introduction to VLSI Systems*, Chapter 9, Allison-Wesley, 1980.

· STRUCTURED DESIGN


objective : to reduce the global amount of effort involved in the design and longest, and to allow for direct extension and alteration


- · HIERARCHY
- . REGULARITY
- · MODULARITY
- · LOCALITY


(Design for testubility) • TESTABLE DESIGN objective: to reduce the burden of exhaustively testing the fubricated VLSI circuit for structural faults and other non-idealities

- · OBSERVABILITY
- · CONTROLLABILITY


STRUCTURED DESIGN

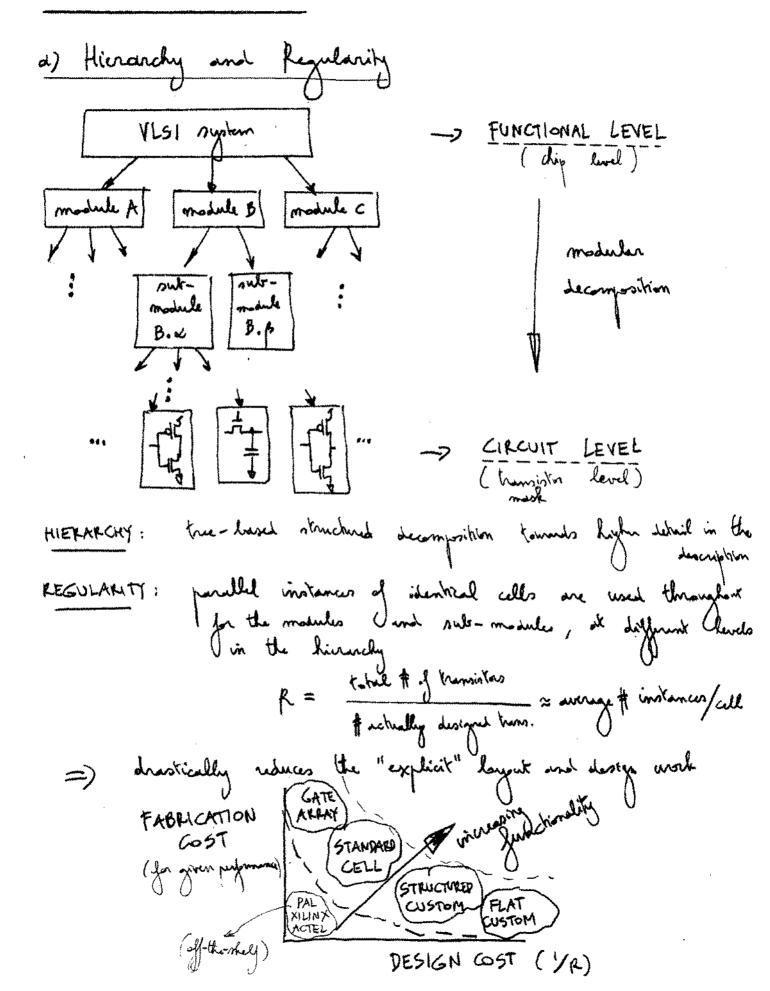

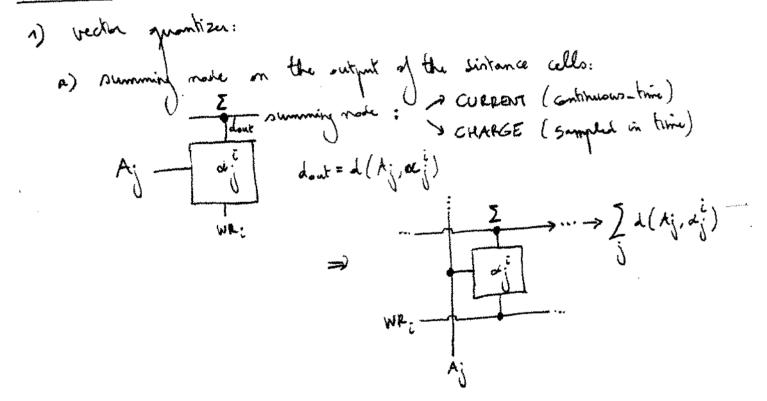

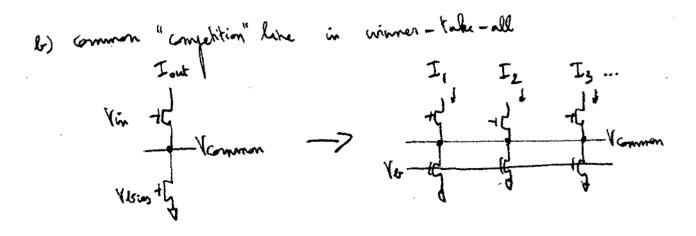

EXAMPLES (Continued):

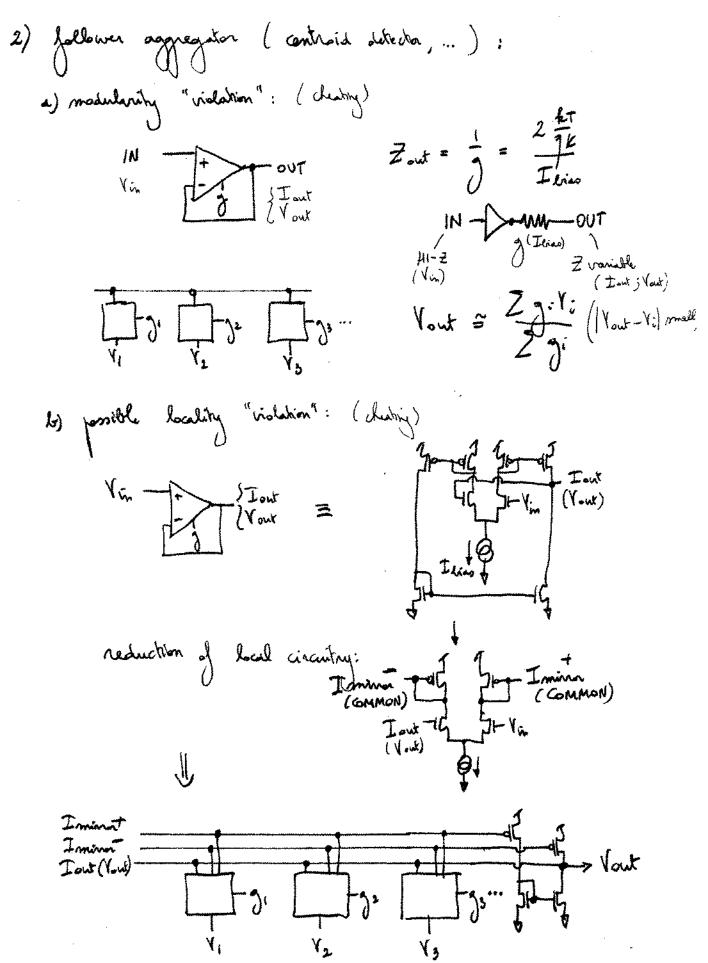



DESIGN FOR TESTABILITY

CONTROLLABLE

ASSUMES A GIVEN MODEL FOR CORRECT OPERATION

•BERVABLE

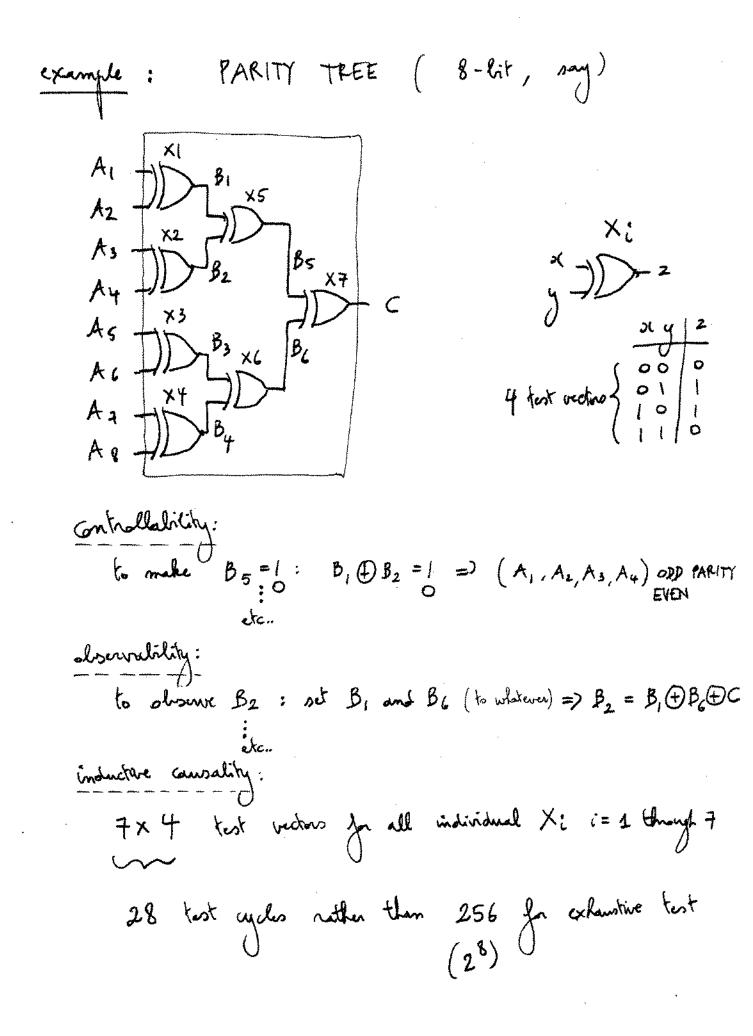

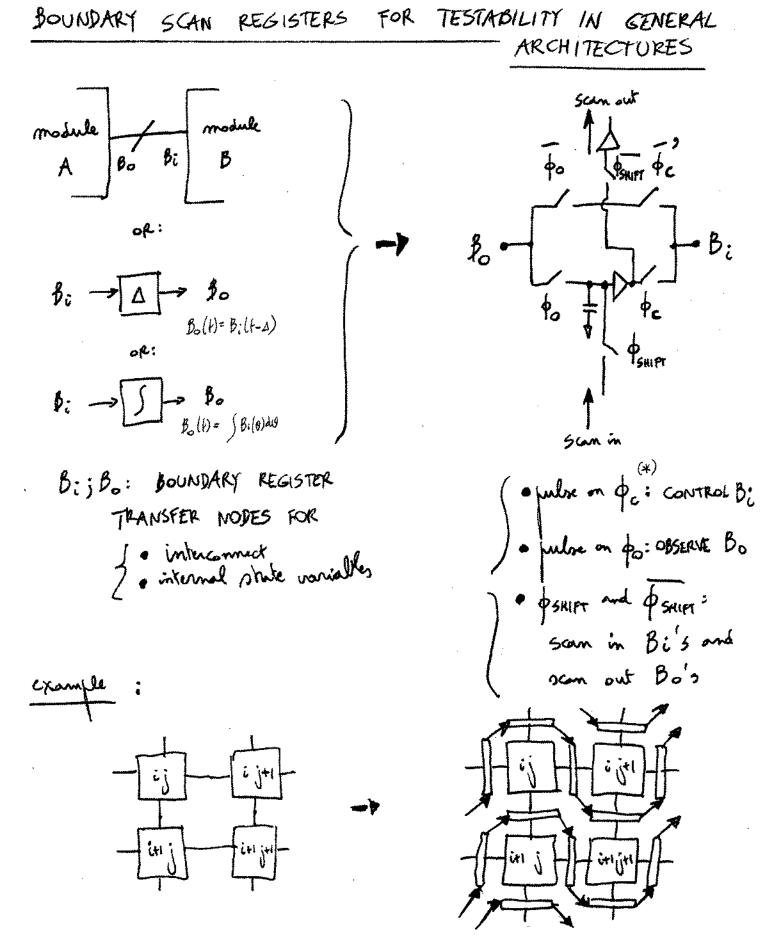

(*) and then retain $\overline{\phi_{c}}^{2}$ Low

RANDOM-ACCESS TESTABILITY

