

Lecture 12

Biopotential Amplifiers: Problems and Solutions

References

Webster, Ch. 6 (Sec. 6.3-6.6).

Common-mode and interference reduction

Ch. 6

- Interference : unwanted signals, present with the wanted signals, and considered as "noise"

The goal in good bioinstrumentation design is to maximize the SIGNAL-TO-NOISE RATIO (SNR) :

$$SNR = \frac{S}{N} = \frac{\text{Signal power}}{\text{noise power}} \quad (\text{at the output})$$

Expressed in decibels (dB) :

$$SNR (dB) = 10 \log_{10} \frac{S}{N} = 20 \log_{10} \frac{\text{signal amplitude}}{\text{noise amplitude}}$$

because: power is proportional to the square amplitude (magnitude)

Example: ECG signal = 1 mV pp (peak-to-peak amplitude)
electrode noise = 1 μ V pp


$$\Rightarrow SNR = 20 \log_{10} 1,000 = 60 \text{ dB} \quad (\text{pretty good})$$

Note: can express amplitude in pp (peak-to-peak) or rms (root mean square), but be consistent with signal & noise.

- Common-mode rejection :

Most sources of interference are COMMON-MODE: they appear with equal strength at all terminals of the instrument.

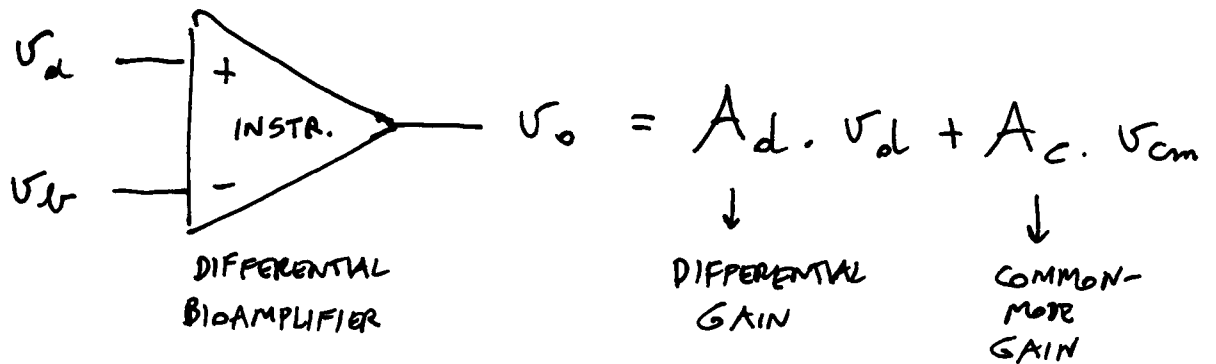A good instrument design is DIFFERENTIAL and eliminates the common-mode component by subtraction.



where $V_d = V_a - V_b$: DIFFERENTIAL signal of interest

$V_{cm} = \frac{V_a + V_b}{2}$: COMMON-MODE component NOT of interest
(drift, noise)

Common-mode rejection ratio: $CMRR = |A_d|/|A_c|$

Expressed in dB: $CMRR_{(dB)} = 20 \log_{10} (|A_d|/|A_c|)$
 $= A_d (dB) - A_c (dB)$

Typically would like $CMRR (dB) \geq 80 dB$


(OK for most differential amplifiers)

Good CMRR is critical for attaining a reasonable SNR when amplifying a weak differential signal, such as ECG, subject to substantial common-mode noise, such as 60 Hz line noise:

- Still heart in floating (or incompletely grounded) body:




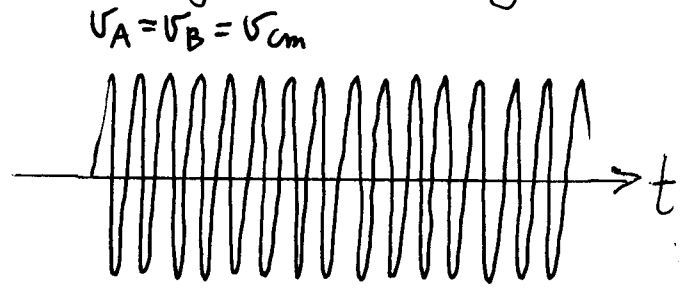All electrodes pick up the same common-mode voltage V_{cm} due to the body's high volume conduction




Typical 60 Hz line noise as common-mode voltage

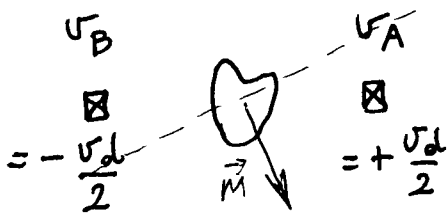- Active heart in perfectly grounded body:



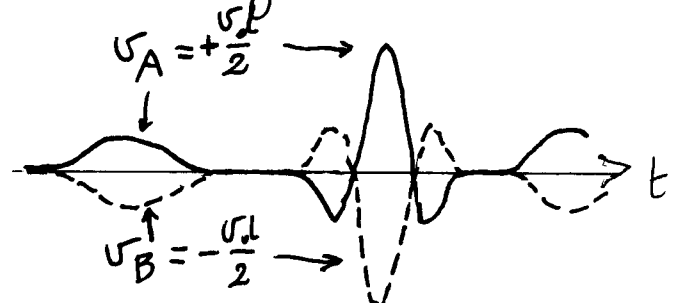Electrodes pick up ECG leads differentially, relative to the body ground at same potential as the instrument ground.




(NOTE: V_A and V_B are not necessarily complementary, but the average of all (RA, LA, LL) electrodes is zero here.)

- Active heart in actual (incompletely grounded) body: SUPERPOSITION



low SNR!


(typically $\ll 1$, or $SNR_{(dB)} < 0$)

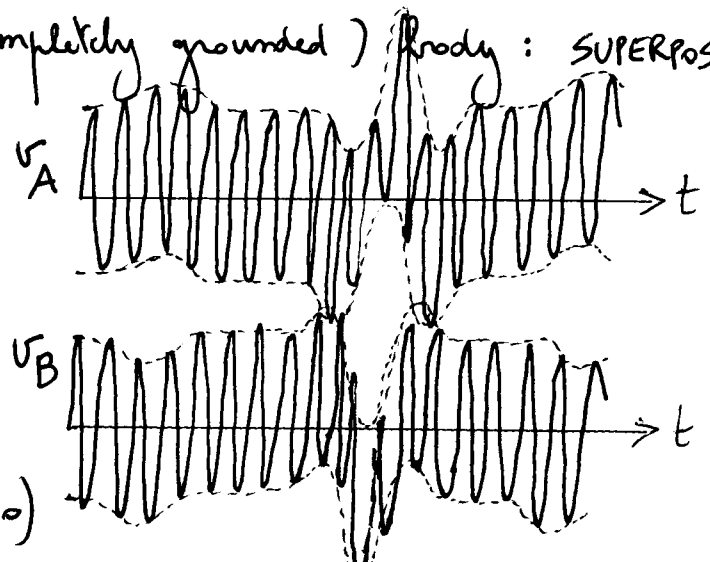

- Effect of differential amplification with high CMRR:



$$v_A = v_{cm} + \frac{v_d}{2}$$

$$v_B = v_{cm} - \frac{v_d}{2}$$

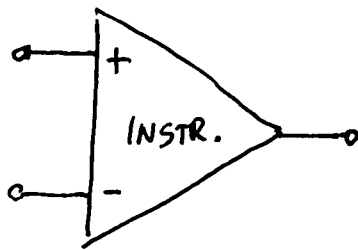

$$v_o = A_d v_d + A_c v_{cm}$$

$$CMRR = \left| \frac{A_d}{A_c} \right| \gg 1$$

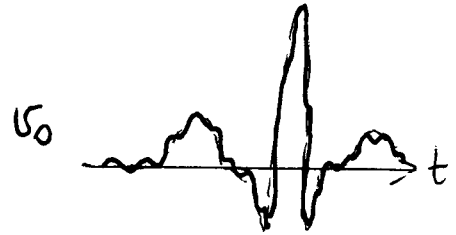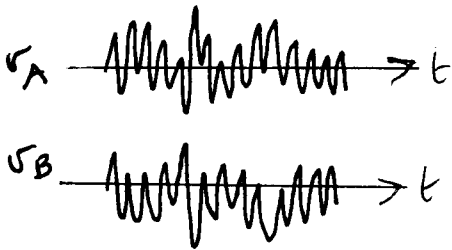

$$SNR_{in} = \frac{|\frac{1}{2} v_d|}{|v_{cm}|}$$

(either v_A or v_B)

$$SNR_{out} = \frac{|A_d \cdot v_d|}{|A_c \cdot v_{cm}|}$$

$\underbrace{\quad\quad\quad}_{CMRR} \quad \underbrace{\quad\quad\quad}_{2 SNR_{in}}$

$$\Rightarrow SNR_{out} = 2 \cdot CMRR \cdot SNR_{in}$$

$$\text{or } SNR_{out} (dB) = 6 dB + CMRR (dB) + SNR_{in} (dB)$$

\Rightarrow CMRR helps boost the SNR directly!

Example: $v_{cm} = 100 \text{ mV}_{pp}$ typically observed (without active grounding)


$v_d = 1 \text{ mV}_{pp}$ typical lead II ECG

$$\rightarrow SNR_{in} = -46 \text{ dB} \quad !!$$

\Rightarrow Need $CMRR \geq 80 \text{ dB}$ to obtain $SNR_{out} \geq 40 \text{ dB}$
(the least useful)

How to build an amplifier with high CMRR?

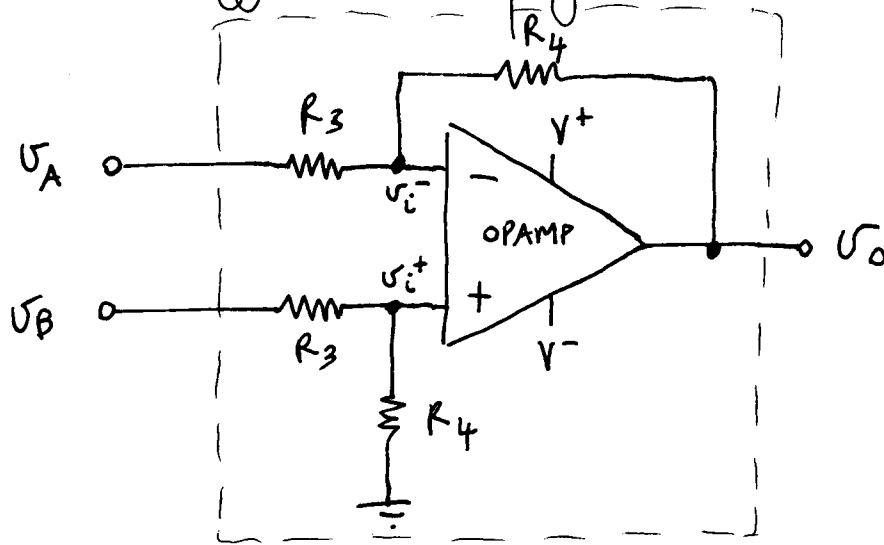TRIAL 1: Differential amplifier (Sec. 3.4)



(NOTE: Can make the output trivially NON-INVERTING by swapping the V_A and V_B inputs.)


$$\text{KCL@ } v_i^- : \frac{V_A - v_i^-}{R_3} = \frac{v_i^- - V_O}{R_4}$$

$$\text{KCL@ } v_i^+ : \frac{V_B - v_i^+}{R_3} = \frac{v_i^+ - 0}{R_4}$$

and $v_i^- = v_i^+$
IDEAL OPAMP


$$\Rightarrow V_O = -\frac{R_4}{R_3} (V_A - V_B), \text{ or } \left. \begin{array}{l} A_d = -\frac{R_4}{R_3} \\ A_c = 0 \\ \text{CMRR} = \infty (!) \end{array} \right\}$$

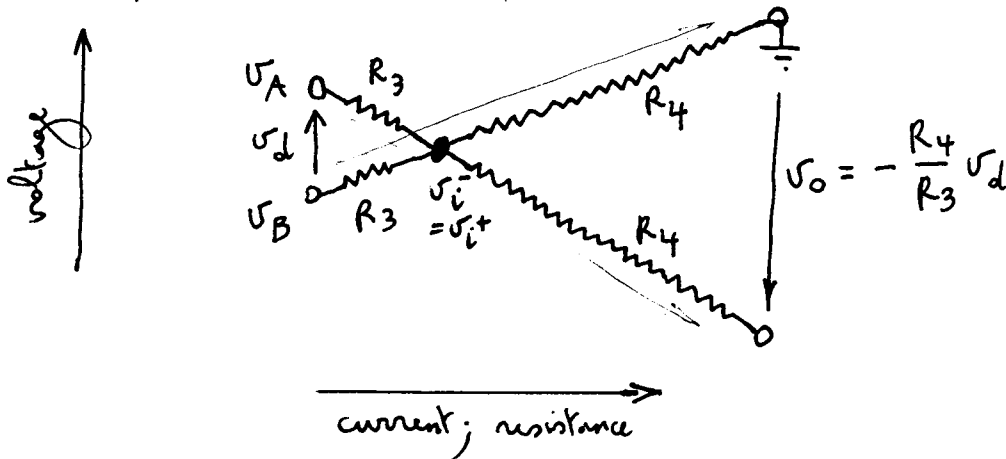Interpretation: voltage drop is linear in resistance:



Problems:

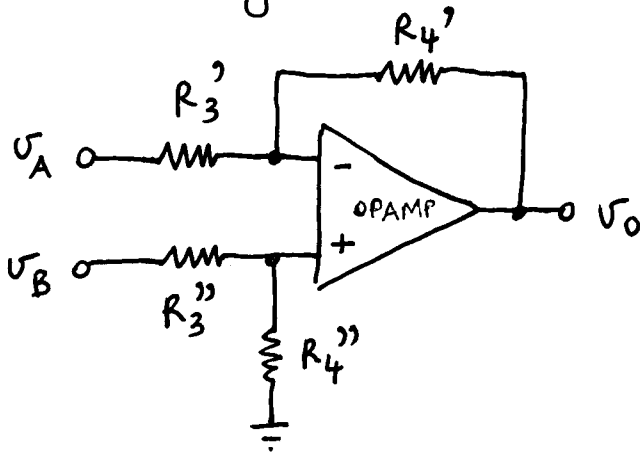1. Sensitivity to TOLERANCE (relative accuracy) in resistance values:



e.g., R_3' and R_3'' : $R_3 \pm 1\%$
 R_4' and R_4'' : $R_4 \pm 1\%$

↓ nominal values (design) ↓ relative accuracy (tolerance)

$$V_0 = -\frac{R_4'}{R_3'} \cdot V_A + \frac{R_4''}{R_3'} \cdot \frac{R_3' + R_4'}{R_3'' + R_4''} \cdot V_B$$


$$\Rightarrow A_d = -\frac{1}{2} \frac{R_4'}{R_3'} - \frac{1}{2} \frac{R_4''}{R_3'} \frac{R_3' + R_4'}{R_3'' + R_4''} \approx -\frac{R_4}{R_3}$$

$$\text{but } A_c = -\frac{R_4'}{R_3'} + \frac{R_4''}{R_3'} \frac{R_3' + R_4'}{R_3'' + R_4''} \neq 0!$$

Corner analysis: worst effects are expected when the resistances are at their corner tolerance values, i.e.:

at +1%, or at -1%, for ±1% tolerance interval:

e.g. for R_3' :

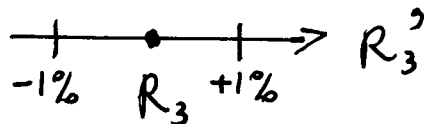

←→ guaranteed range of R_3' values for a nominal R_3 value

↓
lowest corner (worst)

↓
highest corner (worst)

All errors considered:

$\frac{R_3' - R_3}{R_3}$:	+1%	-1%			+1%	-1%	+1%	-1%
$\frac{R_4' - R_4}{R_4}$:	+1%	-1%			-1%	+1%	-1%	+1%
$\frac{R_3'' - R_3}{R_3}$:			+1%	-1%	+1%	-1%	-1%	+1%
$\frac{R_4'' - R_4}{R_4}$:			+1%	-1%	-1%	+1%	+1%	-1%

↓ ↓ ↓ ↓
NO EFFECT!
 same voltage division
 as for nominal R_3 & R_4

↓ ↓
NO EFFECT
ON A_c !
 same voltage
 division for
 V_A & V_B

↓ ↓
GREATEST
EFFECT
ON
 A_c
 $\approx \pm 4\%$ of A_d

Worst case: $A_c \approx \pm 4\%$ of A_d

$\Rightarrow CMRR = \left| \frac{A_d}{A_c} \right| \approx 25!$ clearly unacceptable

2. Differential gain A_d is limited by ratio R_4/R_3 .
 Can't make this ratio too large in practice!

e.g. $\begin{cases} R_3 = 1k\Omega \\ R_4 = 100k\Omega \end{cases} \Rightarrow A_d = -\frac{R_4}{R_3} = -100$

3. Input impedance is too low for use with practical electrodes

$Z_{in}: \begin{cases} \bullet V_A: R_3 = 1k\Omega \\ \bullet V_B: R_3 + R_4 = 101k\Omega \end{cases} < R_{electrode} \sim 150k\Omega - 2M\Omega$

→ The signal is lost before it reaches the amplifier input
 → Input impedance mismatch further contributes to low CMRR


Graphical interpretation of $A_c \approx \left(1 - \frac{R_3''}{R_3'} \cdot \frac{R_4'}{R_4''}\right) \cdot A_d$

(for large $A_d = -\frac{R_4}{R_3}$)

e.g. :


$$\left. \begin{array}{l} R_3' : -1\% \\ R_4' : +1\% \\ R_3'' : +1\% \\ R_4'' : -1\% \end{array} \right\}$$

$\Rightarrow A_c \approx -4\%$ of A_d

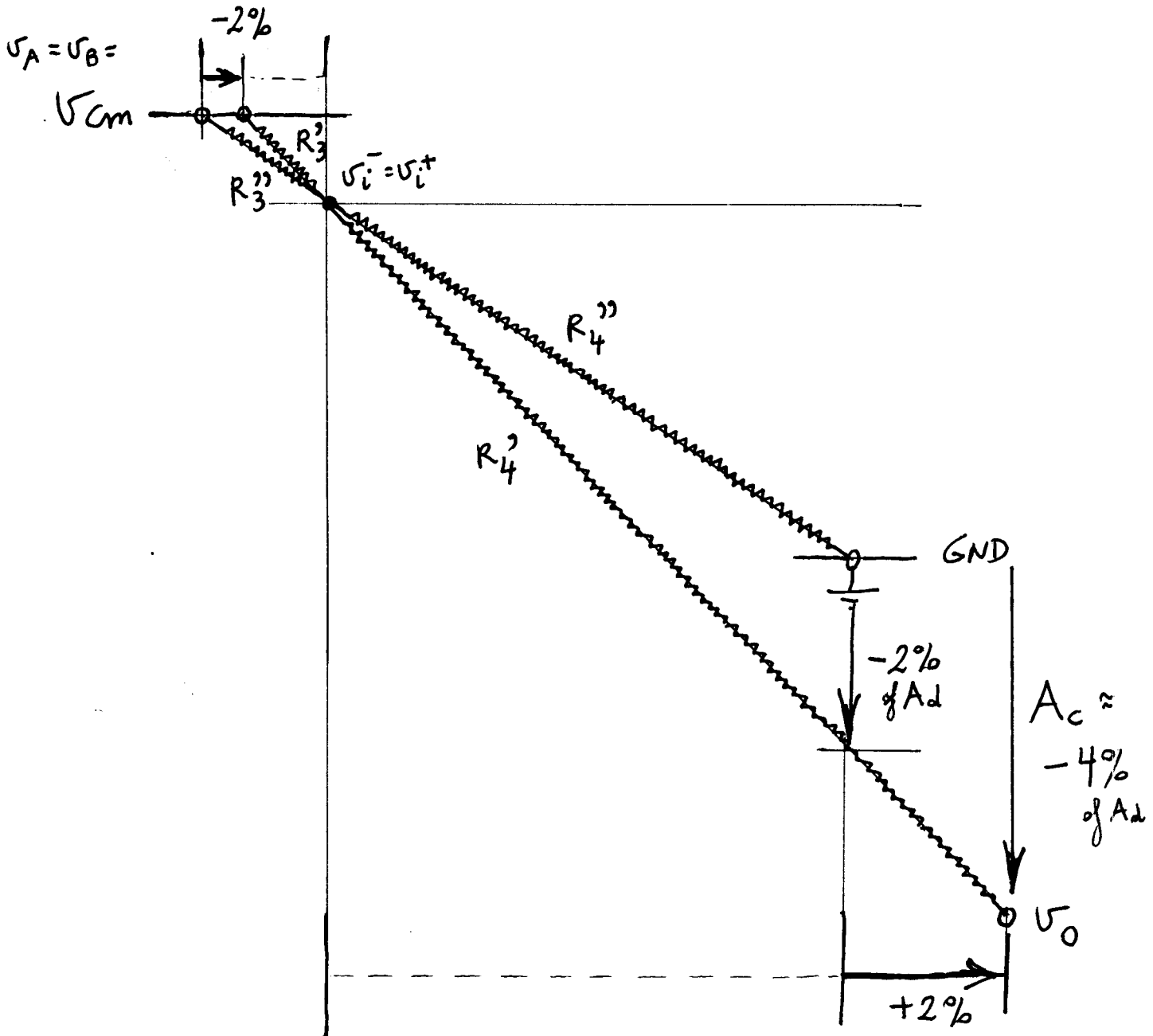

Let us try to fix all these problems by adding a fully differential, high-impedance gain stage in front of this differential amplifier:

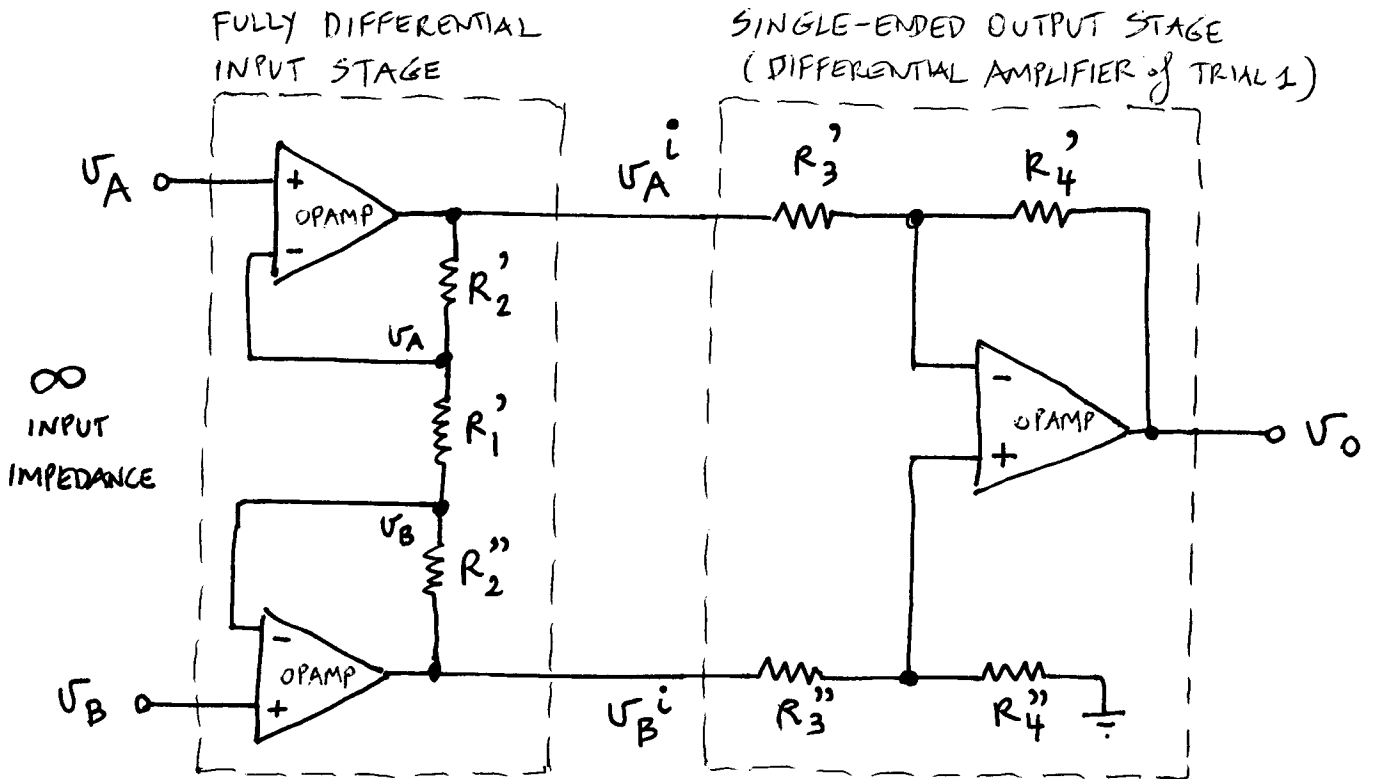TRIAL 2: Instrumentation amplifier (Sec. 3.4)



$$R_1' = R_1 \pm 1\%$$

$$R_2', R_2'' = R_2 \pm 1\%$$

$$R_3', R_3'' = R_3 \pm 1\%$$

$$R_4', R_4'' = R_4 \pm 1\%$$

$$CMRR_{in} \approx 2 \frac{R_2}{R_1}$$

$$A_{d in} \approx 1 + 2 \frac{R_2}{R_1}$$

$$A_{d out} \approx - \frac{R_4}{R_3}$$

$$CMRR_{out} \approx 25$$

$$A_{c in} \approx 1$$


$$A_{c out} \approx 0 \pm 0.04 \frac{R_4}{R_3}$$

gains multiply across stages!

$$A_d \approx - \left(1 + 2 \frac{R_2}{R_1} \right) \cdot \frac{R_4}{R_3}$$

$$A_c \approx 0 \pm 0.04 \frac{R_4}{R_3}$$
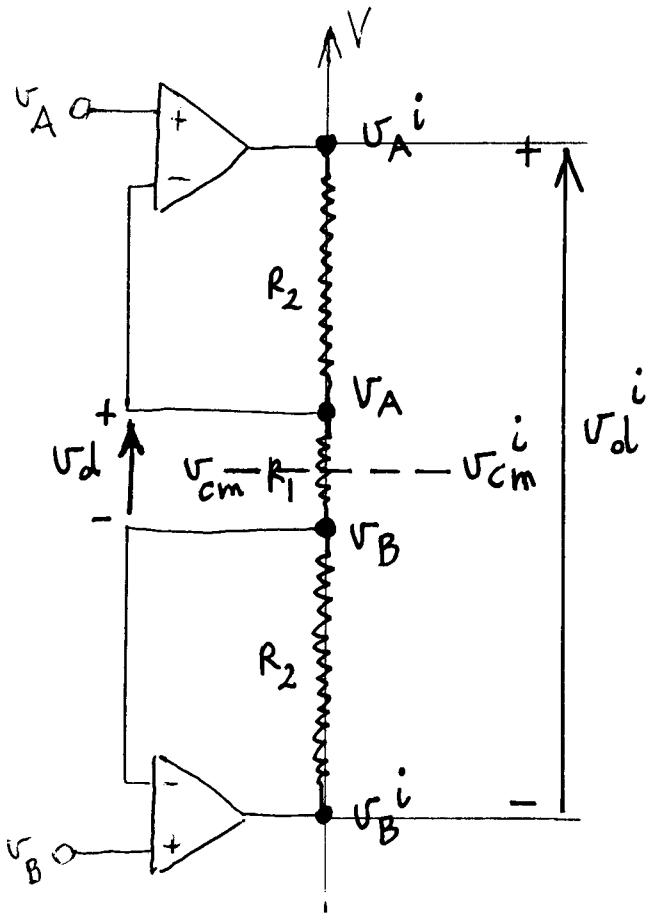
$$CMRR \approx 50 \frac{R_2}{R_1} = CMRR_{in} \cdot CMRR_{out}$$



• INPUT:

$$V_d = V_A - V_B$$

$$V_{cm} = \frac{V_A + V_B}{2}$$

• INTERMEDIATE STAGE:

$$V_d^i = V_A^i - V_B^i$$

$$\approx \frac{R_2 + R_1 + R_2}{R_1} (V_A - V_B)$$

$$= \left(1 + 2 \frac{R_2}{R_1}\right) V_d$$



$$V_{cm}^i = \frac{V_A^i + V_B^i}{2} \approx \frac{V_A + V_B}{2} = V_{cm}$$

$$\Rightarrow A_{d\text{in}} = \frac{V_d^i}{V_d} \approx 1 + 2 \frac{R_2}{R_1}$$


$$A_{c\text{in}} = \frac{V_{cm}^i}{V_{cm}} \approx 1$$

So the input stage boosts the overall CMRR by

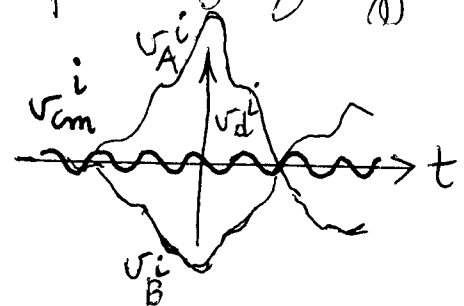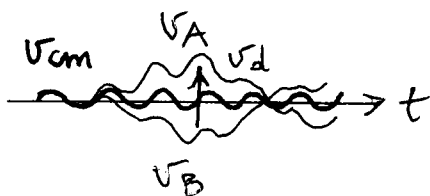$1 + 2 \frac{R_2}{R_1} \approx 2 \frac{R_2}{R_1} \gg 1$, even though it does not reject common-mode inputs by itself! (purely by high differential gain)



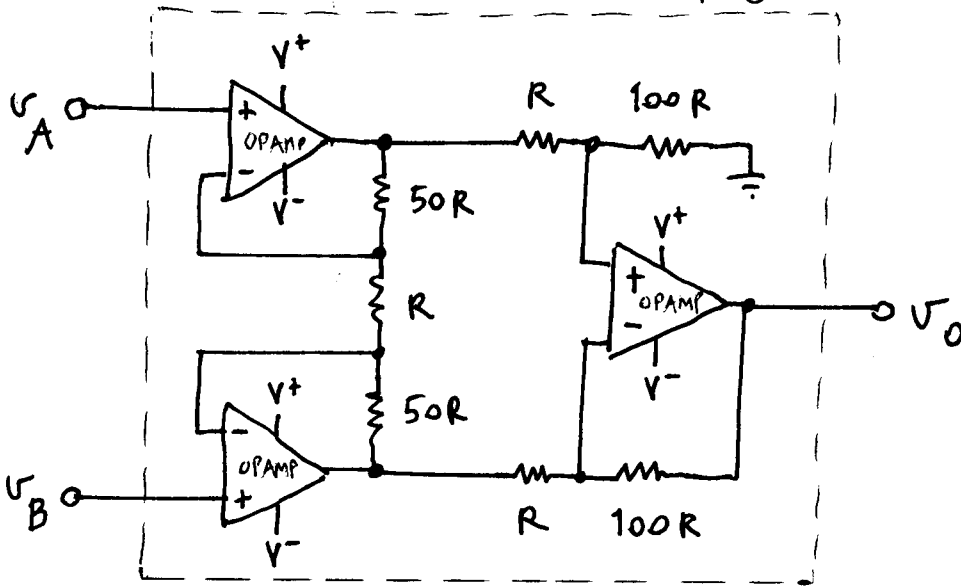Practical instrumentation amplifier (non-inverting):



OPAMP: $\frac{1}{4}$ TLC084
(quad low-power opamp)

$V^+ = 2.5V$ (2 AAA batteries each)
 $V^- = -2.5V$

$R = 1k\Omega$ (or higher, for lower power, at the cost of higher thermal noise)

All resistances $\pm 1\%$

$$\Rightarrow \left\{ \begin{array}{l} A_d = +10,100 \approx 10,000 \\ CMRR \geq 2,525 \approx 2,500 \text{ (worst case)} \\ Z_{inA} = Z_{inB} \approx \infty \end{array} \right.$$



NOTE: Designing / using an I.A. with very high CMRR is NECESSARY but NOT SUFFICIENT for effective common-mode rejection:

- reduce sources of common-mode noise / interference
- reduce sources of CMRR degradation
- perform ACTIVE GROUNDING (DRIVEN RIGHT LEG)


- Good practice for effective common-mode interference rejection:

- Avoid any differential noise coupling


- avoid loops in electrode wiring

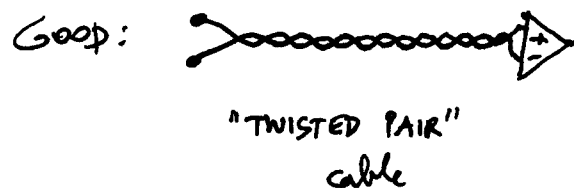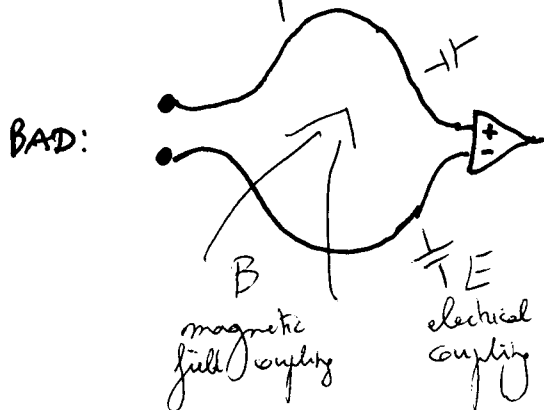

- shield wherever possible

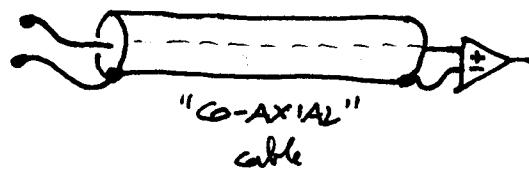

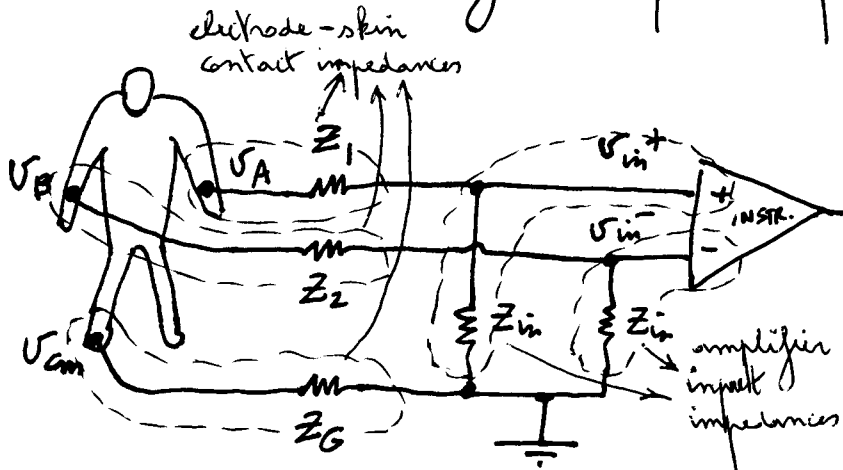- Avoid mismatch in electrode impedance, where the instrument has finite input impedance.




$$V_o = A_d \cdot (V_{in+} - V_{in-})$$


"IDEAL" instrumentation amplifier (CMRR = ∞)

$$V_{in+} - V_{in-} = \frac{Z_{in}}{Z_{in} + Z_1} \cdot V_A - \frac{Z_{in}}{Z_{in} + Z_2} \cdot V_B$$

$$\begin{matrix} |Z_1| \ll |Z_{in}| \\ |Z_2| \ll |Z_{in}| \end{matrix} \quad \approx \quad \frac{Z_2 - Z_1}{Z_{in}} \cdot \underbrace{\frac{V_A + V_B}{2}}_{V_{cm}} + \underbrace{V_A - V_B}_{V_d}$$

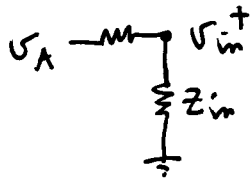

and

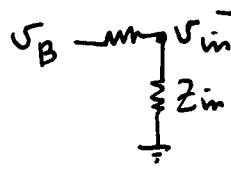

$$V_{cm} + \frac{V_d}{2}$$

$$V_{cm} - \frac{V_d}{2}$$

$$V_{in}^+ - V_{in}^- = \frac{Z_{in}}{Z_{in} + Z_1} \cdot V_A - \frac{Z_{in}}{Z_{in} + Z_2} \cdot V_B$$

$$\frac{Z_{in}}{Z_{in} + Z_1} = \frac{1}{1 + \frac{Z_1}{Z_{in}}} \approx 1 - \frac{Z_1}{Z_{in}} \quad \text{for } |Z_1| \ll |Z_{in}|$$

$$\text{and similarly } \frac{Z_{in}}{Z_{in} + Z_2} \approx 1 - \frac{Z_2}{Z_{in}}$$

$$\approx \left(1 - \frac{Z_1}{Z_{in}}\right) \left(V_{cm} + \frac{V_d}{2}\right) - \left(1 - \frac{Z_2}{Z_{in}}\right) \left(V_{cm} - \frac{V_d}{2}\right)$$

$$= \frac{Z_2 - Z_1}{Z_{in}} \cdot V_{cm} + \left(1 + \frac{Z_1 + Z_2}{2 Z_{in}}\right) \cdot V_d$$

$\ll 1$

$$\approx \frac{Z_2 - Z_1}{Z_{in}} \cdot V_{cm} + V_d$$

$$\Rightarrow V_o \approx A_d \cdot \frac{Z_2 - Z_1}{Z_{in}} \cdot V_{cm} + A_d \cdot V_d$$

$A_{c,eff}$ effective common-mode gain due to impedance mismatch

$$\Rightarrow CMRR = \frac{|A_d|}{|A_{c,eff}|} = \frac{|Z_{in}|}{|Z_2 - Z_1|}$$

$$\Rightarrow \text{CMRR} = \frac{|Z_{in}|}{|Z_2 - Z_1|} = \frac{\text{input impedance}}{\text{electrode impedance MISMATCH}}$$

\Rightarrow Mismatch in electrode impedance degrades the CMRR of even a perfect bioamplifier


Example:


$$\left\{ \begin{array}{l} Z_{in} = 100 \text{ M}\Omega \text{ (large!)} \\ Z_1 = 100 \text{ k}\Omega \\ Z_2 = 110 \text{ k}\Omega \end{array} \right. \Rightarrow \text{CMRR} = 10,000 \text{ (80 dB)}$$

$$\left\{ \begin{array}{l} Z_{in} = 1 \text{ M}\Omega \\ Z_1 = 200 \text{ k}\Omega \\ Z_2 = 100 \text{ k}\Omega \end{array} \right. \Rightarrow \text{CMRR} = 10 \text{ (20 dB) BAD!}$$

Note: Z_1 , Z_2 and Z_{in} are affected by capacitance, and depend on frequency

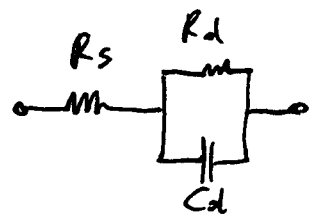• Z_1, Z_2 : $R_s + \frac{R_d}{1 + j\omega R_d C_d}$



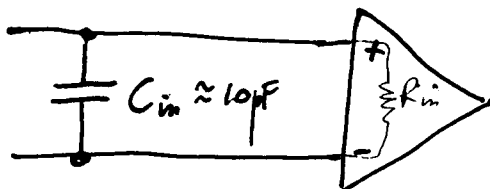
• Z_{in} :  : $\frac{1}{j\omega C_{in}}$ is significant at higher frequencies

Remedy: ACTIVE grounding of the body by COMMON-MODE FEEDBACK: "DRIVEN RIGHT LEG" (DRL).

• Active grounding: "DRIVEN RIGHT LEG" (DRL)

Solution to the CMRR degradation due to impedance mismatch, by reducing V_{cm} directly.

- Passive grounding (not recommended):

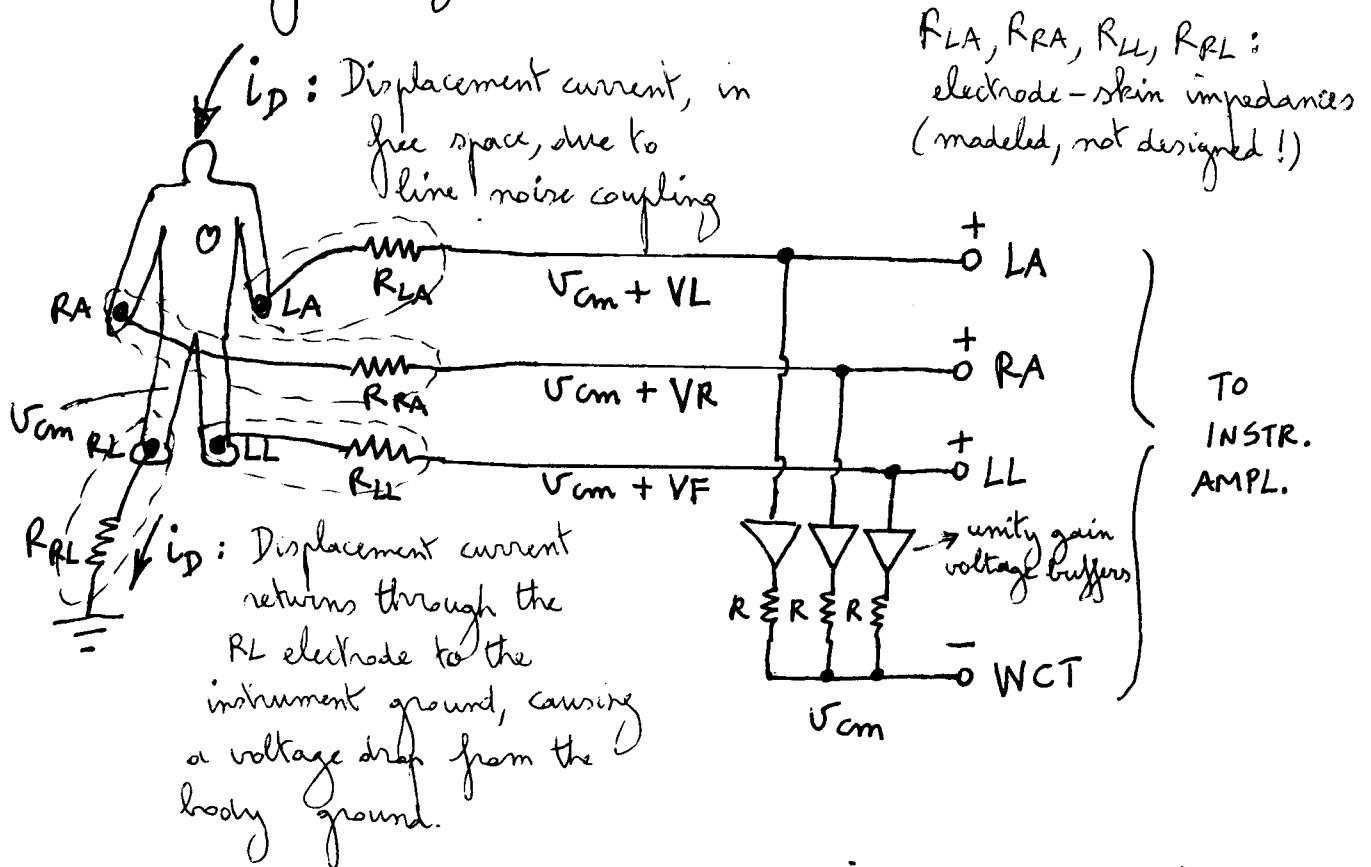

$$V_{cm} \approx R_{RL} \cdot i_D$$

↓
Common-mode noise in the body

↓
right leg electrode impedance

↓
line noise displacement current injected into the body by coupling

$$i_D \approx 1 \mu A_{pp} \text{ typical}$$


$$R_{RL} \approx 100 k\Omega \text{ typical}$$

$$\Rightarrow V_{cm} \approx 100 mV_{pp}$$

but can be much larger!

Large V_{cm} may leak through at the differential outputs and may saturate the instrumentation amplifiers.

- DRL active grounding:

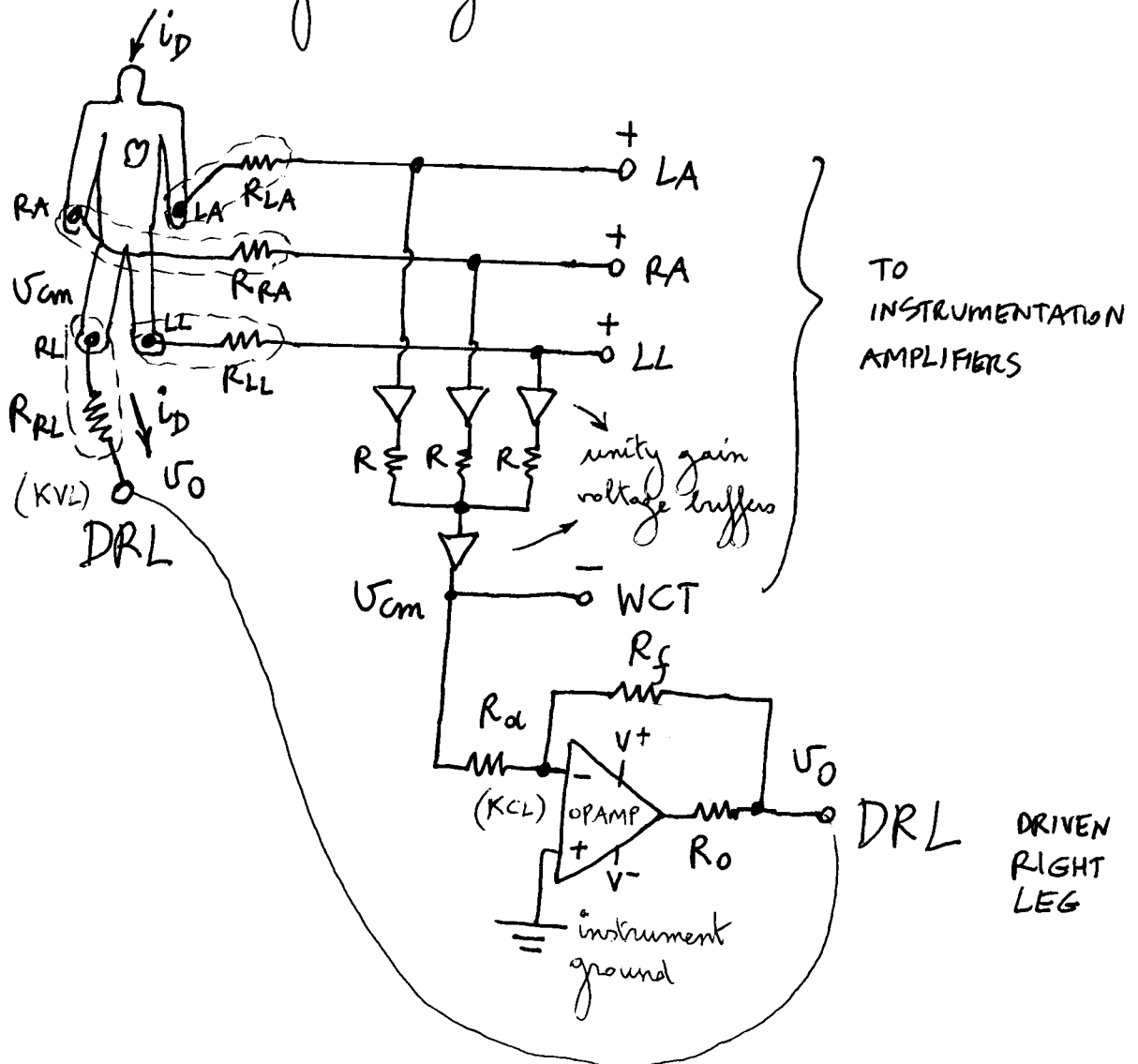

$$V_0 = -\frac{R_f}{R_a} \cdot V_{cm} \quad (\text{KCL})$$

$$V_{cm} = R_{RL} \cdot i_D + V_0 \quad (\text{KVL})$$

$$V_{cm} = R_{RL} i_D - \frac{R_f}{R_a} V_{cm}$$

$$\Rightarrow V_{cm} = \frac{R_{RL} i_D}{1 + \frac{R_f}{R_a}} = R_{RL \text{ eff}} \cdot i_D \quad \text{with } R_{RL \text{ eff}} = \frac{R_{RL}}{1 + \frac{R_f}{R_a}}$$

\downarrow
 effective electrode resistance
 equivalent to
 passive grounding

\Rightarrow DRL active grounding reduces R_{RL} (and V_{cm}) by feedback gain $1 + \frac{R_f}{R_a}$.

Example :

$$i_D = 1 \mu A_{pp}$$

$$R_{RL} = 100 k\Omega$$


$$R_a = 1 k\Omega$$

$$R_f = 100 k\Omega$$


$$\left. \begin{array}{l} R_a = 1 k\Omega \\ R_f = 100 k\Omega \end{array} \right\} 1 + \frac{R_f}{R_a} = 101 (\approx 100)$$

$\Rightarrow R_{RL \text{ effective}} \approx 1 k\Omega$ and $V_{cm} \approx 1 mV_{pp}$
 hundred-fold improvement in SNR
 (for common mode noise)

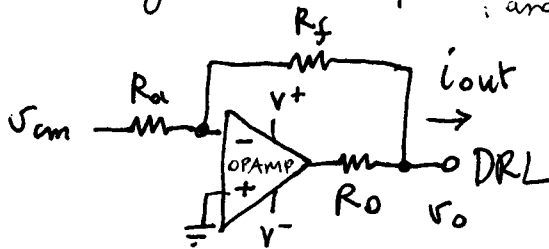Function of R_o : patient and instrument protection against short circuit
 (and caregivers)



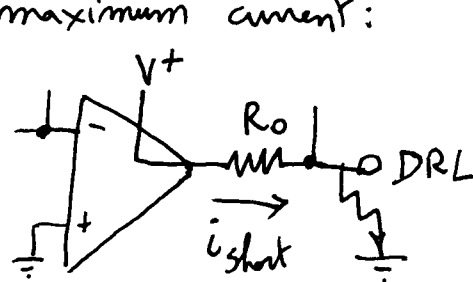- normal operation : OPAMP in linear region
 - \rightarrow zero output impedance for effective driving of R_L
- current limiting operation during short circuit: OPAMP saturated
 - \rightarrow maximum current:



$$i_{short} = \frac{V^+}{R_o}$$


and $\frac{V^-}{R_o}$ in other polarity

e.g.:

$$\left. \begin{array}{l} V^+ = 2.5V \\ R_o = 1 M\Omega \end{array} \right\} i_{short} = 2.5 \mu A \text{ (SAFE)}$$

Practical one-lead ECG circuit with DRL active grounding: (Sec. 6.5 ; Fig. 6.15)

e.g., lead I:

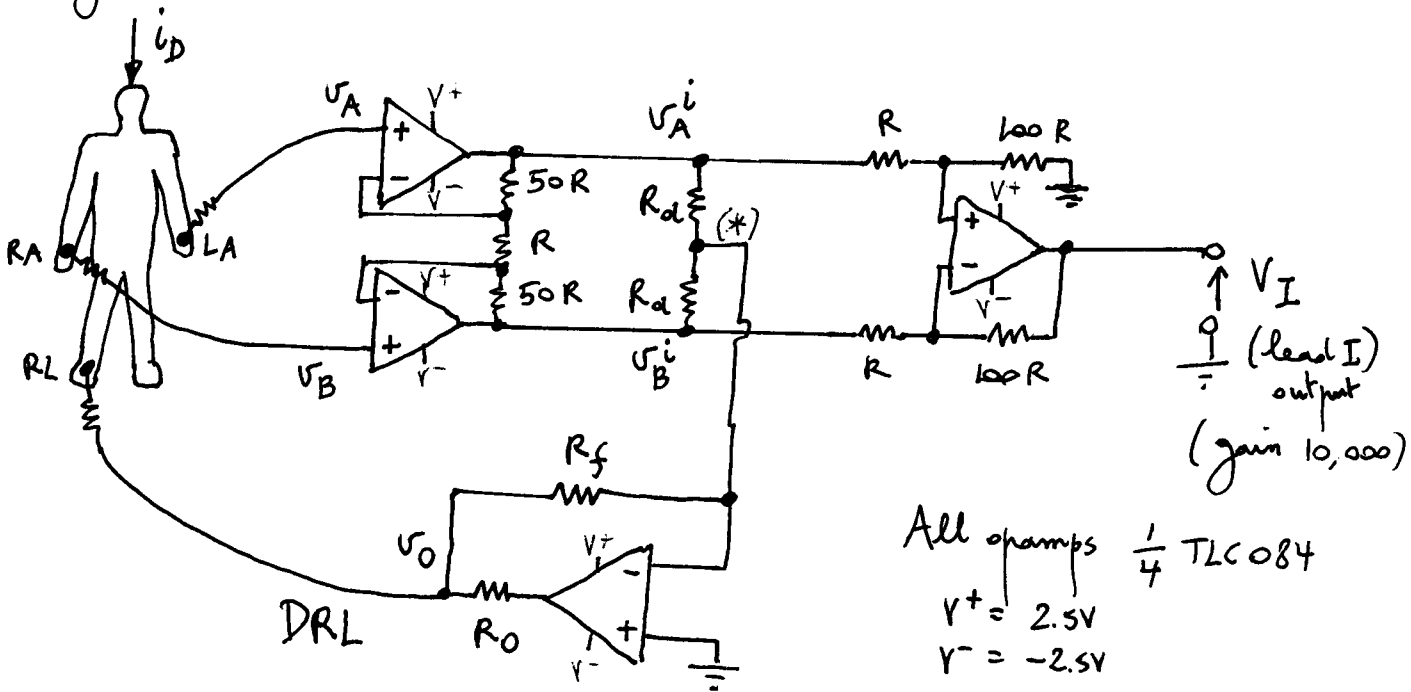

All opamps $\frac{1}{4}$ TLC084

$V^+ = 2.5V$
 $V^- = -2.5V$


$R = 1k\Omega$

$R_a = 20k\Omega$ all $\pm 1\%$

$R_f = 1M\Omega$

$R_0 = 1M\Omega$

DRL equivalent circuit:

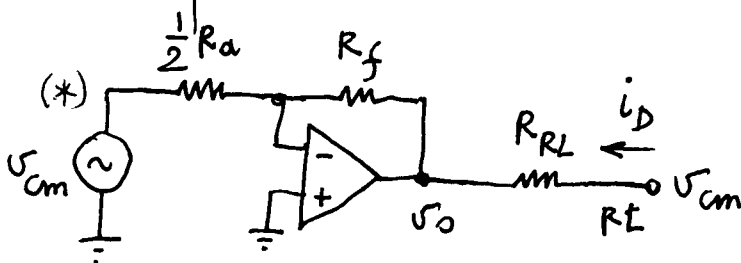


$$\Rightarrow R_{RL\text{eff}} = \frac{R_{RL}}{1 + 2\frac{R_f}{R_a}} : \text{factor } 101 \text{ reduction in } V_{cm}$$

and $i_{\text{short}} = 2.5\mu A$



- Transient protection and AC signal coupling (Sec. 6.4)

Diodes can be used to clamp over-voltage for protection of voltage-sensitive inputs:

- Single diode, positive clipping:

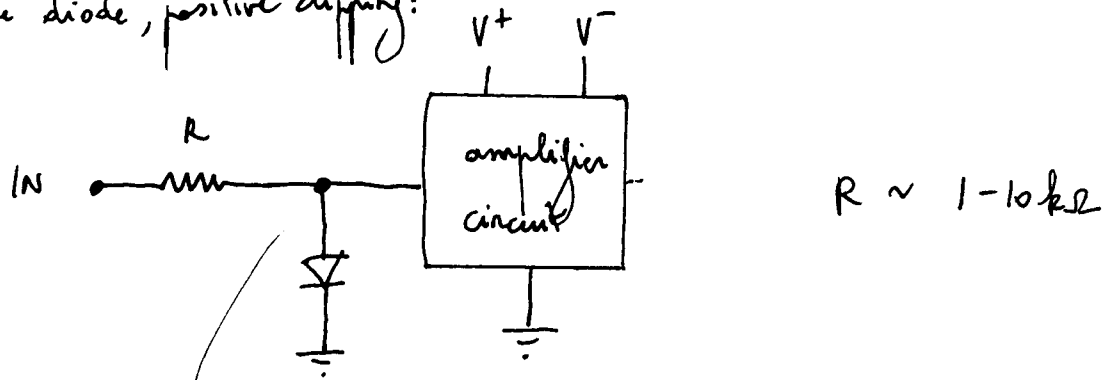

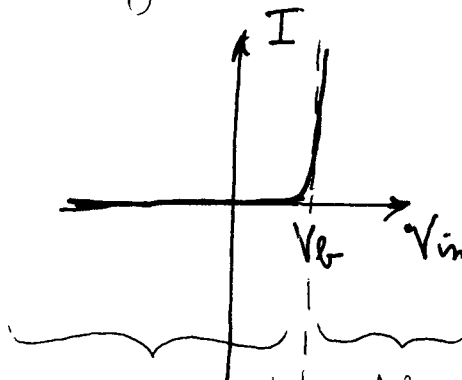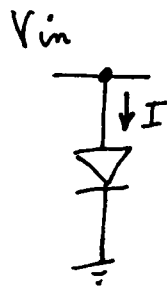
protects the amplifier input from voltages coming in that are greater than $+V_b$:




$V_b \approx 0.7V$
for a typical diode

Almost zero current for $V_{in} < V_b$
 \Rightarrow input signal passes through unattenuated

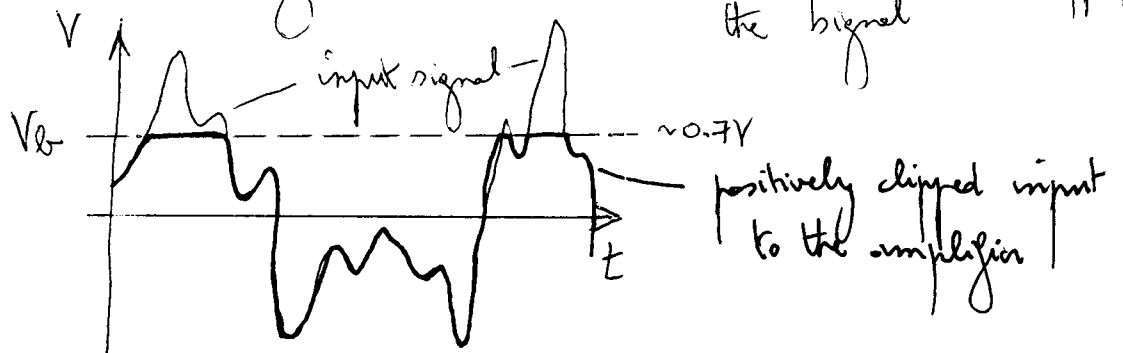
Almost infinite current for $V_{in} > V_b$
 \Rightarrow amplifier input is clamped at V_b , clipping the signal




- single diode, negative clipping:

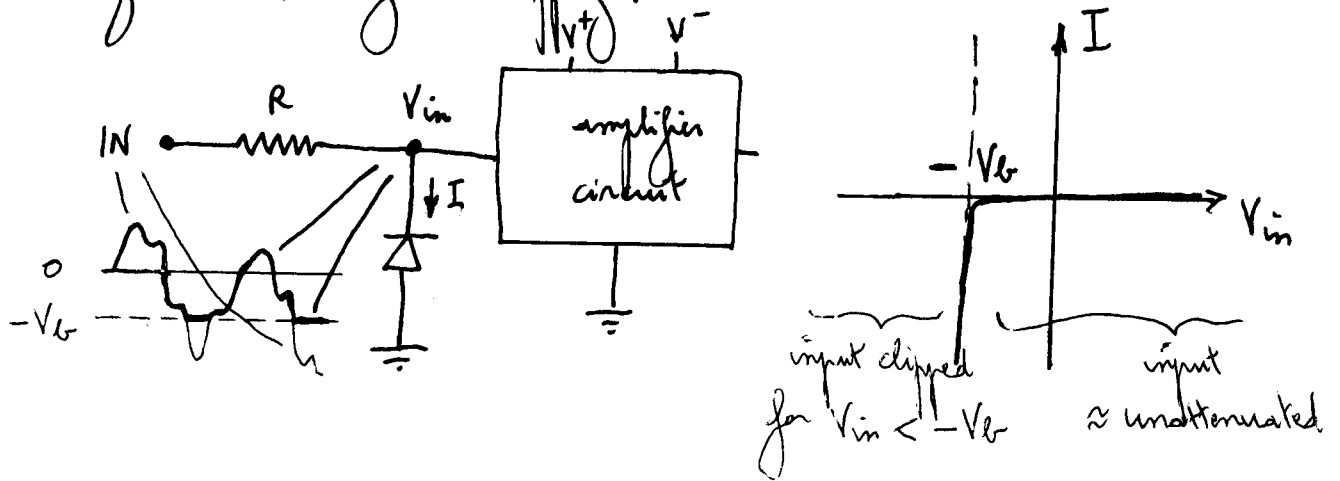

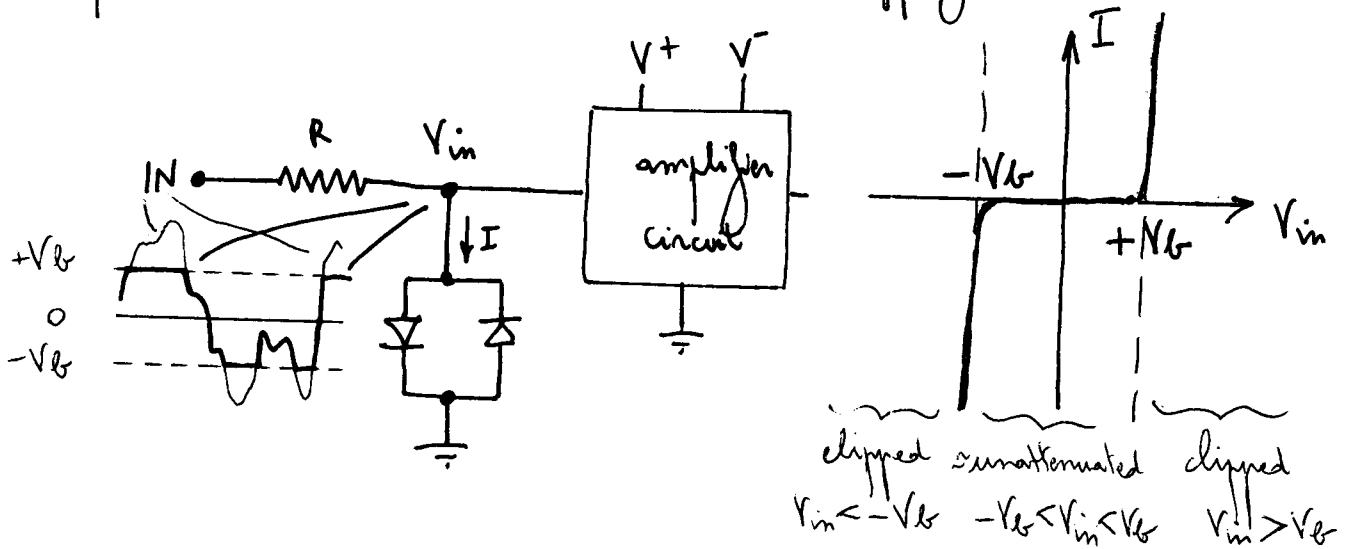
- parallel double diode, bidirectional clipping:



- double-rail diode protection:

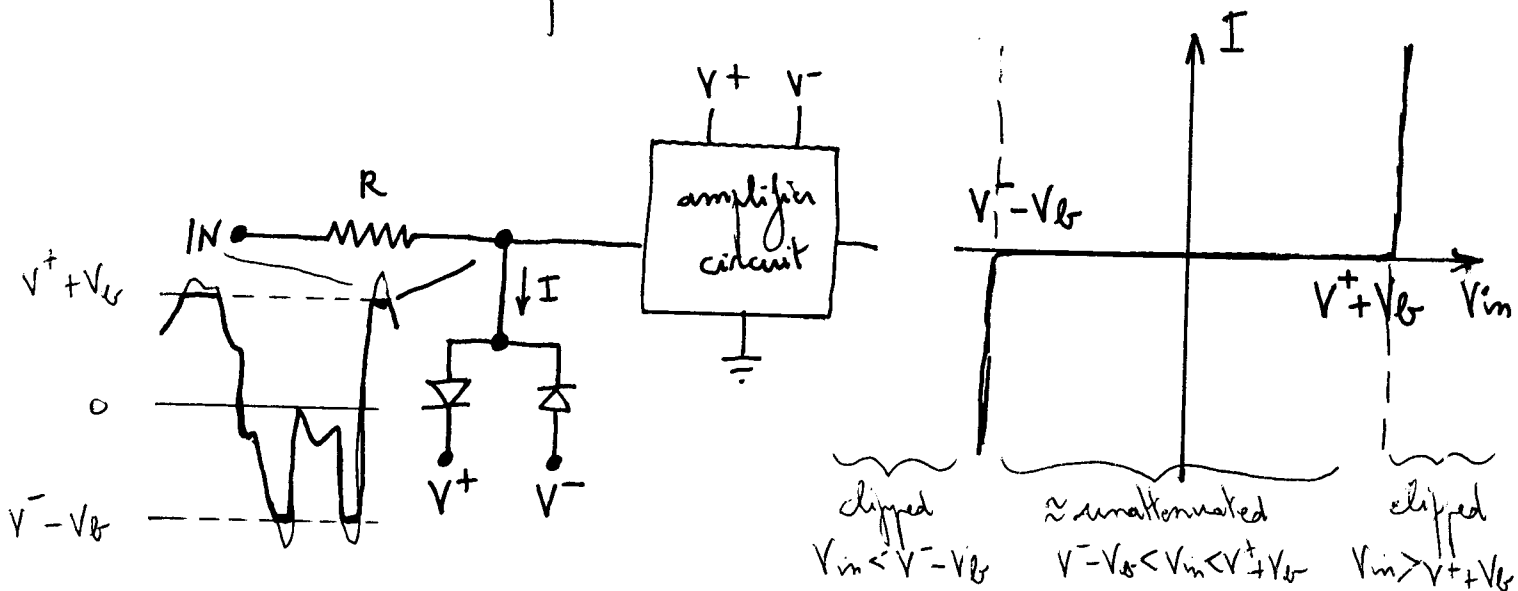


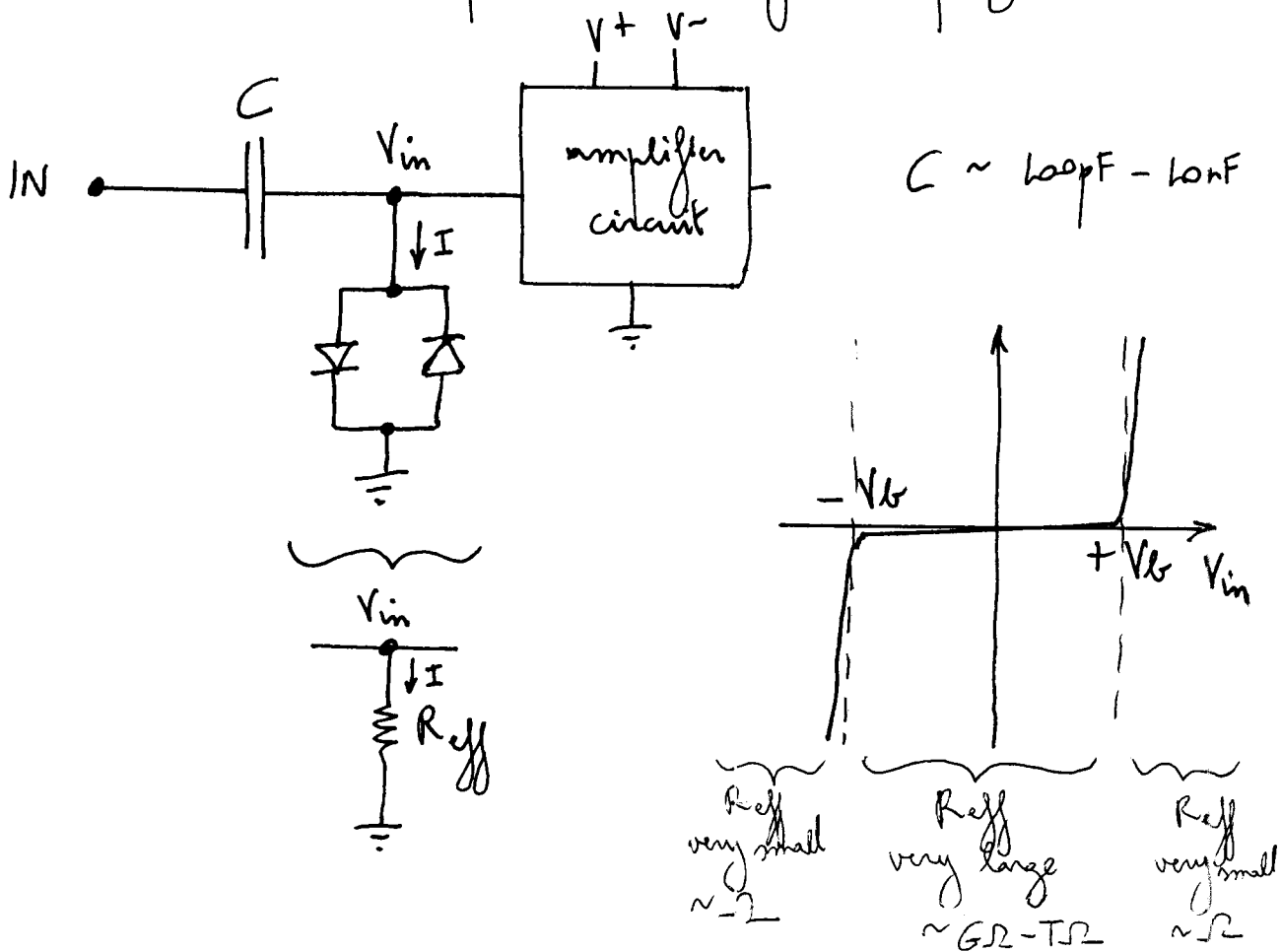- parallel double diode, capacitive AC signal coupling:




\Rightarrow HIGHPASS at very low cut-off frequency $f_c \ll 1 \text{ Hz}$


for SMALL SIGNALS

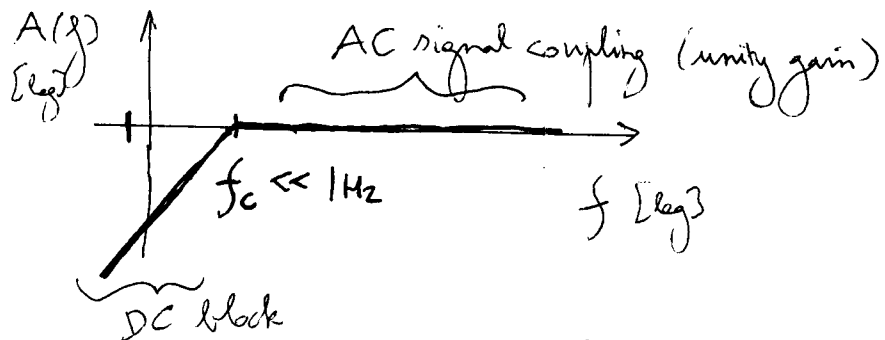

\Rightarrow CLIPPING and over-voltage protection for LARGE SIGNALS ($|V_{in}| > V_b$)

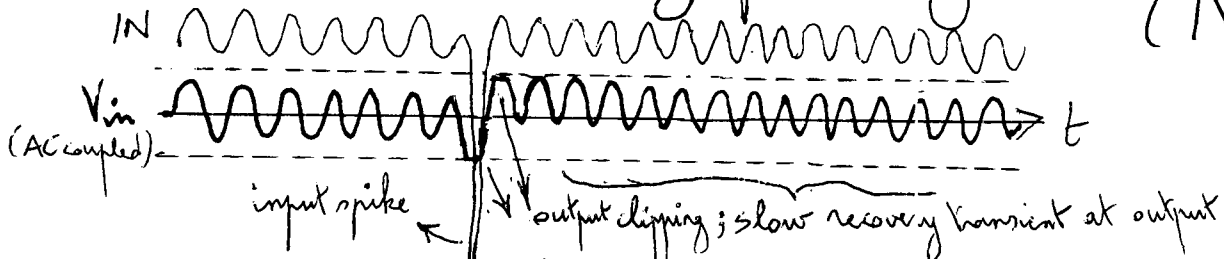

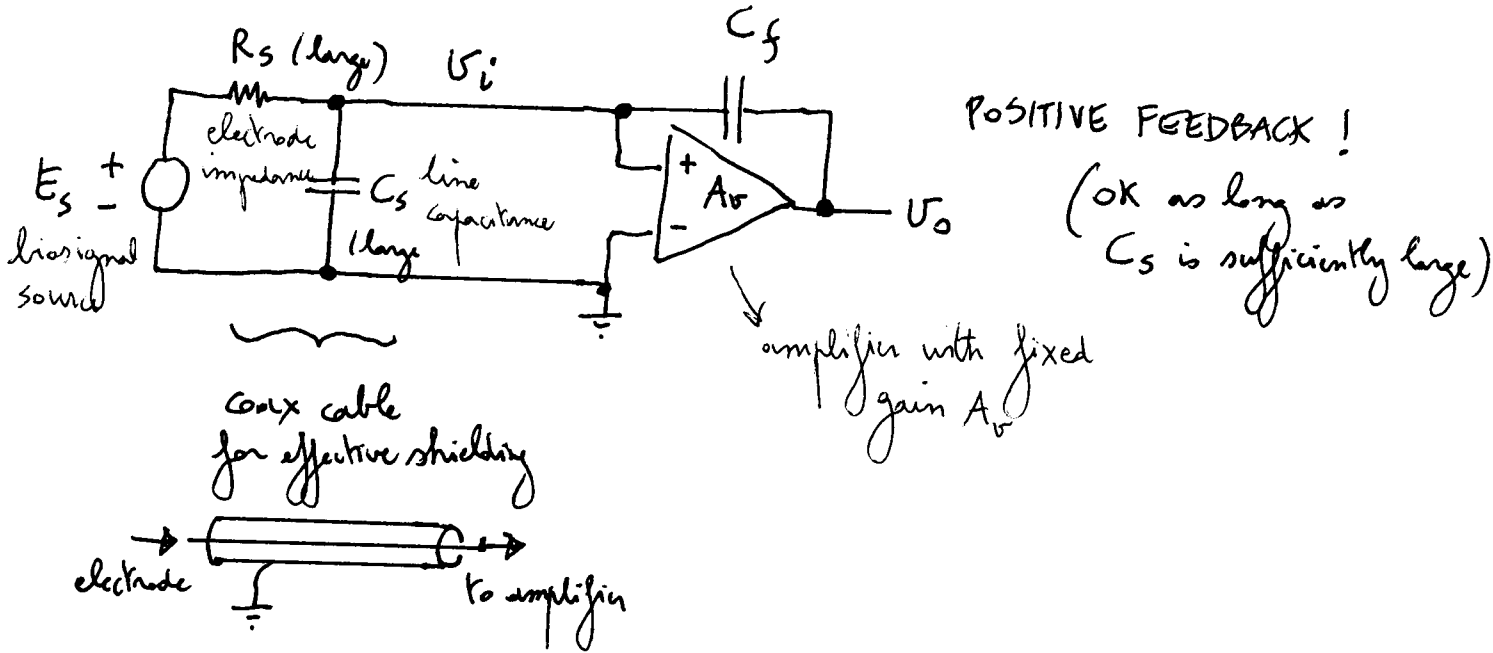- Impedance cancellation: necessary to compensate for large RC delays due to high electrode impedance and high line capacitance.
(Sec. 6.6)



$$\Rightarrow \text{(KCL @ } v_i) \quad - (E_s - v_i)/R_s + j\omega C_s v_i = j\omega C_f (A_v v_i - v_i)$$

$$\text{or } v_i = \frac{1}{1 + j\omega R_s C_{eff}} E_s$$

$$v_o = \frac{A_v}{1 + j\omega R_s C_{eff}} E_s$$

where $C_{eff} = C_s - (A_v - 1)C_f$ effective capacitance due to feedback

$\Rightarrow Z = 0$ when $C_{eff} = 0$ for $C_s = (A_v - 1)C_f$
but careful to avoid instability! $C_s > (A_v - 1)C_f$