

Lecture 18

Design for Electrical Protection

References

Webster, Ch. 14 (Sec. 14.3-14.9).


DESIGN FOR PROTECTION

- Source of macroshock/microshock hazards: typically GROUND CURRENTS
 - wireless or implanted systems → no issue! (no ground current path)
 - wireline systems → avoid GROUND FAULTS

Typical distribution of line power (Chap. 14.3)





supplied through transformer:

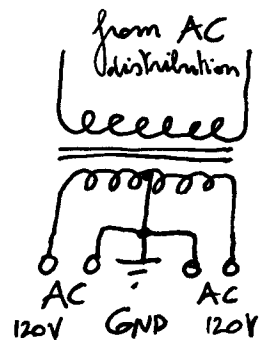

(Fig. 14.8)

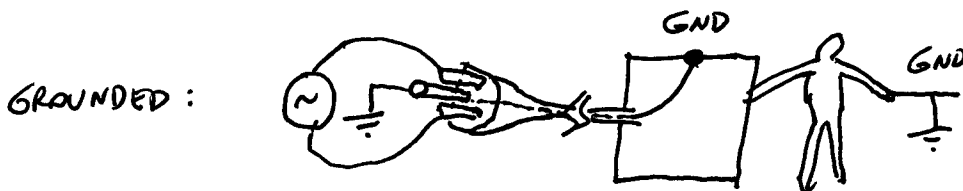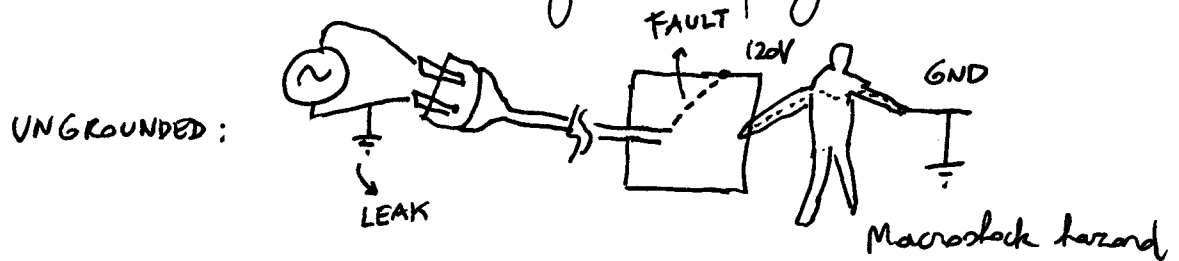- Always ground the chassis of the bioinstrument! Don't use ungrounded plugs:



- Additional protection at power distribution:
 - circuit breakers (always); surge protectors; etc.

- Equipment design for protection → Sec. 14.9, and Chap. 6 revisited

• Electrical isolation, when feasible: SEPARATE GROUNDS


e.g.: • optocouplers (V or I → light → V or I)

• wireless power/telemetry (for many great reasons!)
→ see guest lectures

• Circuit protection against ground faults:

- INPUTS:

e.g.:

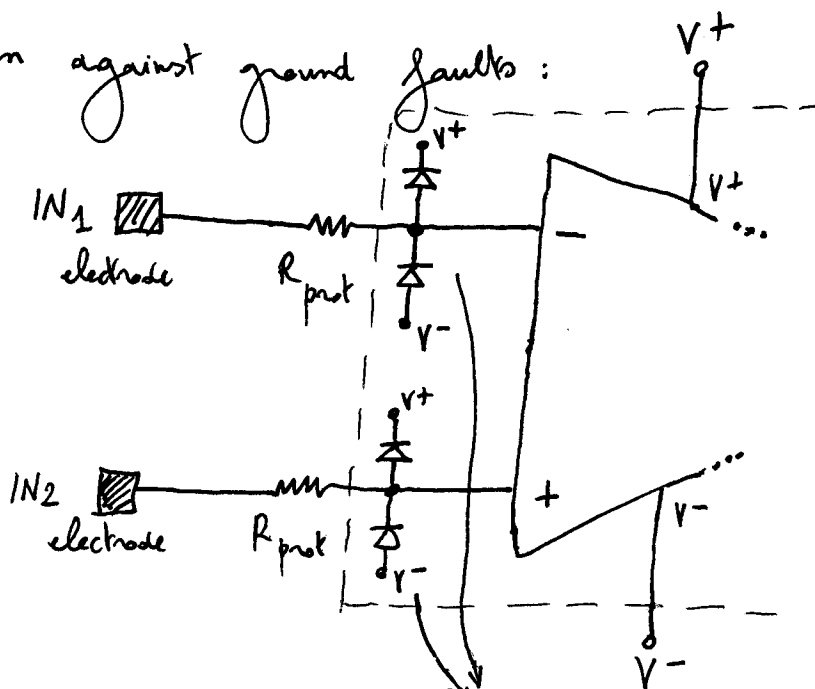

$R_{prot} = 100k\Omega$ typically OK:
maximum current:


$$V_{AC} / R_{prot} = 120V / 100k\Omega = 1.2mA \text{ (OK)}$$

typically included in commercial amplifiers such as OP27

- OUTPUTS:

Can't add a large R_{prot} in series with the output!
(because $R_{out} \geq R_{prot}$)

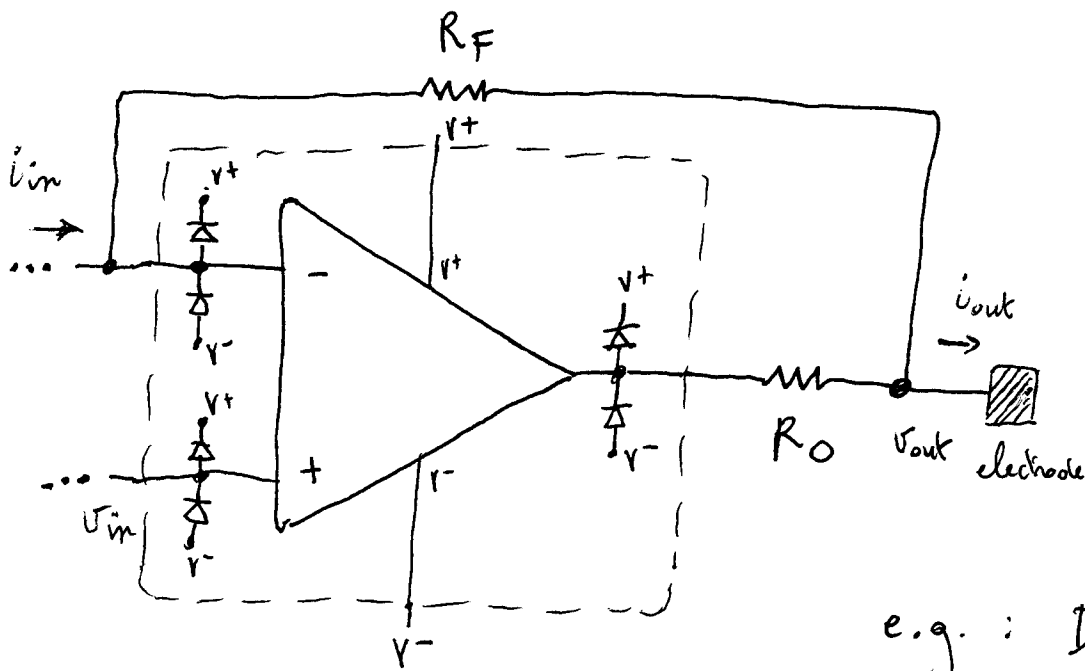SOLUTION: add the resistance BEFORE the feedback:



e.g.: DRL (Chap. 6)

- ⇒
- Output impedance is low as desired
(typically $\sim 100\Omega$, way smaller than the electrode impedance onto the body)

$R_{out} \ll R_O$! because the high-gain negative feedback: $V_{out} = V_{in} - R_F i_{in}$
independent of i_{out} as long as the opamp is not saturated.

- Maximum output current is low as desired owing to opamp saturation

$$i_{out \max} \approx V^+ / R_O$$

$$i_{out \min} \approx V^- / R_O$$

typically μA 's for low V^+ and V^-

ground fault: $V_{AC} / R_O = 12V / 100k\Omega = 1.2 \text{ mA}$
OK