

BENG 186B Winter 2024

Quiz 1

Friday, January 26, 2024

Name (Last, First): _____

- This quiz is on-line, open-book, and open-notes, but web search is prohibited. You may follow electronic links from Canvas or the class web pages, but not any further. **No collaboration or communication in any form is allowed**, except for questions to the instructor and TAs.
- The quiz is due January 26, 2024 at 11:59pm, over Canvas Gradescope. It should approximately take 2 hours to complete, but there is no time limit other than the submission deadline. Do not discuss any class-related topics among yourselves before or after you have completed your quiz, and until the submission deadline has passed.
- There are 3 problems. Points for each problem are given in **[brackets]**. There are 100 points total.

1. [20 pts] Circle the **best answer (only one answer per question)**:

(a) [4 pts] The Thévenin and Norton equivalents of an electrical circuit:

- i. represent the circuit as a source in series with an impedance.
- ii. assume a perfect load with infinite impedance.
- iii. have identical impedance.
- iv. none of the above.

(b) [4 pts] The accuracy of a bioinstrument:

- i. is independent of precision.
- ii. can be improved by calibration.
- iii. is half of its resolution at worst.
- iv. all of the above.

(c) [4 pts] At zero frequency an inductor:

- i. is an open circuit.
- ii. induces a voltage.
- iii. has zero magnetic field.
- iv. none of the above.


(d) [4 pts] The piezoelectric effect causes:

- i. a change in voltage with pressure.
- ii. a change in resistance with strain.
- iii. a stress proportional to strain.
- iv. all of the above.

(e) [4 pts] The sensitivity of a Wheatstone bridge sensor is maximized by:

- i. choosing equal resistances.
- ii. maximizing the supply voltage.
- iii. adding complementary sensors in a double differential configuration.
- iv. all of the above.

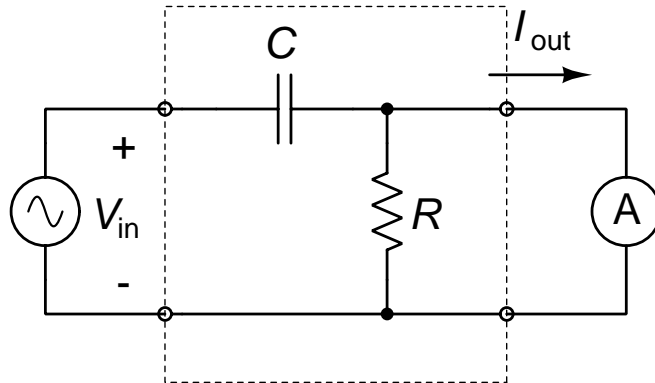2. [40 pts] Consider the *voltage-input, current-output* filter circuit below. You may assume an ideal voltage source for V_{in} , and an ideal ammeter for I_{out} .




- (a) [10 pts] Find the input impedance $Z_{in}(j\omega)$.

(b) [10 pts] Find the output impedance $Z_{out}(j\omega)$.

(c) [10 pts] Find the transfer function $H(j\omega) = I_{out}(j\omega) / V_{in}(j\omega)$. Verify the units.

- (d) [10 pts] Sketch the Bode plot of the transfer function $H(j\omega)$ for $C = 1$ nF and $R = 100$ k Ω . Be sure to label the axes and indicate the units.

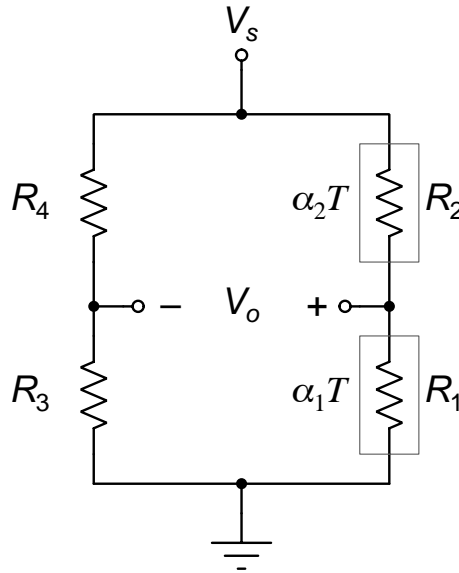3. [40 pts] Consider the temperature transducer below, with constant supply voltage $V_s = 1$ V, a first thermistor R_1 with nominal resistance R_{nom} and temperature coefficient α_1 , a second thermistor R_2 with same nominal resistance but with complementary temperature coefficient $\alpha_2 = -\alpha_1$, and two identical resistors $R_3 = R_4 = R$. The transducer produces a differential output voltage V_o in response to temperature T acting on both thermistors.



$$R_1 = R_{\text{nom}} (1 + \alpha_1 T)$$

$$R_2 = R_{\text{nom}} (1 + \alpha_2 T)$$

- (a) [10 pts] Find the output voltage V_o as a function of temperature T . Is the voltage response linear in temperature, and why?

(b) [10 pts] Find the sensitivity and the offset of the transducer.

- (c) [10 pts] The flexible wearable temperature sensor is mounted on the skin of a patient to monitor body temperature. Due to stretching during movement the thermistors and resistors are all subject to the same strain ϵ . If all four resistances have the same strain gauge factor G , show that the voltage response of the transducer is insensitive to strain.

- (d) [10 pts] The wearable sensor is powered by a lithium-ion battery which is subject to voltage variations. How do the offset and sensitivity change for a 10 % drop in the voltage supplied by the battery? Explain.