

# 520.492 Mixed-Signal VLSI Systems

*Week 4*

## **Data Conversion**

### **References**

1. Geiger, Allen and Strader: pp. 612-672.
2. Franca and Tsividis, Chapter 9.


# DATA CONVERSION

ref # { • GEIGER, ALLEN & STRADER, pp 612-672  
 • FRANCA & TSINIDIS, CHAPTER 9

- D/A Conversion:  $\{D_i\} \rightarrow A$
- A/D Conversion:  $A \rightarrow \{D_i\}$






$$D = D_{n-1} D_{n-2} \dots D_3 D_2 D_1 D_0$$

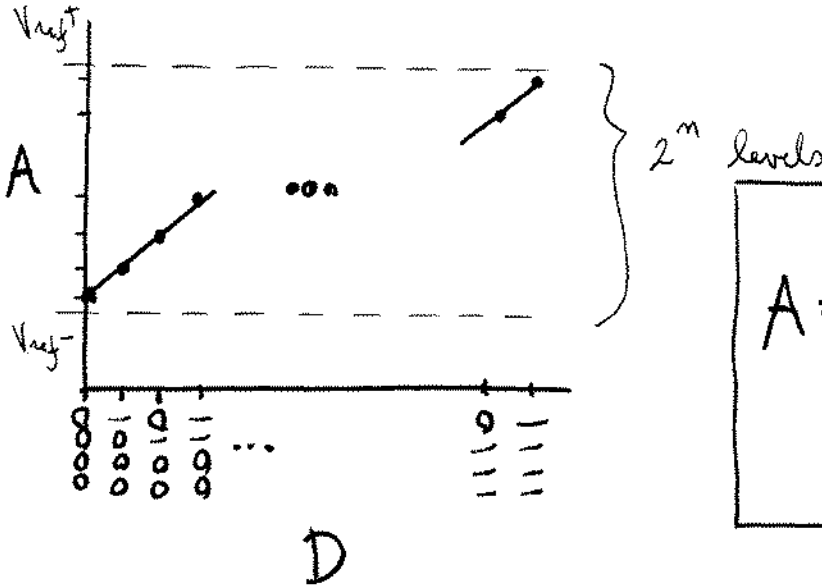$i=0$ : LSB  
 $i=m-1$ : MSB  
 $m = \# \text{ bits}$



$$A = \left( \sum_{i=0}^{n-1} 2^{i-m} D_i + 2^{-1-m} \right) (V_{ref+} - V_{ref-}) + V_{ref-}$$

## Applications (just a few of them ...)

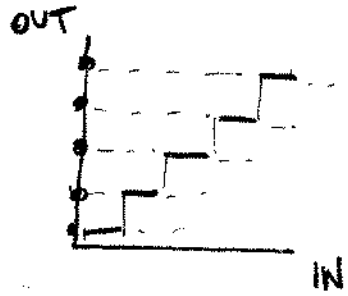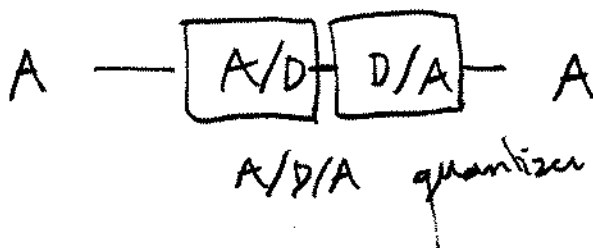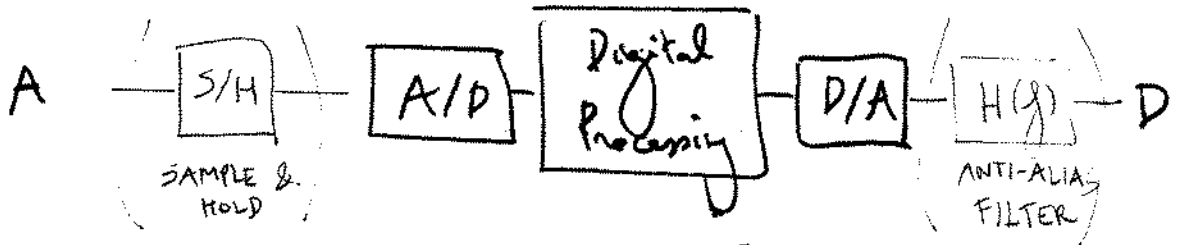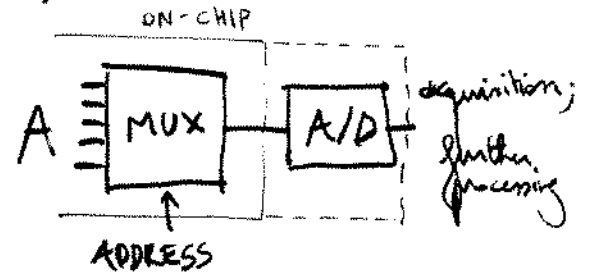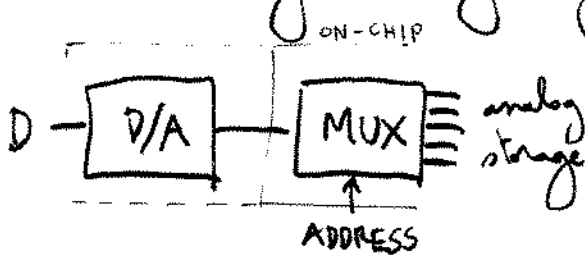




# D/A CONVERTERS



1) PARALLEL :



• voltage mode:

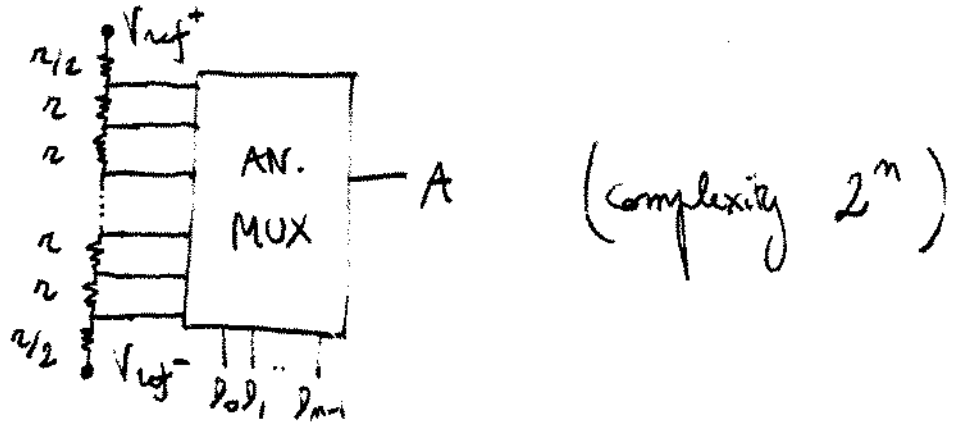


• current mode:

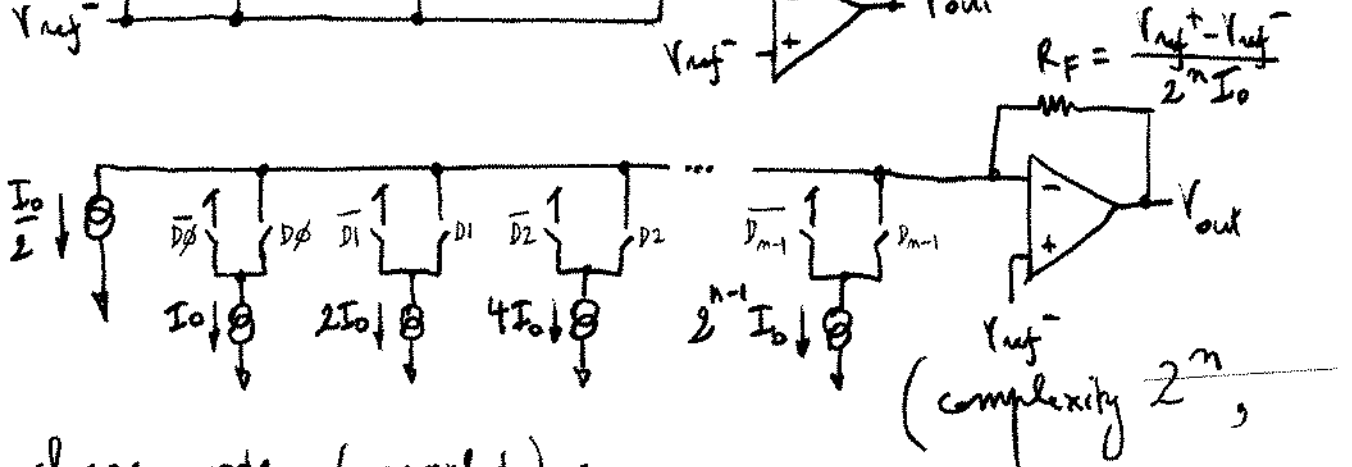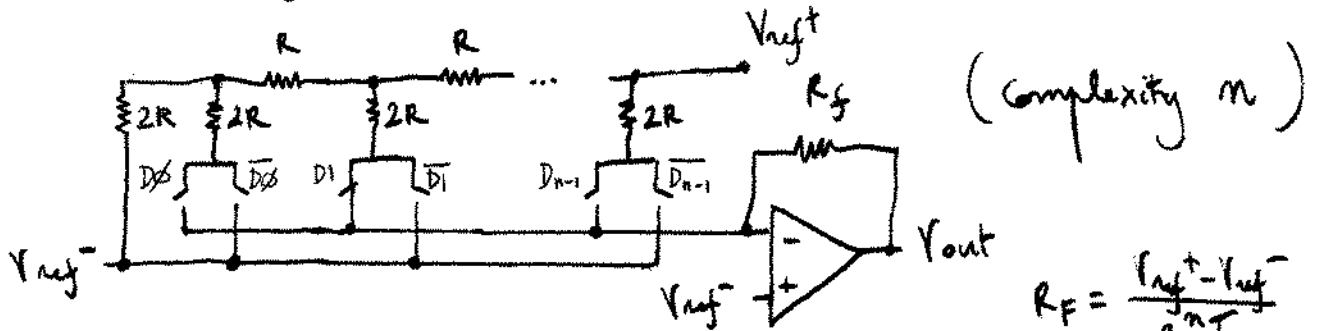


• charge mode (sampled):

(unless pre-scaled)

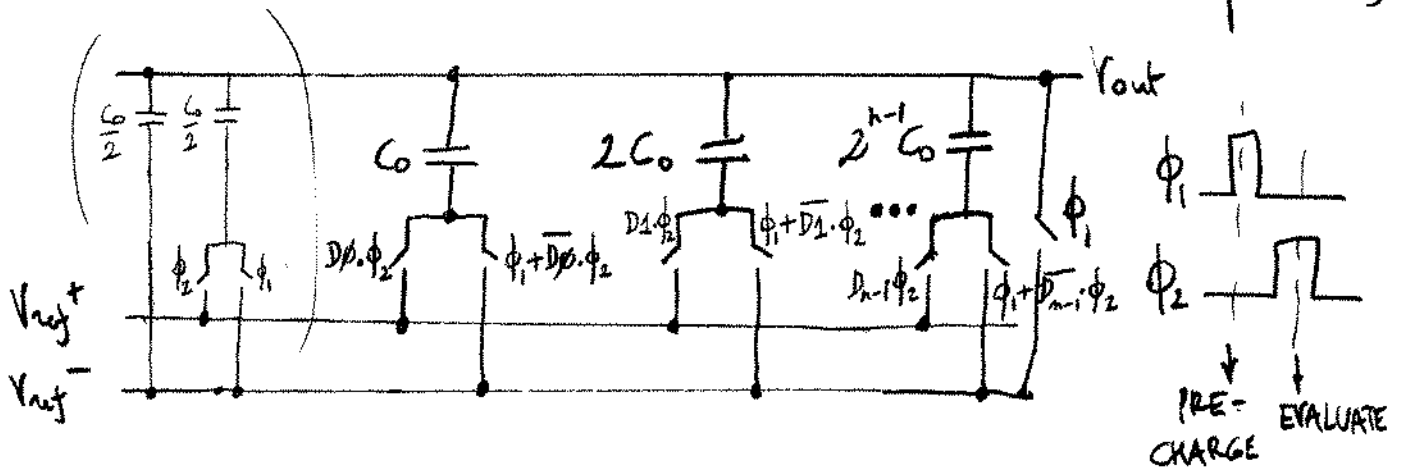

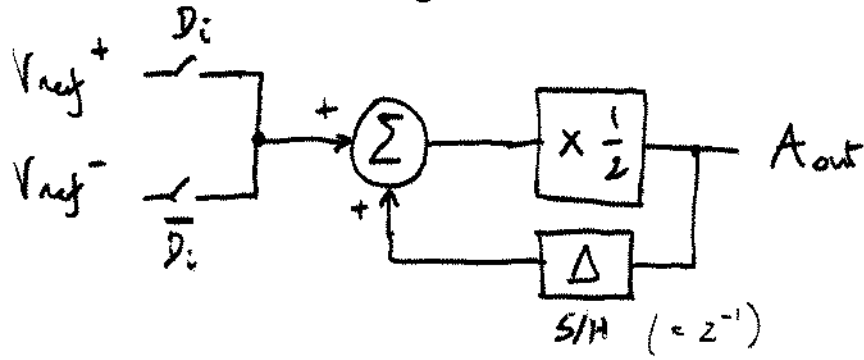2) BIT-SERIAL "algorithmic" D/A converter:  $D_i$  —  $D/A$  —  $A$  (sampled)



$\begin{cases} V_{ref}^- = "0" \\ V_{ref}^+ = "1" \end{cases}$


$$A_{out}(0) = \frac{1}{2}$$

$$A_{out}(1) = \frac{1}{2} \left( \frac{1}{2} + D_0 \right) = \frac{1}{4} + \frac{1}{2} D_0$$

$$A_{out}(2) = \frac{1}{2} \left( \left( \frac{1}{4} + \frac{1}{2} D_0 \right) + D_1 \right) = \frac{1}{8} + \frac{1}{4} D_0 + \frac{1}{2} D_1$$


⋮
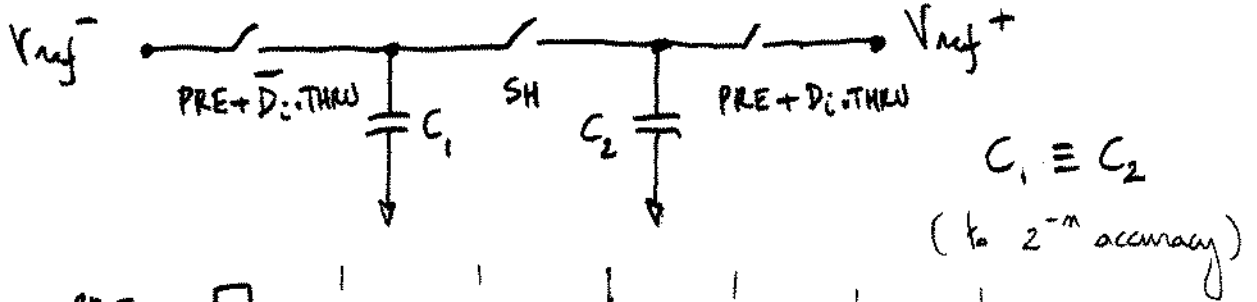
$$A_{out}(m) = \frac{1}{2} \left( \left( \frac{1}{2^n} + \frac{1}{2^{n-1}} D_0 + \frac{1}{2^{n-2}} D_1 + \dots \right) + D_{m-1} \right) = \frac{1}{2^{n+1}} + \sum_{i=0}^{n-1} 2^{i-n} D_i$$






3) PIPE LINED "algorithmic" D/A converter:  $\begin{matrix} D_0^{(i)} \\ D_1^{(i-1)} \\ \vdots \\ D_{m-1}^{(i-m+1)} \end{matrix}$  —  $D/A$  —  $A$


name:

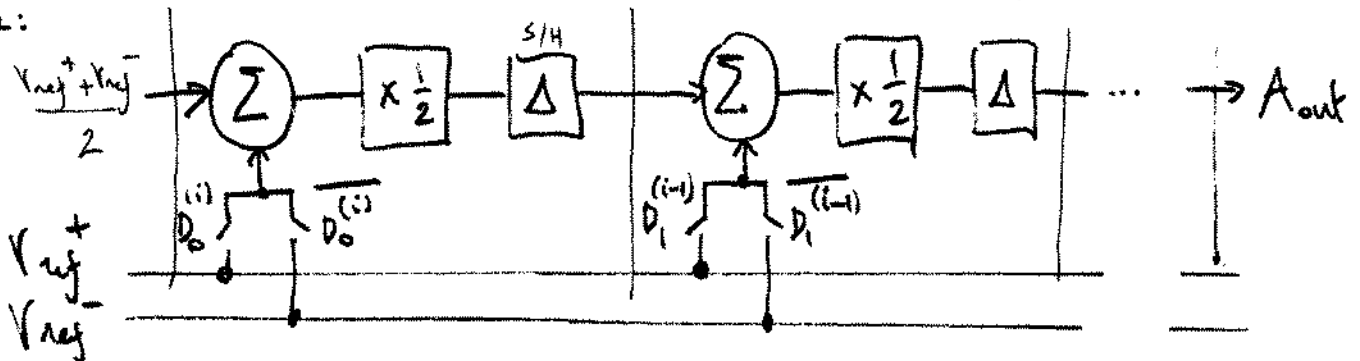



# A/D CONVERSION

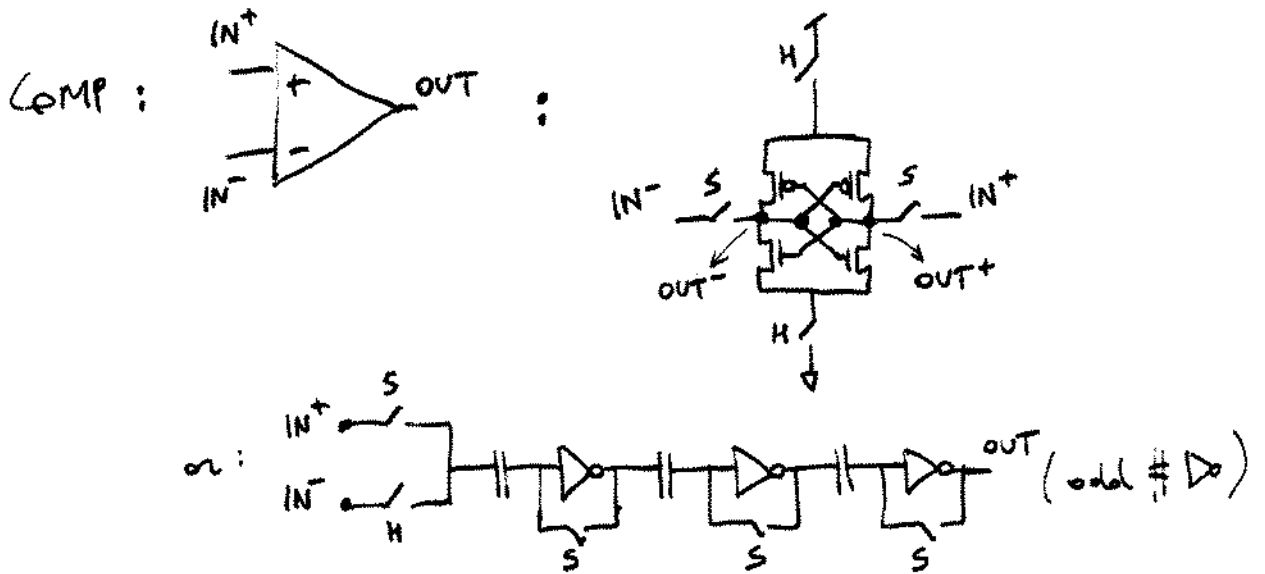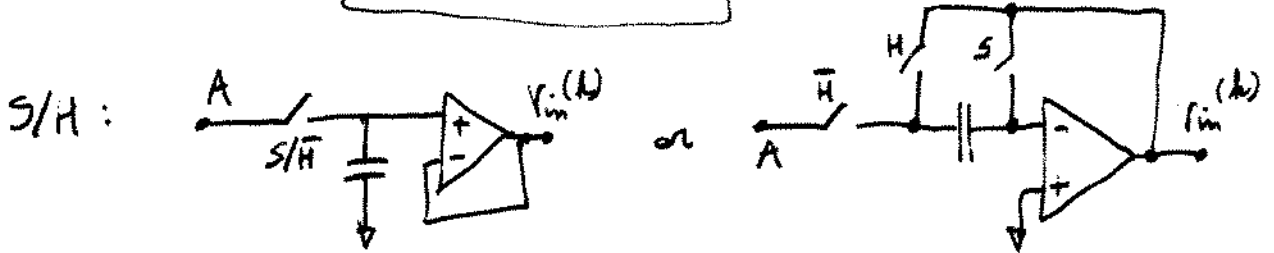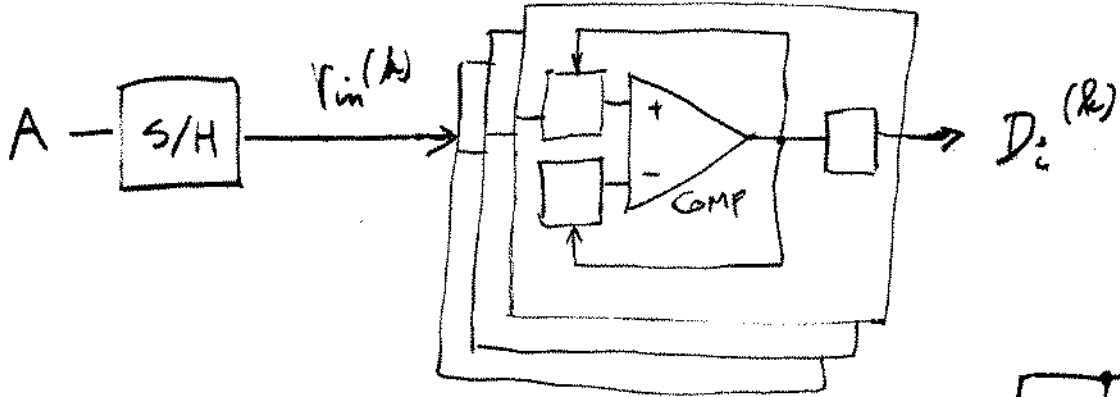

## 1) FLASH :

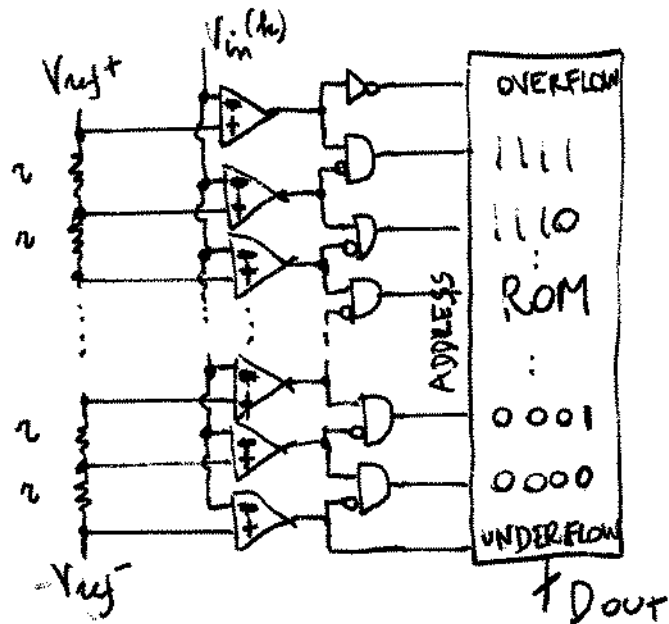

## 2) SUCCESSIVE APPROXIMATION

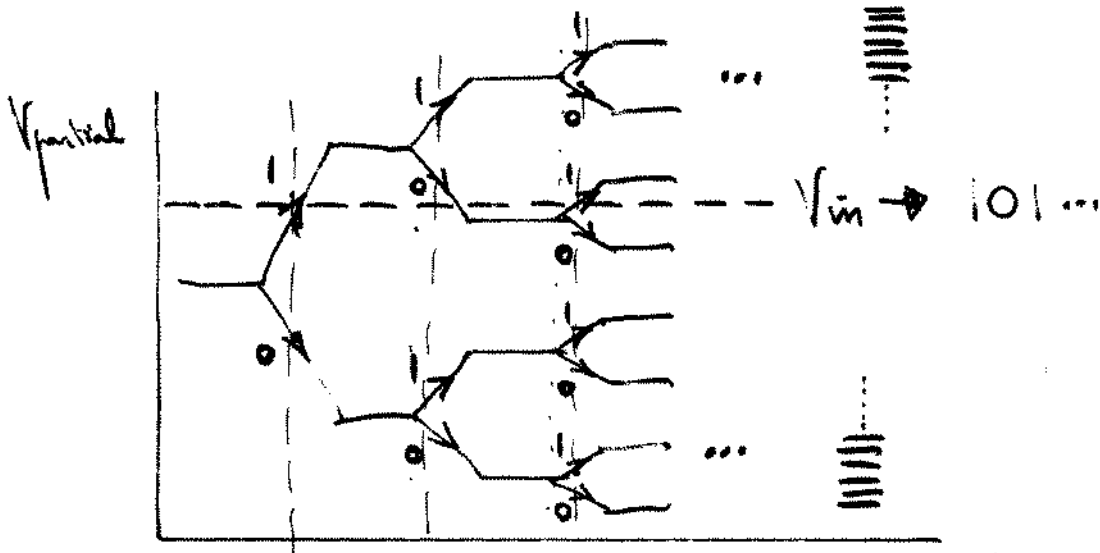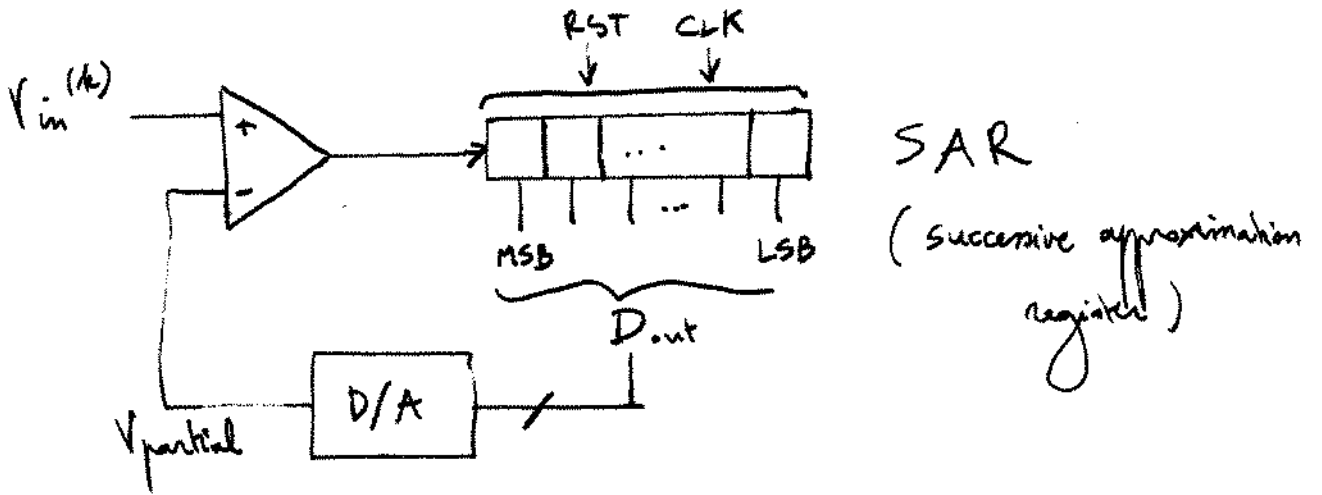


$$\begin{array}{ccccccc}
 \downarrow & D_{m-1} & \downarrow & D_{m-2} & \downarrow & D_{m-3} & \downarrow & \dots & \downarrow & D_0 \\
 \frac{1}{2} & \frac{1}{2}D_{m-1} & + & \frac{1}{4}D_{m-2} & + & \frac{1}{8}D_{m-3} & + & \dots & + & \frac{1}{2^n} \\
 & & & & & & & & & \sum_{i=0}^{n-1} 2^{-i} D_i
 \end{array}$$

### 3) ALGORITHMIC A/D CONVERTERS


$$D_i := (V_i^{int} > V_{ref})$$

with  $\begin{cases} V_0^{int} := V_{in} \\ V_{i+1}^{int} := 2(V_i^{int} - D_i \cdot V_{ref}) \end{cases}$


$$(V_{ref} = \frac{FS}{2})$$

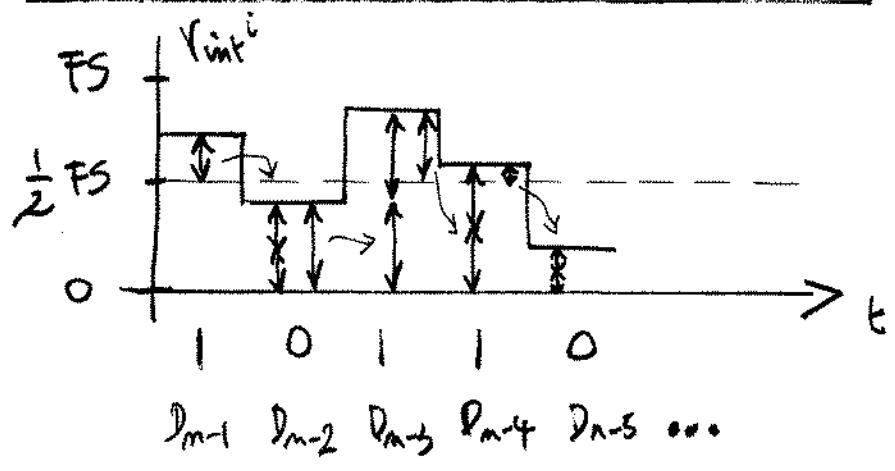

BIT-SERIAL:

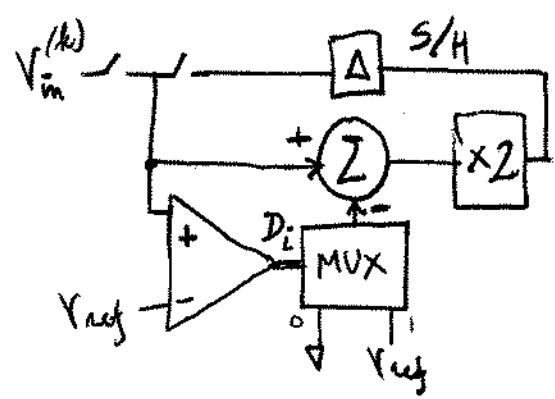



PIPELINED:

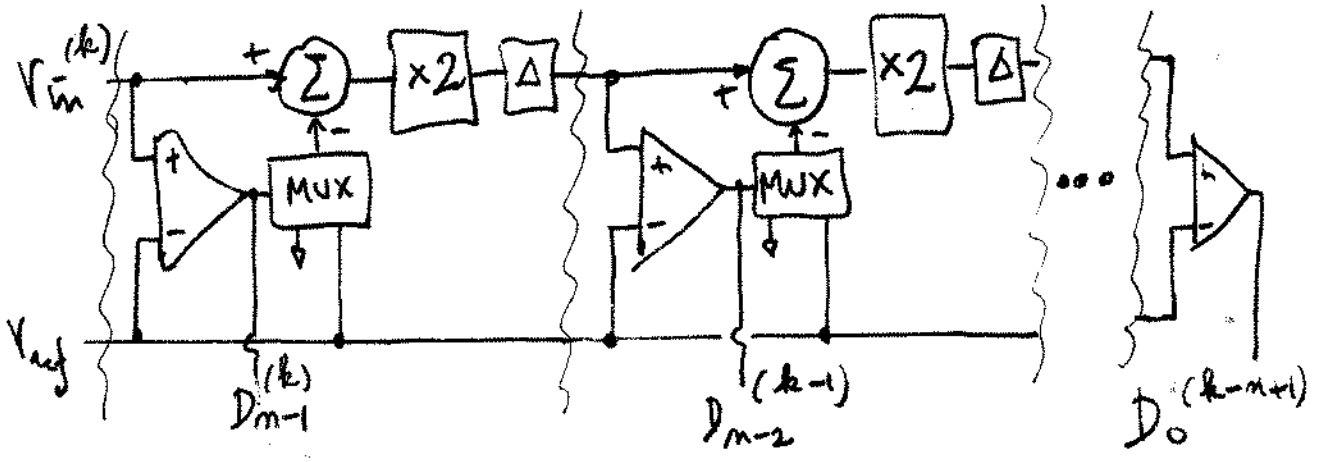





# 4) INTEGRATING

Single - Slope:

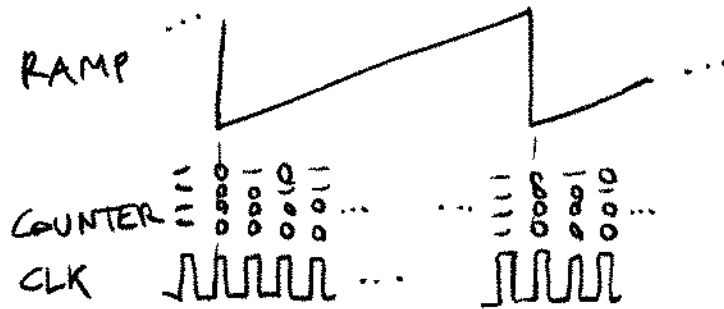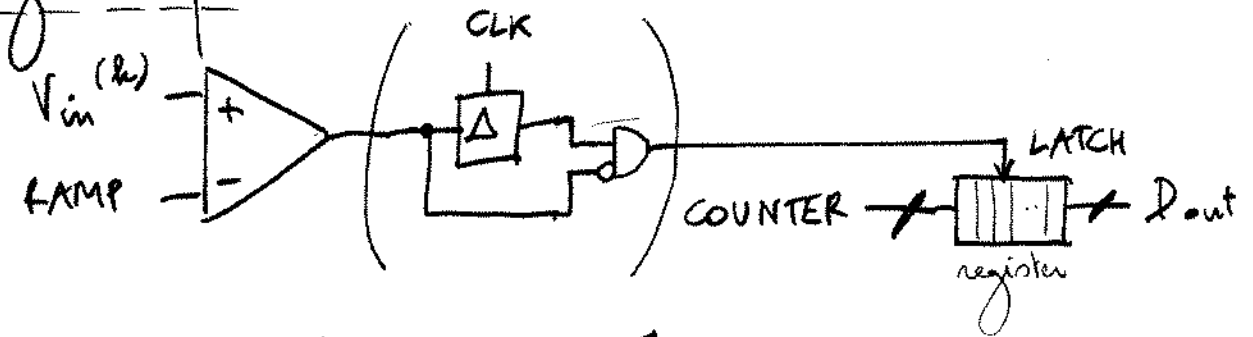

Dual - Slope:

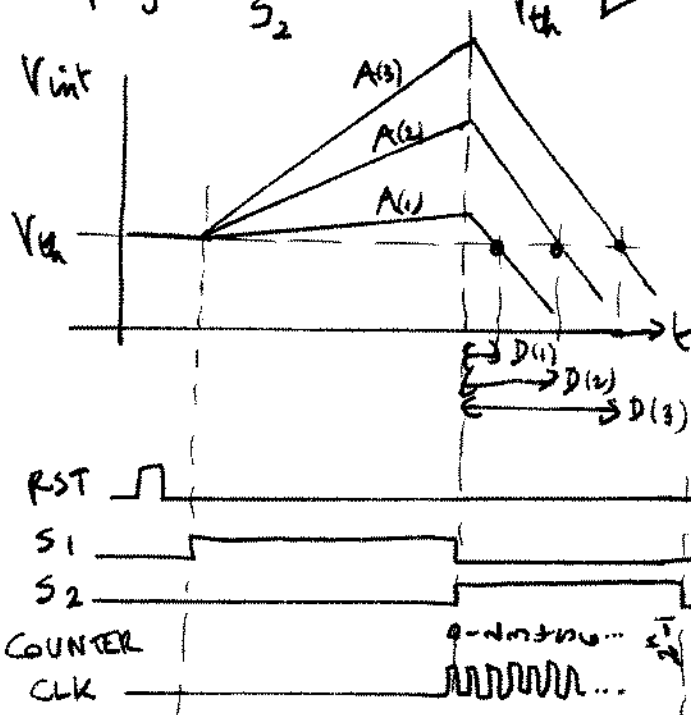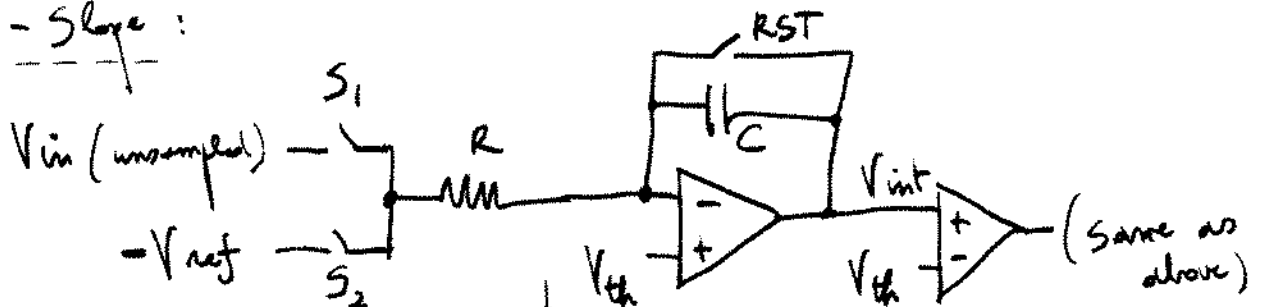

5) OVERSAMPLED (Sigma - Delta) → NEXT