

Wearable Airflow Monitor System

Seoye



Introduction

Problem Statement:

- Traditional methods for monitoring respiratory health are predominantly confined to clinical settings.
- Existing methods lack accessibility and convenience for continuous, everyday monitoring.

Introduction:


- Wearable Airflow Monitor System offers continuous tracking of respiratory patterns.
- Captures the pattern of breathing through sensor and interprets into understandable electrical signals, offering users insights into their health
- The system includes circuit that alters the input physiological signals to electric signal that is correlated with user's airflow



Assumptions

- The thermistor has a near-linear response within the temperature range of interest.
- Ambient temperature and humidity remain relatively constant.
- All electronic components (op-amps, resistors, capacitors) are ideal, with no intrinsic noise or offset.
- The temperature field around the thermistor is uniform, which means the thermistor's temperature is a good representation of the ambient or target temperature.
- The buffer op-amp (voltage follower) presents an infinite input impedance and zero output impedance, ensuring no loading effect on the Wheatstone bridge and subsequent stages.



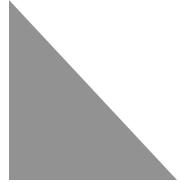

Sensor

TR91 Series Thermistor - utilized for detecting respiratory movements

- The resistance varies with temperature changes that occur with the user's inhalation and exhalation.
- Base setting: $10\text{k}\Omega$ at 25C (room temperature)
- Has high sensitivity
- Can be attached to the body in form of Chest Strap or Band, Adhesive Patches, etc.







Wheatstone Bridge

Wheatstone Bridge - detects minute changes in temperature through variations in the resistance of a thermistor

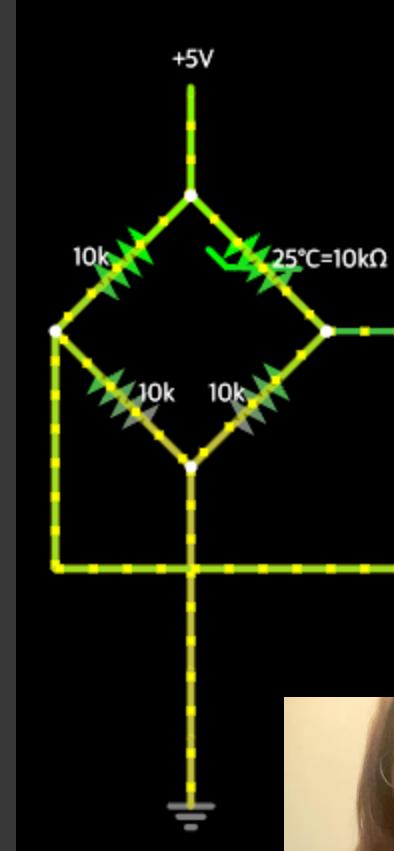- 3 Resistors, one thermistor as substitute of one resistive component
- Powered by power supplies




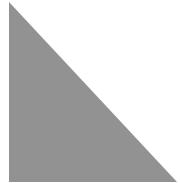


Op-Amp

Operation Amplifier - function as voltage follower

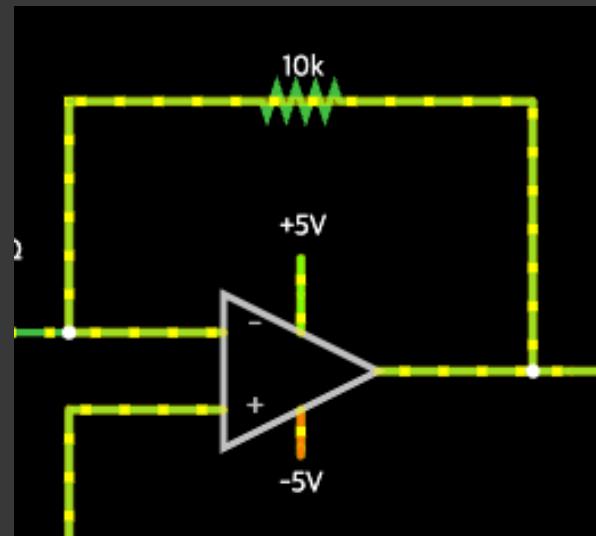- Ensures integrity of the voltage signal from the bridge is maintained
- Isolates the bridge voltage from the rest of the circuit, preventing possible load happening



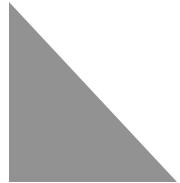



Bandpass Filter

Bandpass Filter - isolates the respiratory signals from unwanted noise and interference

Cutoff Frequency

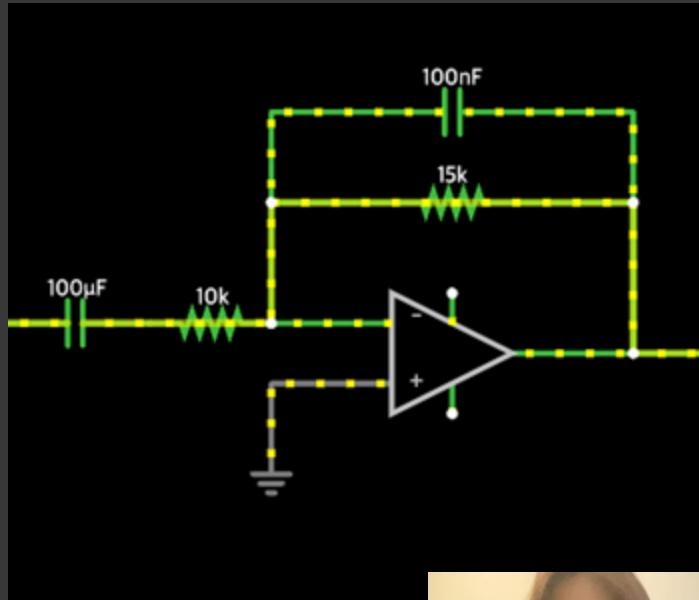- Low-Pass Filter
 - $fc = 1/2\pi RC = 1/(2\pi * 15k\Omega * 100nF) \approx 1.061\text{Hz}$
- High-Pass Filter
 - $fc = 1/2\pi RC = 1/(2\pi * 10k\Omega * 100\mu F) \approx 0.159\text{Hz}$
- Possible range: 0.159~106.1 Hz




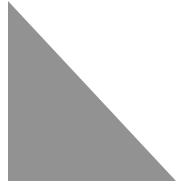

Buffer

Buffer- maintain signal integrity before outputting

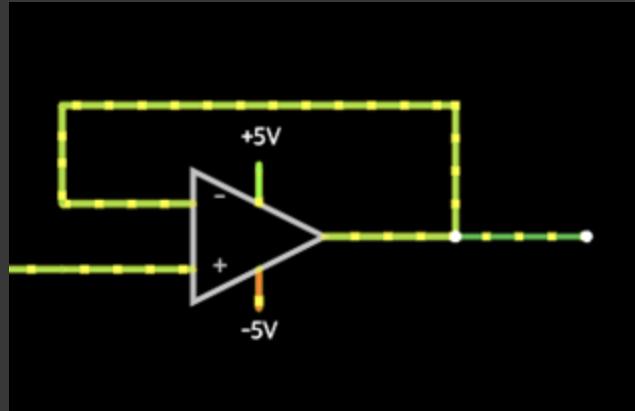
- High input impedance - avoid loading effects
- Low output impedance - drive the output voltage without signal loss



Other components

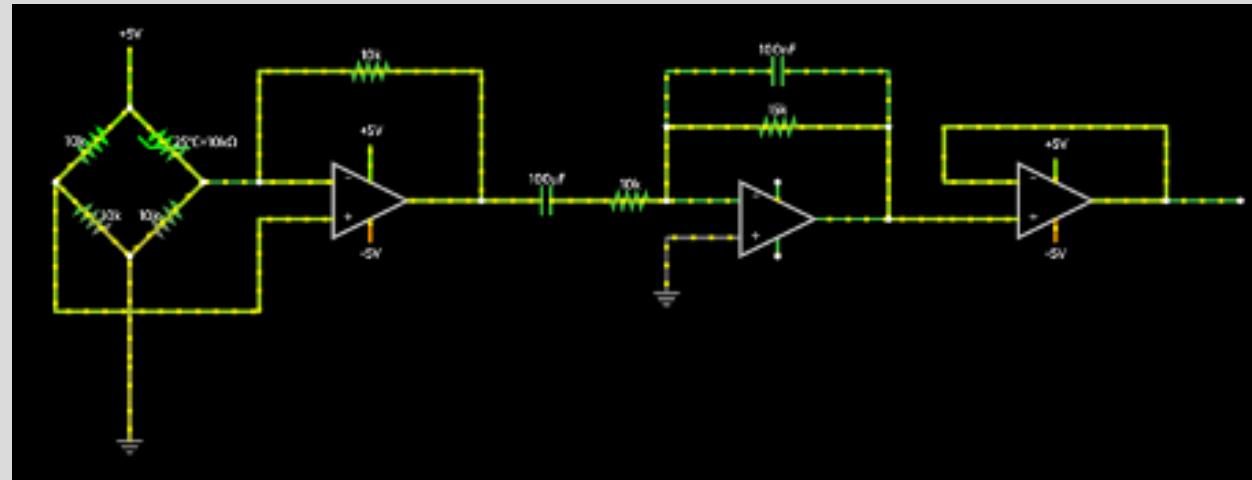- Power Supply
 - A 5V power supply was chosen to ensure broad compatibility.
- Resistors
 - $0\text{k}\Omega$ were chosen for resistors
 - Matching the resistance values of the thermistor and the other bridge resistors at the baseline temperature ensures that bridge operates within its optimal range.





Calculations

- Voltage Output
 - Wheatstone Bridge - Midpoint between two upper resistors and two lower resistors is +2.5V
 - Op-Amp - Act as voltage follower, Vout maintained to be 2.5V
 - Bandpass Filter - Unless AC input signal has frequency out of range of low and high pass cutoff, voltage output maintained to be 2.5V (2.496V with attenuation)

- If yes,

$$V_{out,bandpass} = V_{in} * A * \frac{f/f_1}{\sqrt{1 + (f/f_1)^2} * \sqrt{1 + (f/f_1)^2}}$$

- Buffer - has a unity gain, Vout maintained to be 2.5 (2.496V)





Results

Expected output under base thermistor setting (10k Ω at 25°C) = 2.496V

- By altering temperature reading from thermistor by the Falstad, the following graph outcomed



Above figure - V_{out} of the circuit vs. time.
Below figure – temperature (yellow) and voltage of the



Future Direction and Limitation

Future Direction

- An ADC can sample this V_{out} and convert it into a digital number that reflects the analog voltage magnitude.
- The digital signal output can be displayed in various forms, such as numerical Readout, Graphical Trend, or Alarms.

Limitation

- The thermistor has its thermal response time. This is the time taken for the thermistor to react to a temperature change.
- Thermistors will respond to all temperature variations within their environment, not just those caused by breathing.
- Airflow rate during inhalation and exhalation was not considered during calculation, may not reflect the actual outcome



References

- [1] Falstad, Paul. "Circuit Simulator Applet." Falstad.com, 2019, www.falstad.com/circuit/.
- [2] Nicolò, Andrea, et al. "The Importance of Respiratory Rate Monitoring: From Healthcare to Sport and Exercise." *Sensors*, vol. 20, no. 21, 9 Nov. 2020, pp. 1–46, www.ncbi.nlm.nih.gov/pmc/articles/PMC7665156/, <https://doi.org/10.3390/s20216396>.
- [3] "TR91 SERIES 10KOhm@25°C THERMISTOR SPECIFICATIONS." Mcshaneinc.com, mcshaneinc.com/html/TS91_Specs.html?NewWin. Accessed 21 Mar. 2024.



Thank you

