

# BENG 186B Winter 2019

## Quiz 1

Friday, January 25, 2019


*Name (Last, First):* \_\_\_\_\_

- This quiz is closed book and closed notes. You may use a calculator for algebra and arithmetic.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- Circle or box your final answers and show your work on the pages provided.
- There are 4 problems. Points for each problem are given in **[brackets]**. There are 100 points total.
- You have 50 minutes to complete this quiz.

1. [10 pts] Circle the **best answer (only one answer per question)**:

- (a) [2.5 pts] Biomedical instruments with closed-loop feedback require the processing pipeline to have:
- i. high throughput.
  - ii. low latency.
  - iii. discrete-time dynamics.
  - iv. all poles in the right-hand complex plane.
- (b) [2.5 pts] The Norton equivalent of an electrical circuit can be derived from:
- i. the open-circuit current and short-circuit voltage.
  - ii. the Thévenin equivalent.
  - iii. an equivalent current source in series with an impedance.
  - iv. all of the above.
- (c) [2.5 pts] A piezoelectric sensor transduces:
- i. stress to voltage.
  - ii. strain to charge.
  - iii. strain to voltage.
  - iv. all of the above.
- (d) [2.5 pts] A potentiometer is:
- i. a variable voltage divider.
  - ii. a voltage sensor.
  - iii. and instrument with zero output impedance.
  - iv. all of the above.

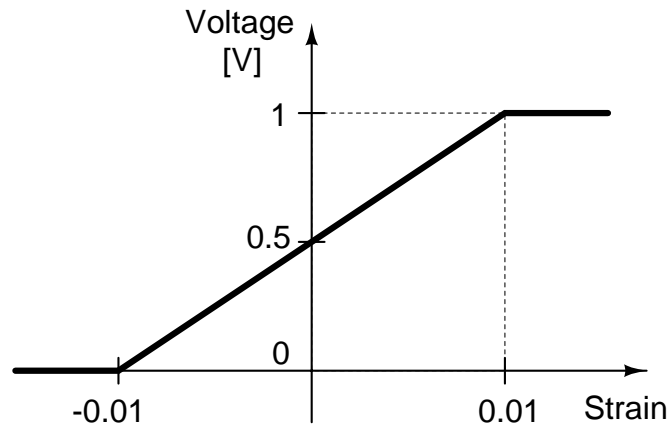2. **[30 pts]** You are given a biomedical instrument that measures strain and produces a digital reading on an output display. The instrument transduces the strain into a voltage, and digitizes this voltage by a 10-bit analog-to-digital converter (ADC). The transducer voltage as a function of strain is shown in the graph below, and the ADC full-scale voltage range is from 0 V to 1 V.




- (a) [5 pts] Find the sensitivity of the strain-to-voltage transducer, and the range of strain over which it operates.
- (b) [5 pts] Find the resolution of the instrument, and the range of strain over which it produces a valid digital reading.

(c) [10 pts] You discover that the transducer for known strain values produces a voltage that on average is 0.05V lower than expected, and with a standard deviation of 0.01V. Find the relative accuracy and precision of the instrument.

(d) [10 pts] Now you are given two identical copies of the instrument. Describe how you would use these two to construct a better instrument that produces a consistent zero reading for zero strain independent of temperature and other environmental variations.

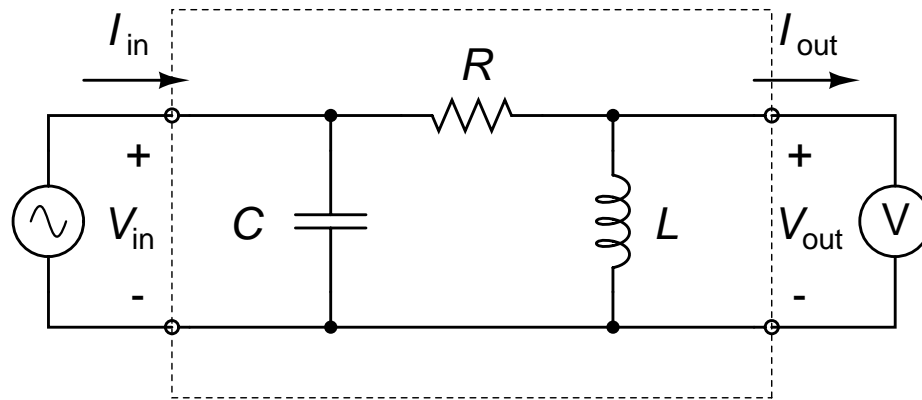3. [35 pts] Consider the voltage-input, voltage-output filter circuit below.




(a) [10 pts] Find the input impedance  $Z_{in}(j\omega)$ .

(b) [5 pts] Find the output impedance  $Z_{out}(j\omega)$ .


(c) [5 pts] Find the transfer function  $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$ .

- (d) [15 pts] Sketch the Bode plot of the transfer function  $H(j\omega)$  for  $C = 10$  nF,  $R = 10$  k $\Omega$ , and  $L = 10$   $\mu$ H. Be sure to label the axes and indicate the units (rad/s, dB, and degrees).


$H(j\omega)$  Magnitude

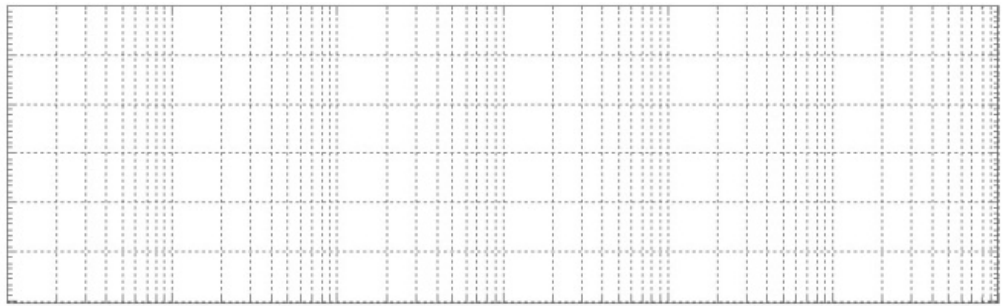

$H(j\omega)$  Phase

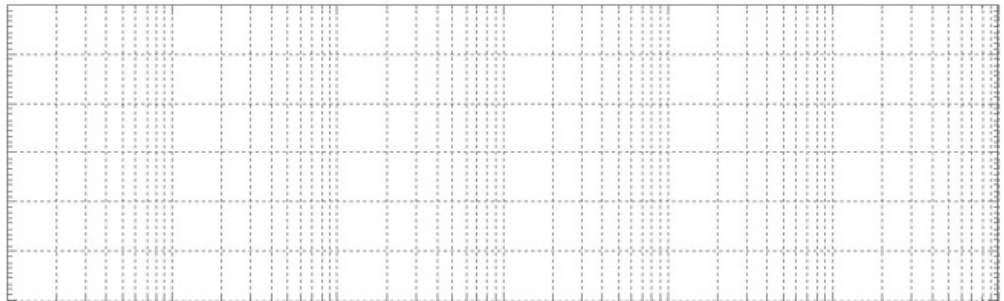

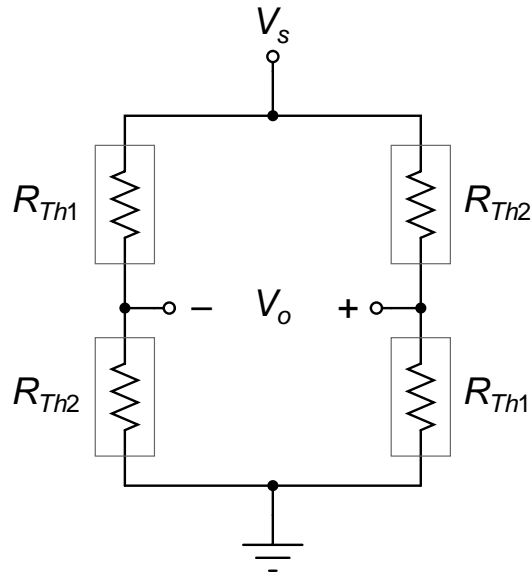4. [25 pts] Consider the temperature-to-voltage transducer shown below, with constant supply voltage and two pairs of identical thermistors  $R_{Th1}$  and  $R_{Th2}$ .



$$R_{Th1} = R_{nom1} (1 + \alpha_1 T)$$

$$R_{Th2} = R_{nom2} (1 + \alpha_2 T)$$

- (a) [10 pts] Find the output voltage  $V_o$  as a function of temperature  $T$ , supply voltage  $V_s$ , nominal resistances  $R_{nom1}$  and  $R_{nom2}$ , and temperature coefficients  $\alpha_1$  and  $\alpha_2$ .

- (b) [15 pts] Show that if  $R_{nom1}\alpha_1 + R_{nom2}\alpha_2 = 0$  the transducer is linear. Find its sensitivity  $S$ , and offset temperature  $T_{off}$  at which the output voltage is zero.