

BENG 186B Winter 2019

Quiz 1

Friday, January 25, 2019


Name (Last, First): SOLUTIONS

- This quiz is closed book and closed notes. You may use a calculator for algebra and arithmetic.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- Circle or box your final answers and show your work on the pages provided.
- There are 4 problems. Points for each problem are given in **[brackets]**. There are 100 points total.
- You have 50 minutes to complete this quiz.

1. [10 pts] Circle the best answer (only one answer per question):

- (a) [2.5 pts] Biomedical instruments with closed-loop feedback require the processing pipeline to have:
- i. high throughput.
 - ii. low latency.
 - iii. discrete-time dynamics.
 - iv. all poles in the right-hand complex plane.
- (b) [2.5 pts] The Norton equivalent of an electrical circuit can be derived from:
- i. the open-circuit current and short-circuit voltage.
 - ii. the Thévenin equivalent.
 - iii. an equivalent current source in series with an impedance.
 - iv. all of the above.
- (c) [2.5 pts] A piezoelectric sensor transduces:
- i. stress to voltage.
 - ii. strain to charge.
 - iii. strain to voltage.
 - iv. all of the above.
- (d) [2.5 pts] A potentiometer is:
- i. a variable voltage divider.
 - ii. a voltage sensor.
 - iii. an instrument with zero output impedance.
 - iv. all of the above.

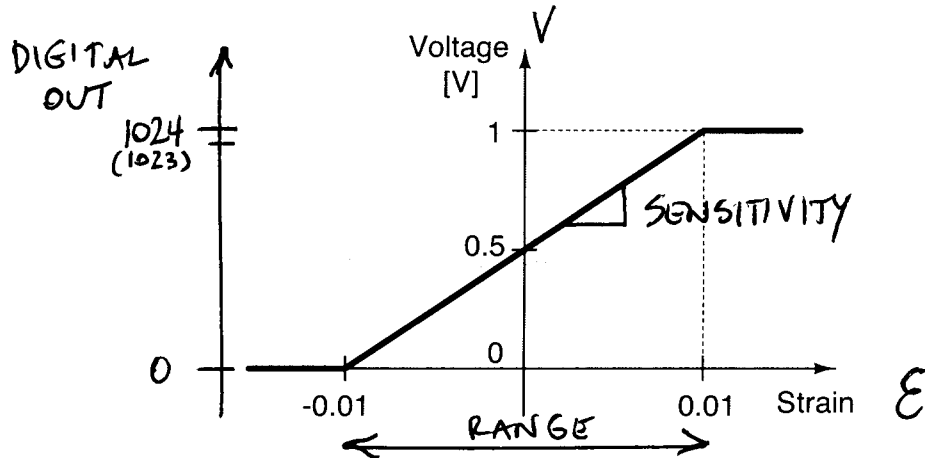2. [30 pts] You are given a biomedical instrument that measures strain and produces a digital reading on an output display. The instrument transduces the strain into a voltage, and digitizes this voltage by a 10-bit analog-to-digital converter (ADC). The transducer voltage as a function of strain is shown in the graph below, and the ADC full-scale voltage range is from 0 V to 1 V.



- (a) [5 pts] Find the sensitivity of the strain-to-voltage transducer, and the range of strain over which it operates.

$$\text{Sensitivity} : S = \frac{dV}{d\epsilon} = \frac{1V}{0.02} = 50 V$$

$$\text{Range} : [-0.01, 0.01] \quad (0.02)$$

- (b) [5 pts] Find the resolution of the instrument, and the range of strain over which it produces a valid digital reading.

$$\text{Resolution} : \frac{\text{Range}}{2^{10}} = \frac{0.02}{1024} = 2 \times 10^{-5}$$

$$\text{Same Range} \quad [-0.01, 0.01] \quad (0.02)$$

- (c) [10 pts] You discover that the transducer for known strain values produces a voltage that on average is 0.05V lower than expected, and with a standard deviation of 0.01V. Find the relative accuracy and precision of the instrument.

Absolute:

$$\text{Accuracy} = \text{True} - \text{Mean} = \frac{0.05V}{S} = 0.001$$

$$\text{Precision} = \text{St. Dev.} = \frac{0.01V}{S} = 0.0002$$

Relative, to full scale:

$$\text{Accuracy} = \frac{\text{True} - \text{Mean}}{\text{Range}} = \frac{0.05V}{1V} = 5\%$$


$$\text{Precision} = \frac{\text{St. Dev.}}{\text{Range}} = \frac{0.01V}{1V} = 1\%$$

- (d) [10 pts] Now you are given two identical copies of the instrument. Describe how you would use these two to construct a better instrument that produces a consistent zero reading for zero strain independent of temperature and other environmental variations.


Subject the first copy to the strain at the input; subject the second copy to zero strain (no input connection)^(*); and subtract the two digital readings to produce the output.

(*) OR: the opposing strain, if available

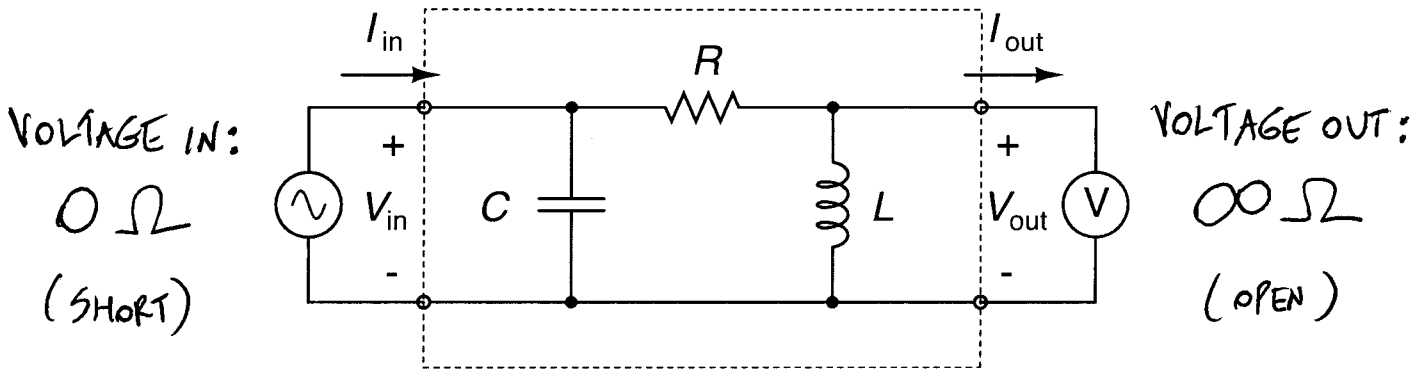3. [35 pts] Consider the voltage-input, voltage-output filter circuit below.



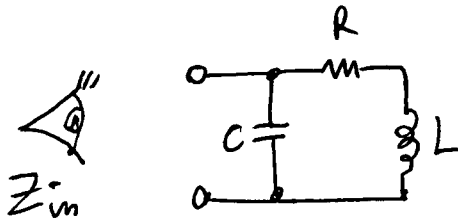(a) [10 pts] Find the input impedance $Z_{in}(j\omega)$.




$$Z_{in}(j\omega) = \frac{1}{j\omega C} \parallel (R + j\omega L)$$

$$= \frac{1}{j\omega C + \frac{1}{R + j\omega L}} = \frac{R + j\omega L}{(R + j\omega L)j\omega C + 1}$$


$$= \frac{R + j\omega L}{1 + j\omega RC - \omega^2 LC}$$

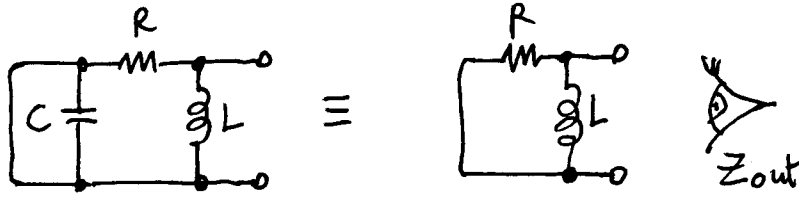(b) [5 pts] Find the output impedance $Z_{out}(j\omega)$.



$$\begin{aligned}
 Z_{out}(j\omega) &= j\omega L \parallel R \\
 &= \frac{1}{\frac{1}{j\omega L} + \frac{1}{R}} \\
 &= \frac{j\omega L}{1 + j\omega \frac{L}{R}}
 \end{aligned}$$

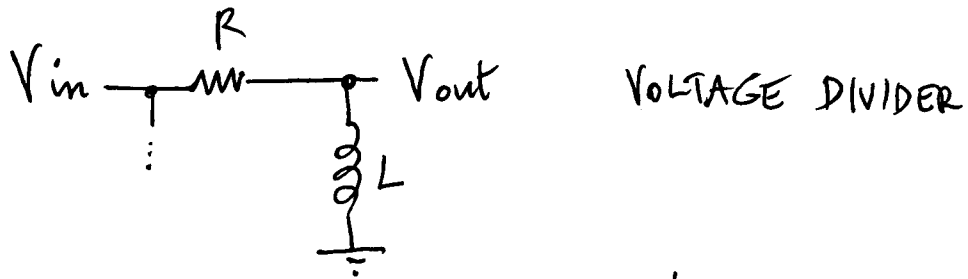(c) [5 pts] Find the transfer function $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$.




$$H(j\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega \frac{L}{R}}{1 + j\omega \frac{L}{R}}$$

(d):

ZERO @ $s = 0$

POLE @ $s = -\frac{R}{L}$

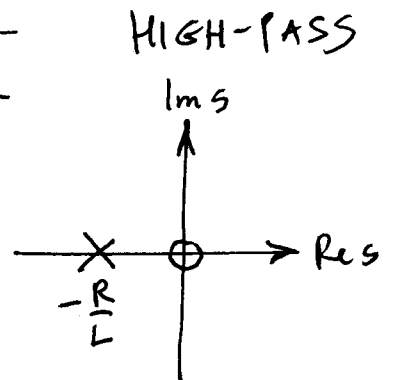


- (d) [15 pts] Sketch the Bode plot of the transfer function $H(j\omega)$ for $C = 10$ nF, $R = 10$ k Ω , and $L = 10$ μ H. Be sure to label the axes and indicate the units (rad/s, dB, and degrees).


HIGH-PASS with ?

$$\text{cut-off frequency: } \omega_c = \frac{R}{L} = \frac{10 \text{ k}\Omega}{10 \mu\text{H}} = 10^9 \frac{\text{rad}}{\text{s}}$$

$$\text{in-band gain: } |H(\omega)| = 1 \quad (0 \text{ dB})$$

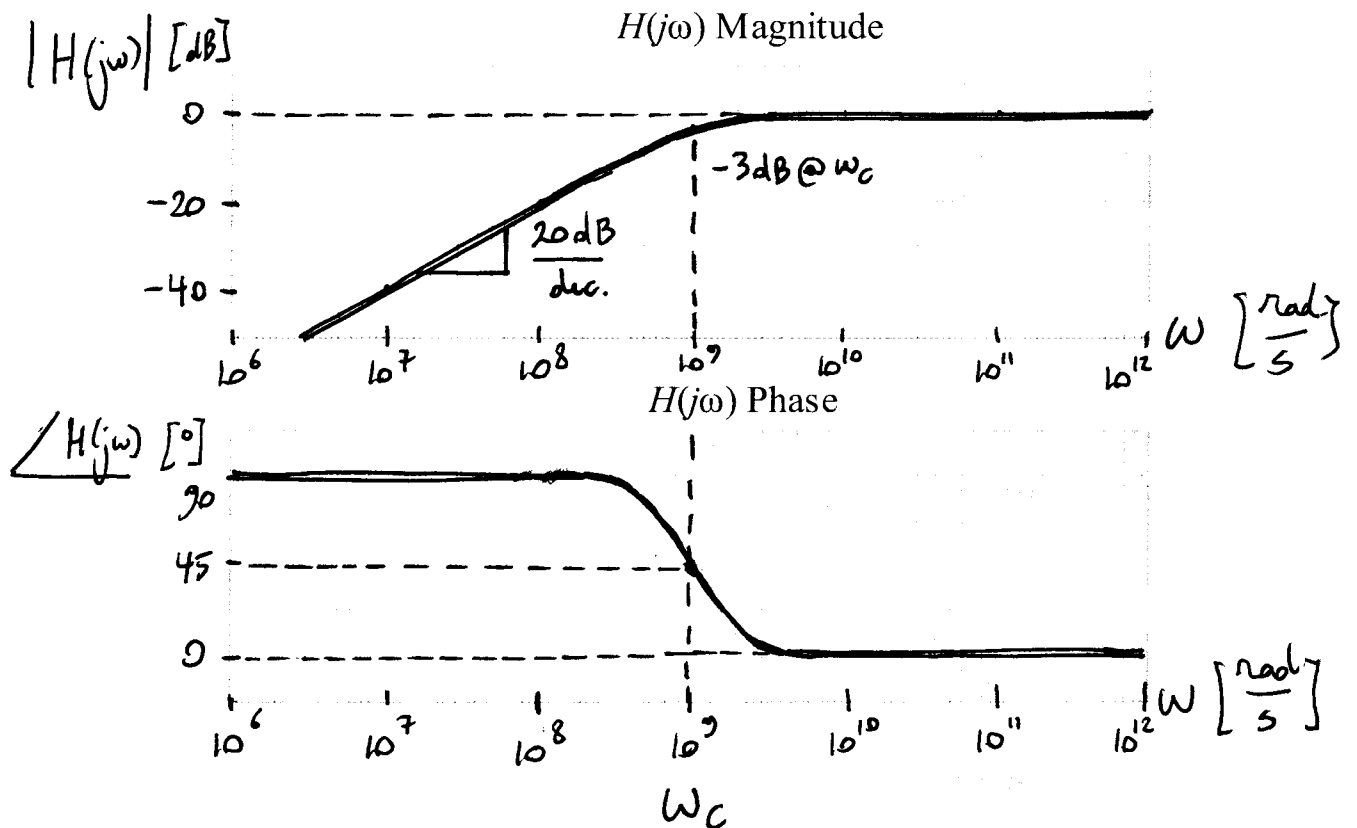

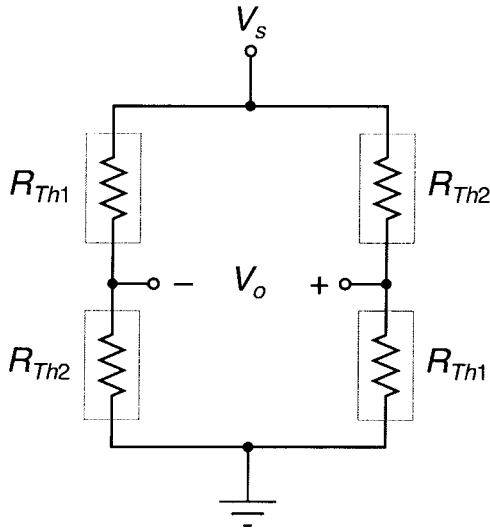4. [25 pts] Consider the temperature-to-voltage transducer shown below, with constant supply voltage and two pairs of identical thermistors R_{Th1} and R_{Th2} .



$$R_{Th1} = R_{nom1} (1 + \alpha_1 T)$$

$$R_{Th2} = R_{nom2} (1 + \alpha_2 T)$$

- (a) [10 pts] Find the output voltage V_o as a function of temperature T , supply voltage V_s , nominal resistances R_{nom1} and R_{nom2} , and temperature coefficients α_1 and α_2 .

$$V_o = \left(\frac{R_{Th1}}{R_{Th1} + R_{Th2}} - \frac{R_{Th2}}{R_{Th1} + R_{Th2}} \right) V_s$$

$$= \frac{R_{Th1} - R_{Th2}}{R_{Th1} + R_{Th2}} V_s$$

$$= \frac{(R_{nom1} - R_{nom2}) + (R_{nom1} \alpha_1 - R_{nom2} \alpha_2) T}{(R_{nom1} + R_{nom2}) + (R_{nom1} \alpha_1 + R_{nom2} \alpha_2) T} V_s$$

- (b) [15 pts] Show that if $R_{nom1}\alpha_1 + R_{nom2}\alpha_2 = 0$ the transducer is linear. Find its sensitivity S , and offset temperature T_{off} at which the output voltage is zero.

$$R_{nom1}\alpha_1 + R_{nom2}\alpha_2 = 0 \Rightarrow$$

$$V_o = \frac{V_s}{R_{nom1} + R_{nom2}} \left((R_{nom1} - R_{nom2}) + (R_{nom1}\alpha_1 - R_{nom2}\alpha_2)T \right)$$

LINEAR in T

$$\text{Sensitivity } S = \frac{dV_o}{dT} = \frac{R_{nom1}\alpha_1 - R_{nom2}\alpha_2}{R_{nom1} + R_{nom2}} V_s$$

Offset T_{off} such that $(R_{nom1} - R_{nom2}) + (R_{nom1}\alpha_1 - R_{nom2}\alpha_2)T_{off} = 0$

$$\Rightarrow T_{off} = - \frac{R_{nom1} - R_{nom2}}{R_{nom1}\alpha_1 - R_{nom2}\alpha_2}$$