

BENG 186B Winter 2020

Quiz 1

Friday, January 24, 2020


Name (Last, First): _____

- This quiz is closed book and closed notes. You may use a calculator for algebra and arithmetic.
- Do not attach separate sheets. If you need more space, use the back of the pages.
- Circle or box your final answers and show your work on the pages provided.
- There are 3 problems. Points for each problem are given in **[brackets]**. There are 100 points total.
- The quiz takes 50 minutes to complete.

1. [15 pts] Circle the **best answer (only one answer per question)**:

- (a) [3 pts] Averaging readings from multiple measurements of the same measurement improves its:
- sensitivity.
 - accuracy.
 - precision.
 - none of the above.
- (b) [3 pts] The transfer function of an underdamped ($\zeta < 1$) second-order low-pass filter has:
- two complex conjugate poles.
 - two identical real poles.
 - two different real poles.
 - one real pole and one imaginary pole.
- (c) [3 pts] Measuring the open-circuit voltage and short-circuit current of a circuit element determines its:
- Thévenin equivalent.
 - Norton equivalent.
 - equivalent impedance.
 - all of the above.
- (d) [3 pts] The sensitivity of a piezoresistive stress transducer depends on the:
- gauge factor.
 - Young's modulus.
 - nominal resistance.
 - all of the above.
- (e) [3 pts] The sensitivity of a capacitive displacement transducer can be improved by:
- decreasing the area of the two plates
 - decreasing the distance between the two plates.
 - lowering the dielectric constant of the insulator between the plates.
 - all of the above.

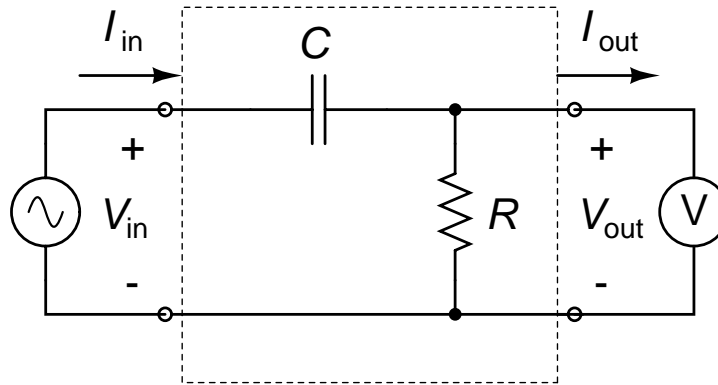2. [45 pts] Consider the voltage-input, voltage-output filter circuit below.




(a) [5 pts] Find the input impedance $Z_{in}(j\omega)$.

(b) [10 pts] Find the output impedance $Z_{out}(j\omega)$.

- (c) [10 pts] Find the transfer function $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$.
- (d) [10 pts] Sketch the Bode plot of the transfer function $H(j\omega)$ for $C = 100$ nF and $R = 100$ k Ω . Be sure to label the axes and indicate the units (*e.g.*, rad/s, dB, and degrees). What type of filter is this?

- (e) [10 pts] Sketch the Bode plot of the input impedance $Z_{in}(j\omega)$ for the same values of C and R as in (d). Again be sure to label the axes and indicate the units (*e.g.*, rad/s, dB Ω , and degrees).

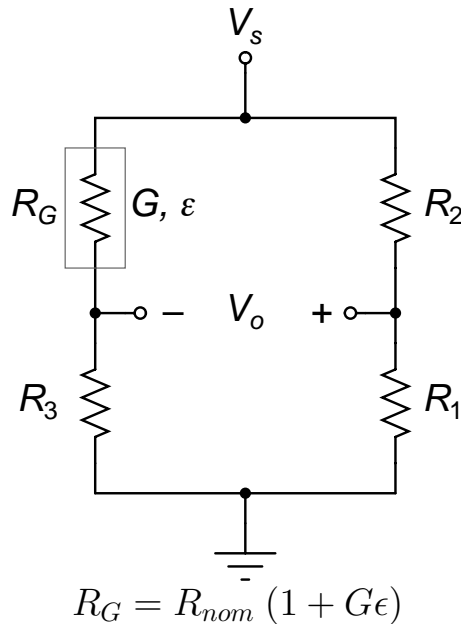3. [40 pts] Consider the strain transducer below, with constant supply voltage $V_s = 1$ V, three resistors with identical resistances $R_1 = R_2 = R_3 = R$, and a strain gauge R_G with nominal resistance $R_{nom} = 100$ k Ω and gauge factor $G = 100$. The transducer produces a differential output voltage V_o in response to a strain ϵ applied to the strain gauge.



- (a) [10 pts] Find the value of resistance R that maximizes the sensitivity of the transducer. Find this maximum sensitivity. *Hint*: you may assume that the applied strain is sufficiently small in magnitude so that $|G\epsilon| \ll 1$.

(b) [5 pts] Find the offset of the transducer.

(c) [10 pts] Due to mismatch in manufacturing, the actual R_1 is 1% smaller than expected, and the actual R_2 is 1% larger than expected. Find the accuracy of the strain measurement.

(d) [10 pts] An 8-bit analog-to-digital converter (ADC) is used to digitize the voltage output V_o for a digital reading of the strain ϵ . The full-scale voltage range of the ADC is from 0.4 V to 0.6 V. Find the resolution of the strain measurement.

- (e) [5 pts] You observe that the transducer is sensitive to temperature. What simple change could you make to the design to eliminate this temperature dependence? *Hint:* you may assume that all resistances R have identical temperature coefficient, and also that strain gauge nominal resistances have identical temperature coefficient, but these two are different.