

# BENG 186B Winter 2022

## Quiz 1

Friday, January 21, 2022

Name (Last, First): SOLUTIONS

- This quiz is on-line, open-book, and open-notes, but web search is prohibited. You may follow electronic links from Canvas or the class web pages, but not any further. **No collaboration or communication in any form is allowed**, except for questions to the instructor and TAs.
- The quiz is due January 21, 2022 at 11:59pm, over Canvas Gradescope. It should approximately take 2 hours to complete, but there is no time limit other than the submission deadline. Do not discuss any class-related topics among yourselves before or after you have completed your quiz, and until the submission deadline has passed.
- There are 3 problems. Points for each problem are given in **[brackets]**. There are 100 points total.

1. [15 pts] Circle the best answer (only one answer per question):

(a) [3 pts] Precision of a bioinstrument can be improved by:

- i. lowering the measurement noise.
- ii. averaging multiple readings.
- iii. increasing the signal amplitude at its input.
- iv. all of the above.

(b) [3 pts] To accurately digitize a 1 kHz bandwidth biosignal the sampling rate needs to be at least:

- i. 500 samples per second.
- ii. 1,000 samples per second.
- iii. 2,000 samples per second.
- iv. Whatever, it doesn't matter.

(c) [3 pts] Cascading two first-order lowpass filter sections with different cut-off frequencies produces a second-order lowpass filter that is:

- i. underdamped.
- ii. critically damped.
- iii. overdamped. *(two real, different poles)*
- iv. none of the above.


(d) [3 pts] A thermistor is a resistor with a temperature coefficient that is:

- i. always positive.
- ii. relatively large.
- iii. temperature independent.
- iv. all of the above.


(e) [3 pts] The sensitivity of an inductive displacement transducer can be improved by:

- i. choosing a core with larger magnetic permeability  $\mu$ .
- ii. lowering the number of windings in the coil.
- iii. bringing a permanent magnet in close proximity.
- iv. all of the above.

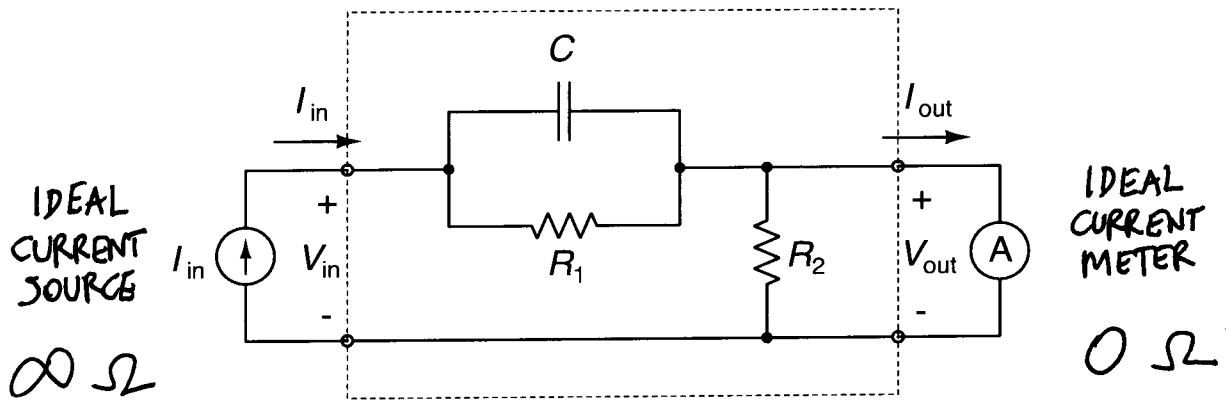2. [40 pts] Consider the *current-input, current-output* filter circuit below. You may assume an ideal current source for  $I_{in}$ , and an ideal ammeter for  $I_{out}$ .




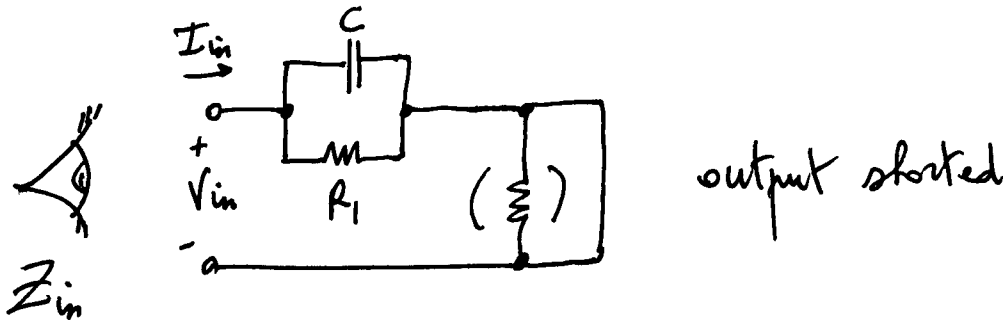- (a) [10 pts] Find the input impedance  $Z_{in}(j\omega)$ .




$$Z_{in} = \frac{1}{j\omega C} \parallel R_1 = \frac{\frac{1}{j\omega C} \cdot R_1}{\frac{1}{j\omega C} + R_1} = \frac{R_1}{1 + j\omega R_1 C}$$

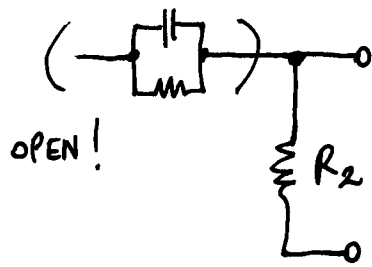(b) [10 pts] Find the output impedance  $Z_{out}(j\omega)$ .



$$Z_{out} = R_2$$

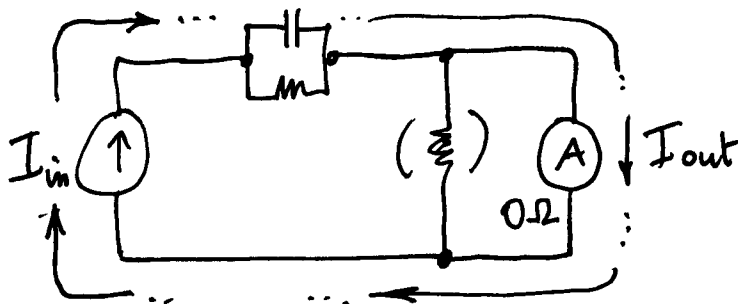(c) [10 pts] Find the transfer function  $H(j\omega) = I_{out}(j\omega) / I_{in}(j\omega)$ . What are the units? Does it depend on frequency?



Current flows through the path of least resistance:  $0 \Omega$


$$\Rightarrow I_{out} = I_{in} \Rightarrow H(j\omega) = 1$$

Dimensionless & Constant over frequency


- (d) [10 pts] Sketch the Bode plot of the input impedance  $Z_{in}(j\omega)$  for  $C = 10$  nF,  $R_1 = 100$  k $\Omega$ , and  $R_2 = 1$  M $\Omega$ . Be sure to label the axes and indicate the units (e.g., rad/s, dB $\Omega$ , and degrees).

$$Z_{in}(j\omega) = \frac{R_1}{1 + j\omega R_1 C} \quad : \quad 1 \text{ pole @ } s = j\omega = -\frac{1}{R_1 C}$$

$$= -10^3 \frac{\text{rad}}{\text{s}}$$

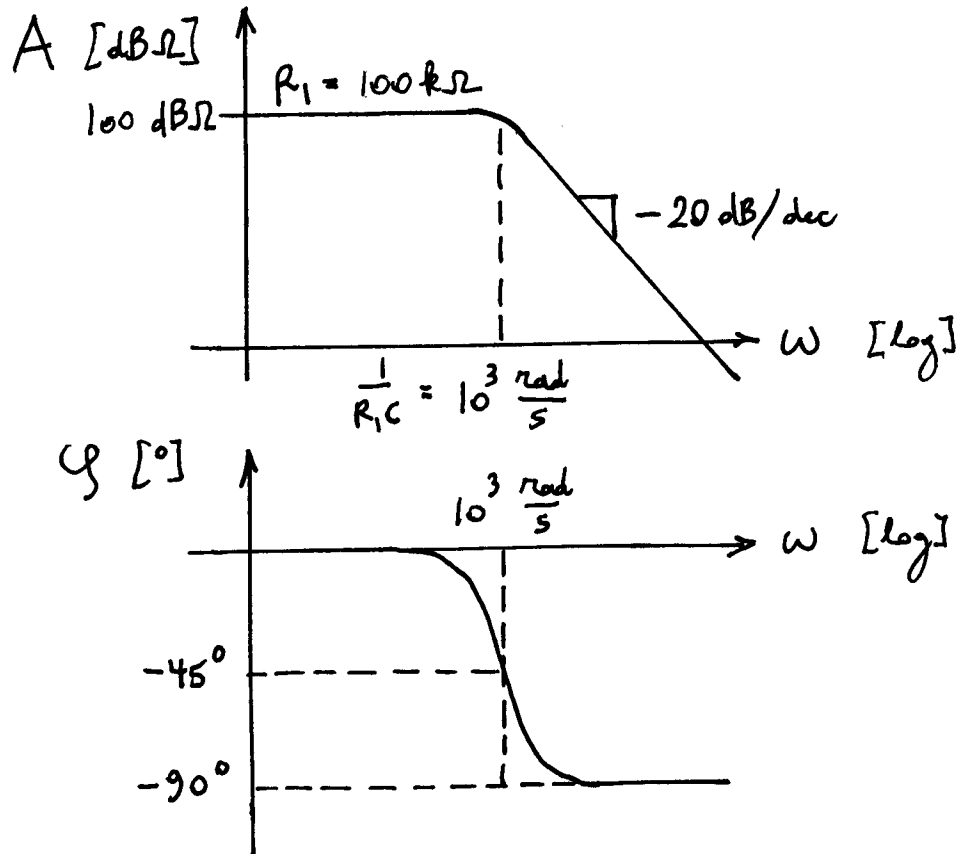

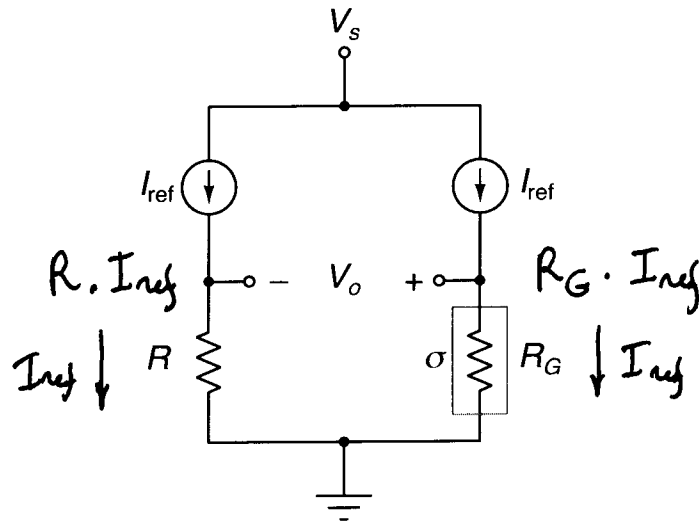3. [45 pts] Consider the stress transducer below, with constant supply voltage  $V_s = 3$  V, two identical current sources  $I_{ref} = 10 \mu\text{A}$ , a resistor  $R$ , and a strain gauge  $R_G$  with nominal resistance  $R_{nom} = 100 \text{ k}\Omega$ , gauge factor  $G = 100$ , and Young's modulus  $E = 100 \text{ kPa}$ . The transducer produces a differential output voltage  $V_o$  in response to a stress  $\sigma$  applied to the strain gauge.



$$R_G = R_{nom} (1 + G \epsilon)$$

$$\sigma = E \epsilon$$

- (a) [10 pts] Find the output voltage  $V_o$  as a function of the applied stress  $\sigma$ . Does it depend on the supply voltage, and why?

$$V_o = R_G \cdot I_{ref} - R \cdot I_{ref}$$

$$= R_{nom} \left(1 + \frac{G}{E} \sigma\right) I_{ref} - R \cdot I_{ref}$$

INDEPENDENT of supply voltage  $V_s$   
for ideal current sources  $I_{ref}$

$$V_o = \underbrace{(R_{nom} - R) \cdot I_{ref}}_{V_{off}} + \underbrace{R_{nom} \cdot I_{ref} \cdot \frac{G}{E}}_S \cdot \delta$$

OFFSET
SENSITIVITY

3(b)
3(c)

- (b) [5 pts] Find the value of resistance  $R$  that nulls the offset of the transducer.  
Use this value of  $R$  for the remainder of this problem.

3(a):  $V_{off} = 0$  for  $R = R_{nom} = 100 \text{ k}\Omega$

- (c) [5 pts] Find the sensitivity of the transducer.

3(a):  $S = R_{nom} \cdot I_{ref} \cdot \frac{G}{E} = 100 \text{ k}\Omega \cdot 10 \mu\text{A} \cdot \frac{100}{100 \text{ kPa}}$

$= 1 \text{ V/kPa}$

- (d) [10 pts] Due to mismatch in manufacturing of the instrument, the left current source  $I_{ref}$  is actually 100 nA lower than expected, whereas the right current source  $I_{ref}$  is actually 100 nA higher than expected. Find the absolute accuracy of stress measurement by the instrument at  $\sigma = 0$ , and at  $\sigma = 1$  kPa.

$$V_{0 \text{ actual}} = R_{nom} \left(1 + \frac{G}{E} \sigma\right) (I_{ref} + 100 \text{ nA}) - R_{nom} (I_{ref} - 100 \text{ nA})$$

$$V_{0 \text{ ideal}} = R_{nom} \left(1 + \frac{G}{E} \sigma\right) I_{ref} - R_{nom} I_{ref}$$

$$\text{Accuracy}(\sigma) = \frac{\text{Accuracy}(V_0)}{S}$$

$$= \frac{1}{S} \cdot |V_{0 \text{ actual}} - V_{0 \text{ ideal}}|$$

$$= \frac{1}{S} \cdot |R_{nom} \left(1 + \frac{G}{E} \sigma\right) \cdot 100 \text{ nA} - R_{nom} \cdot (-100 \text{ nA})|$$

$$= \frac{R_{nom} \cdot 100 \text{ nA}}{S} \cdot \left|2 + \frac{G}{E} \sigma\right|$$

$$= 10 \text{ Pa} \cdot \left|2 + \frac{\sigma}{1 \text{ kPa}}\right|$$

$$\sigma = 0 \quad \Rightarrow \quad \text{Accuracy}(\sigma) = 10 \text{ Pa} \cdot 2 = 20 \text{ Pa}$$

$$\sigma = 1 \text{ kPa} \quad \Rightarrow \quad \text{Accuracy}(\sigma) = 10 \text{ Pa} \cdot \left(2 + \frac{1 \text{ kPa}}{1 \text{ kPa}}\right) = 30 \text{ Pa}$$

- (e) [10 pts] An analog-to-digital converter (ADC) is used to digitize the voltage output  $V_o$  for a digital reading of the stress  $\sigma$ . Find the full-scale voltage range and the number of bits of the ADC required for a full-scale stress range from 0 to 1 kPa at a resolution of 1 Pa.

$$\sigma = 0 \quad \Rightarrow \quad V_o = V_{\text{off}} = 0$$

$$\sigma = 1 \text{ kPa} \quad \Rightarrow \quad V_o = V_{\text{off}} + \frac{1 \text{ kPa}}{1 \text{ kPa/V}} = 1 \text{ V}$$

$\Rightarrow$  ADC voltage range : 0 to 1 V

$$\Delta\sigma = 1 \text{ Pa} \quad \Rightarrow \quad \Delta V_o = \frac{1 \text{ Pa}}{1 \text{ kPa/V}} = 1 \text{ mV}$$

$$\Rightarrow \text{ADC number of bits} = \log_2 \frac{1 \text{ V}}{\underbrace{1 \text{ mV}}_{1,000}} = 10 \text{ bits}$$

- (f) [5 pts] You observe that the transducer is subject to a drifting offset due to variations in temperature. What simple change could you make to the design in order to eliminate this temperature dependence? *Hint*: you may assume that all identical components, such as the two current sources, have identical temperature coefficients.

Replace  $R$  with a matching strain gage  $R_G$ ,  
but with zero stress :

