

BENG 186B Winter 2023

Quiz 1

Friday, January 27, 2023

Name (Last, First): SOLUTIONS

- This quiz is on-line, open-book, and open-notes, but web search is prohibited. You may follow electronic links from Canvas or the class web pages, but not any further. **No collaboration or communication in any form is allowed**, except for questions to the instructor and TAs.
- The quiz is due January 27, 2023 at 11:59pm, over Canvas (Gradescope). It should approximately take 2 hours to complete, but there is no time limit other than the submission deadline. Do not discuss any class-related topics among yourselves before or after you have completed your quiz, and until the submission deadline has passed.
- There are 3 problems. Points for each problem are given in **[brackets]**. There are 100 points total.

1. [20 pts] Circle the **best answer (only one answer per question)**:

(a) [4 pts] The precision of a bioinstrument is affected by:

- i. systematic offset.
- ii. measurement noise.
- iii. saturation.
- iv. all of the above.

(b) [4 pts] An inductor-capacitor undamped second-order system:

- i. oscillates at its natural frequency.
- ii. produces unbounded output when driven with an input at the natural frequency.
- iii. conserves energy.
- iv. all of the above.

(c) [4 pts] The Norton equivalent of a linear circuit is:

- i. an ideal voltage source in parallel with an impedance.
- ii. an ideal voltage source in series with an impedance.
- iii. an ideal current source in series with an impedance.
- iv. an ideal current source in parallel with an impedance.


(d) [4 pts] The gauge factor of a strain gauge depends on:

- i. resistance.
- ii. Young's modulus.
- iii. Poisson ratio.
- iv. all of the above.


(e) [4 pts] The sensitivity of an inductive displacement sensor depends on:

- i. the number of windings of the inductive coil.
- ii. the magnetic susceptibility of the magnetic core.
- iii. its geometry.
- iv. all of the above.

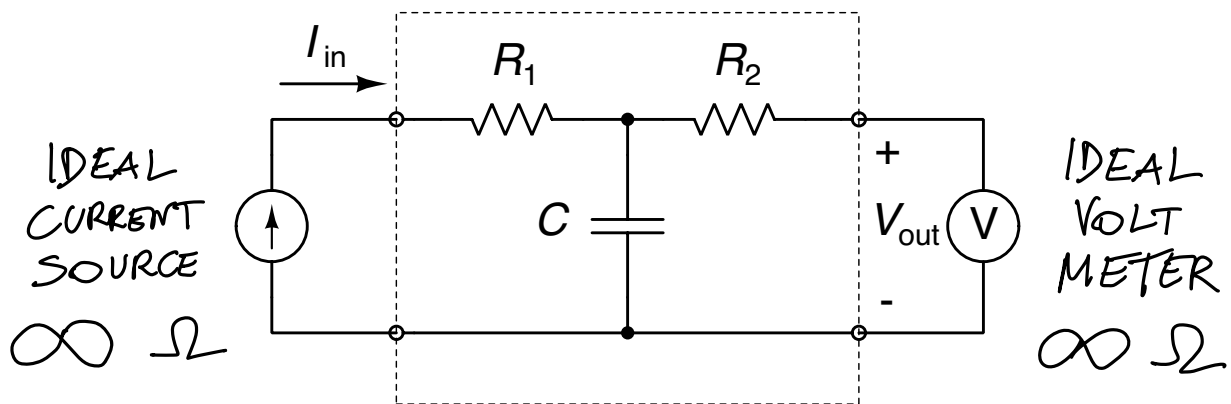2. [40 pts] Consider the **current-input, voltage-output** filter circuit below.




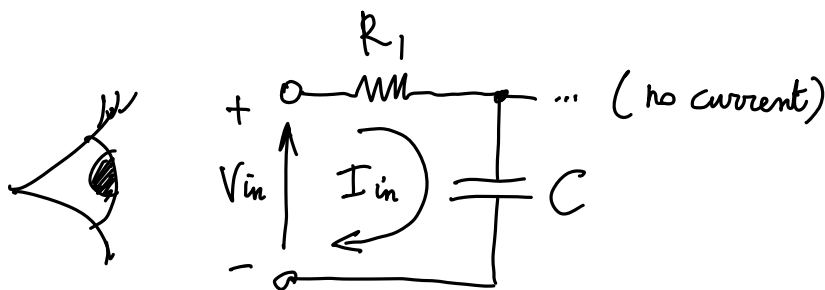(a) [10 pts] Find the input impedance $Z_{in}(j\omega)$.




$$Z_{in} = R_1 + \frac{1}{j\omega C} = \frac{1 + j\omega R_1 C}{j\omega C}$$

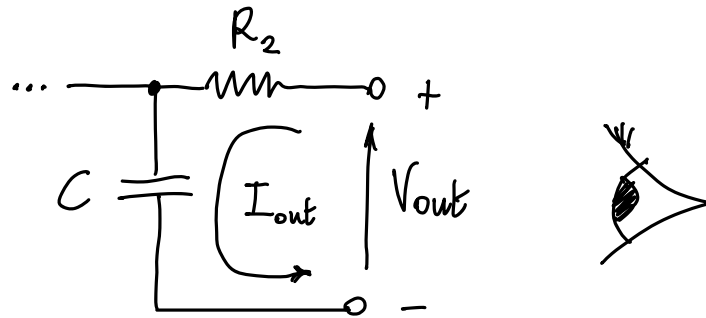(b) [10 pts] Find the output impedance $Z_{out}(j\omega)$.



$$Z_{out} = R_2 + \frac{1}{j\omega C} = \frac{1 + j\omega R_2 C}{j\omega C}$$

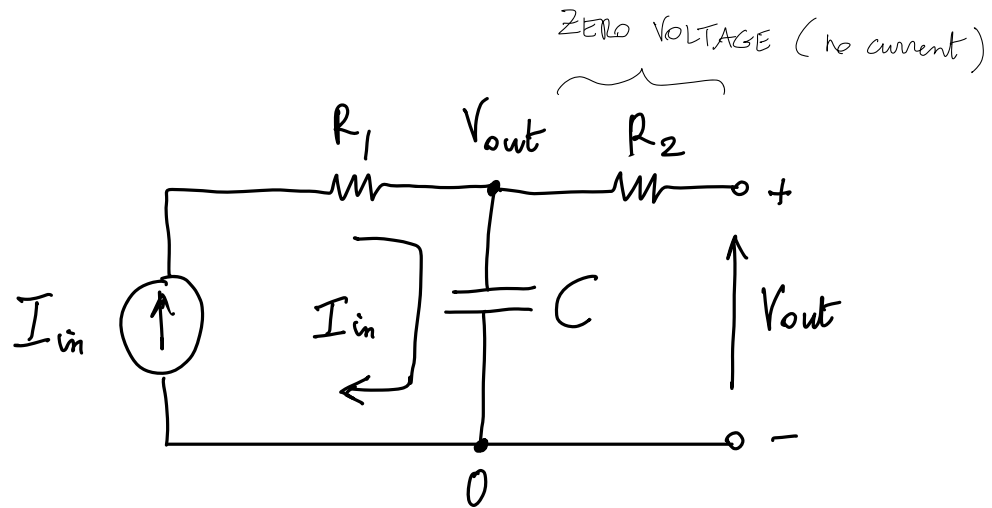- (c) [10 pts] Find the transfer function $H(j\omega) = V_{out}(j\omega) / I_{in}(j\omega)$. What are the units?





$$V_{out} = \frac{1}{j\omega C} I_{in}$$


$$\Rightarrow H(j\omega) = \frac{V_{out}(j\omega)}{I_{in}(j\omega)} = \frac{1}{j\omega C}$$

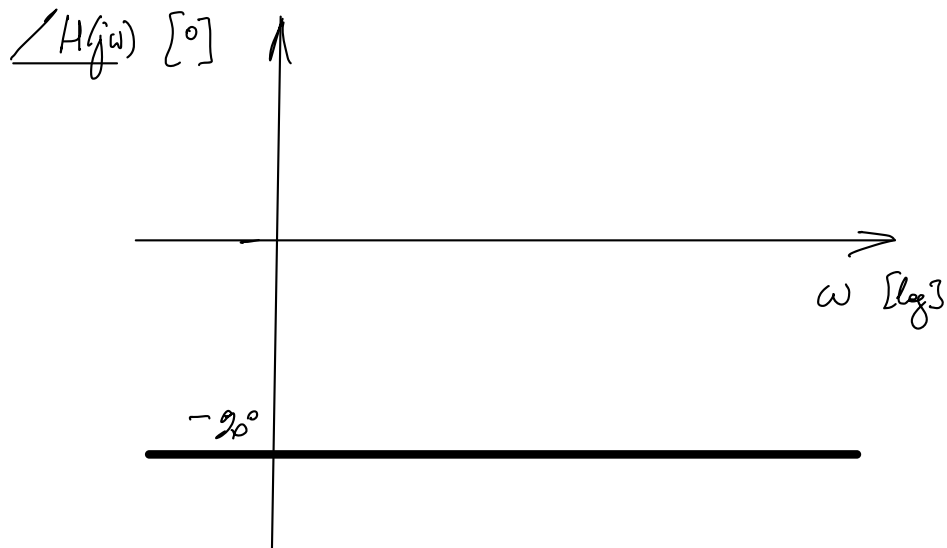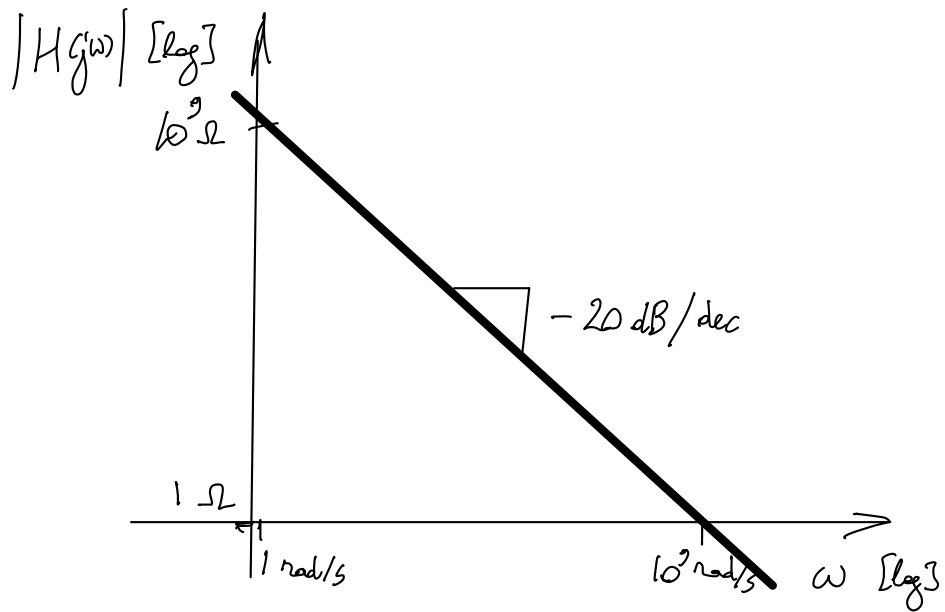- (d) [10 pts] Sketch the Bode plot of the transfer function $H(j\omega)$ for $C = 1 \text{ nF}$, and $R_1 = R_2 = 1 \text{ k}\Omega$. Be sure to label the axes and indicate the units.

$$H(j\omega) = \frac{1}{j\omega C} \quad ; \quad \begin{cases} \text{NO ZEROS} \\ \text{POLE @ } s = 0 \end{cases}$$



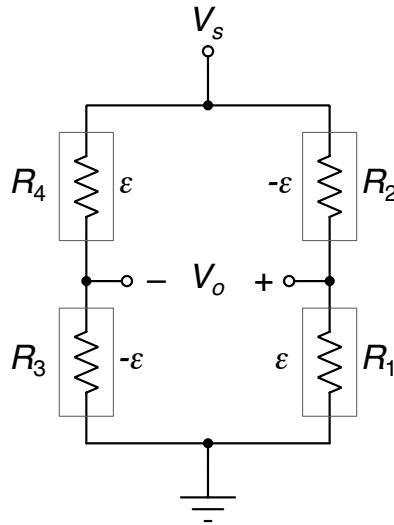3. [40 pts] Consider the strain transducer below, with constant supply voltage $V_s = 1 \text{ V}$, and four strain gauges R_1, R_2, R_3 and R_4 all with identical nominal resistance $R_{nom} = 100 \text{ k}\Omega$, and gauge factor $G = 100$. The transducer produces a differential output voltage V_o in response to positive strain ϵ applied to two of the strain gauges R_1 and R_4 , and exact opposite negative strain $-\epsilon$ applied to the other two strain gauges R_2 and R_3 .



$$R_1 = R_4 = R_{nom} (1 + G \epsilon)$$

$$R_2 = R_3 = R_{nom} (1 - G \epsilon)$$

- (a) [5 pts] Find the output voltage V_o as a function of strain ϵ . Is the response linear, and why?

$$V_o = \left(\frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right) V_s$$

$$= \left(\frac{\cancel{R_{nom}} (1 + G \epsilon)}{2 \cancel{R_{nom}}} - \frac{\cancel{R_{nom}} (1 - G \epsilon)}{2 \cancel{R_{nom}}} \right) V_s$$

$$= \frac{\cancel{2} G \epsilon}{\cancel{2}} V_s = G V_s \cdot \epsilon \quad \text{LINEAR}$$

because differential with
complementary strain gauges

(b) [5 pts] Find the sensitivity and offset of the strain transducer.

$$\text{Sensitivity } S = \frac{dV_o}{d\varepsilon} = G V_s = 100 \text{ V}$$

Zero offset

- (c) [10 pts] Now consider that the gauge factors of both R_1 and R_2 are 10 % smaller than expected, whereas the gauge factors of both R_3 and R_4 are 10 % larger than expected. Find the sensitivity and offset of the strain transducer, and compare with (b). Explain what you observe.

$$V_o = \left(\frac{R_{nom} (1 + 0.9 G \epsilon)}{R_{nom} (1 + 0.9 G \epsilon + 1 - 0.9 G \epsilon)} - \frac{R_{nom} (1 - 1.1 G \epsilon)}{R_{nom} (1 - 1.1 G \epsilon + 1 + 1.1 G \epsilon)} \right) V_s$$

$$= \frac{R_{nom} \cancel{2} G \epsilon}{R_{nom} \cancel{2}} V_s = G V_s \epsilon$$

Sensitivity $S = \frac{dV_o}{d\epsilon} = G V_s = 100 \text{ V}$

Zero offset

Same as (b)!

Because, the variations cancel in the differential complementary combining top and bottom.

- (d) [10 pts] Now consider that the strain gauges R_1 and R_3 have identical temperature coefficients $\alpha = 0.01 \text{ C}^{-1}$, whereas the strain gauges R_2 and R_4 are temperature independent. Find the sensitivity of the transducer output voltage V_o to temperature T , at zero strain $\epsilon = 0$. Explain what you observe.

$$V_o = \left(\frac{R_{nom} (1 + \alpha \Delta T)}{R_{nom} (1 + \alpha \Delta T) + R_{nom}} - \frac{R_{nom} (1 + \alpha \Delta T)}{R_{nom} (1 + \alpha \Delta T) + R_{nom}} \right) V_s$$

@ $\epsilon = 0$

$$= 0$$

Zero sensitivity to temperature !

Because, differential with identical variations left and right.

- (e) [10 pts] Find the worst-case absolute accuracy of digital reading of the strain using a 12-bit analog-to-digital converter that spans a 100 mV range at the output of the strain transducer.

$$\begin{aligned}
 & \text{Worst-case absolute accuracy (strain)} \\
 &= \frac{1}{2} \text{ LSB @ input (strain)} \\
 &= \frac{1}{2} \frac{\text{LSB @ output (voltage)}}{S} \quad \left(\text{sensitivity} = \frac{\text{output}}{\text{input}} \right) \\
 &= \frac{1}{2} \frac{2^{-12} \text{ Range @ output}}{S} \\
 &= \frac{1}{2} \frac{\frac{1}{4,096} \cdot 0.1 \text{ V}}{100 \text{ V}} = 1.22 \cdot 10^{-7} \\
 & \quad \quad \quad (12.2 \text{ ppm})
 \end{aligned}$$