

BENG 186B Winter 2025

Quiz 1

Friday, January 24, 2025

Name (Last, First): _____

- This quiz is on-line, open-book, and open-notes, but web search is prohibited. You may follow electronic links from Canvas or the class web pages, but not any further. **No collaboration or communication in any form is allowed**, except for questions to the instructor and TAs.
- The quiz is due January 24, 2025 at 11:59pm, over Canvas (Gradescope). It should approximately take 2 hours to complete, but there is no time limit other than the submission deadline. Do not discuss any class-related topics among yourselves before or after you have completed your quiz, and until the submission deadline has passed.
- There are 3 problems. Points for each problem are given in **[brackets]**. There are 100 points total.

1. [20 pts] Circle the **best answer (only one answer per question)**:

(a) [4 pts] The accuracy of a bioinstrument can be improved by:

- i. averaging multiple output samples.
- ii. lowering input noise.
- iii. subtracting output offset.
- iv. all of the above.

(b) [4 pts] A resistor-capacitor first-order system:

- i. peaks at its natural frequency.
- ii. produces exponentially decaying output transients.
- iii. conserves energy.
- iv. none of the above.

(c) [4 pts] The Thévenin equivalent of a linear circuit is:

- i. an ideal voltage source in parallel with an impedance.
- ii. an ideal voltage source in series with an impedance.
- iii. an ideal current source in series with an impedance.
- iv. an ideal current source in parallel with an impedance.


(d) [4 pts] The resistance of a strain gauge depends on:

- i. strain.
- ii. stress.
- iii. temperature.
- iv. all of the above.

(e) [4 pts] An ideal transformer:

- i. perfectly couples magnetic field across two coils.
- ii. transfers power without loss.
- iii. insulates input from output.
- iv. all of the above.

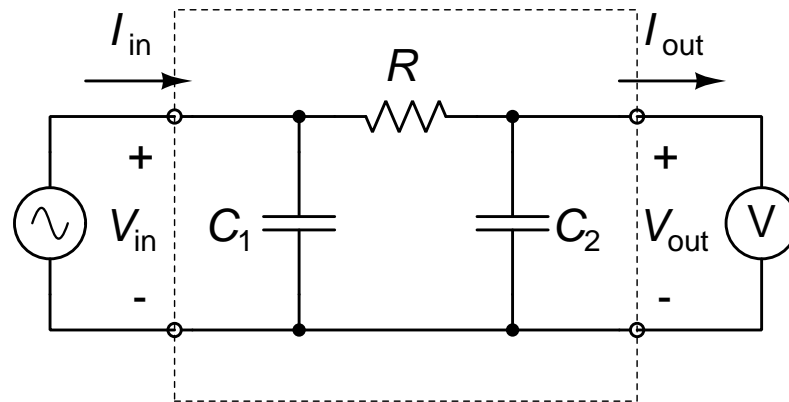2. [40 pts] Consider the **voltage-input, voltage-output** filter circuit below.




(a) [10 pts] Find the input impedance $Z_{in}(j\omega)$.

(b) [10 pts] Find the output impedance $Z_{out}(j\omega)$.

- (c) [10 pts] Find the transfer function $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$. What are the units?

- (d) [10 pts] Sketch the Bode plot of the transfer function $H(j\omega)$ for $C_1 = C_2 = 1 \text{ nF}$, and $R = 1 \text{ k}\Omega$. Be sure to label the axes and indicate the units.

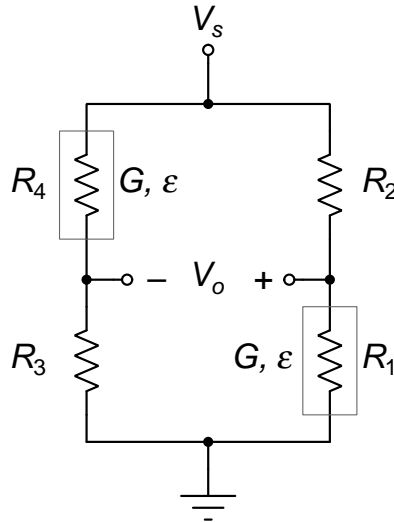3. **[40 pts]** Consider the stress transducer below, with constant supply voltage $V_s = 3 \text{ V}$, and four resistors R_1 , R_2 , R_3 and R_4 all with identical nominal resistance $R_{nom} = 10 \text{ k}\Omega$. Resistors R_1 and R_4 are strain gauges with identical gauge factor $G = 50$, and identical Young's modulus $E = 10 \text{ kPa}$. The transducer produces a differential output voltage V_o in response to stress σ applied to the two strain gauges R_1 and R_4 .



$$R_1 = R_4 = R_{nom} (1 + G \epsilon)$$

$$R_2 = R_3 = R_{nom}$$

- (a) [10 pts] Find the output voltage V_o as a function of stress σ . Is the response linear, and why?

(b) [5 pts] Find the offset of the stress transducer.

(c) [5 pts] Find the sensitivity of the stress transducer at zero stress.

- (d) [10 pts] Now consider that the resistors R_2 and R_3 have identical temperature coefficient α , whereas the strain gauges R_1 and R_4 are temperature independent. Find the sensitivity of the transducer output voltage V_o to temperature T , at zero stress $\sigma = 0$. Explain what you observe.

- (e) [10 pts] Find the worst-case absolute accuracy of digital reading of the stress using a 10-bit analog-to-digital converter that spans a 200 mV range at the output of the strain transducer.