

# BENG 186B Winter 2025

## Quiz 1

Friday, January 24, 2025

*Name (Last, First):* SOLUTIONS

- This quiz is on-line, open-book, and open-notes, but web search is prohibited. You may follow electronic links from Canvas or the class web pages, but not any further. **No collaboration or communication in any form is allowed**, except for questions to the instructor and TAs.
- The quiz is due January 24, 2025 at 11:59pm, over Canvas (Gradescope). It should approximately take 2 hours to complete, but there is no time limit other than the submission deadline. Do not discuss any class-related topics among yourselves before or after you have completed your quiz, and until the submission deadline has passed.
- There are 3 problems. Points for each problem are given in **[brackets]**. There are 100 points total.

1. [20 pts] Circle the **best answer (only one answer per question)**:

(a) [4 pts] The accuracy of a bioinstrument can be improved by:

- i. averaging multiple output samples.
  - ii. lowering input noise.
  - ☒ iii. subtracting output offset.
  - iv. all of the above.
- } these improve precision

(b) [4 pts] A resistor-capacitor first-order system:

- i. peaks at its natural frequency.
- ☒ ii. produces exponentially decaying output transients.
- iii. conserves energy.
- iv. none of the above.

(c) [4 pts] The Thévenin equivalent of a linear circuit is:

- i. an ideal voltage source in parallel with an impedance.
- ☒ ii. an ideal voltage source in series with an impedance.
- iii. an ideal current source in series with an impedance.
- iv. an ideal current source in parallel with an impedance.


(d) [4 pts] The resistance of a strain gauge depends on:

- i. strain.
- ii. stress.
- iii. temperature.
- ☒ iv. all of the above.


(e) [4 pts] An ideal transformer:

- i. perfectly couples magnetic field across two coils.
- ii. transfers power without loss.
- iii. insulates input from output.
- ☒ iv. all of the above.

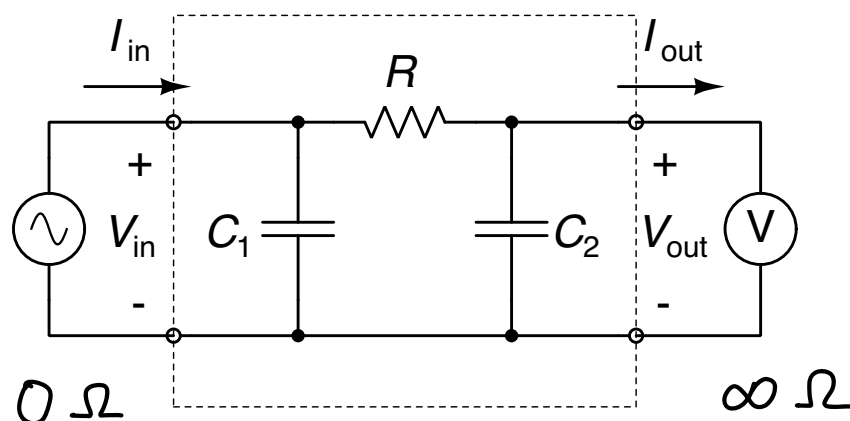2. [40 pts] Consider the **voltage-input, voltage-output** filter circuit below.



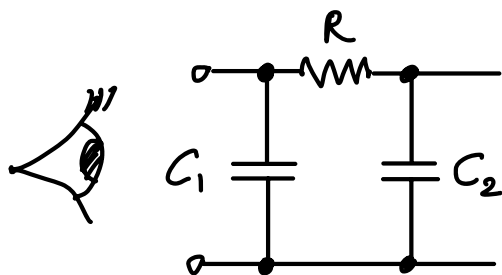
(a) [10 pts] Find the input impedance  $Z_{in}(j\omega)$ .



$$Z_{in} = \frac{1}{j\omega C_1} \parallel R + \frac{1}{j\omega C_2} = \frac{\frac{1}{j\omega C_1} \left( R + \frac{1}{j\omega C_2} \right)}{\frac{1}{j\omega C_1} + R + \frac{1}{j\omega C_2}} \times (j\omega C_1)(j\omega C_2)$$


$$= \frac{1 + j\omega RC_2}{j\omega (C_1 + C_2 + j\omega RC_1 C_2)}$$

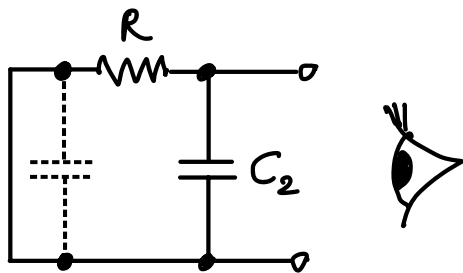(b) [10 pts] Find the output impedance  $Z_{out}(j\omega)$ .



$$Z_{out} = \frac{1}{j\omega C_2} \parallel R = \frac{\frac{1}{j\omega C_2} \cdot R}{\frac{1}{j\omega C_2} + R} = \frac{R}{1 + j\omega RC_2}$$

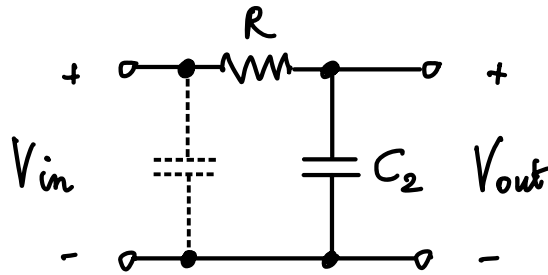- (c) [10 pts] Find the transfer function  $H(j\omega) = V_{out}(j\omega) / V_{in}(j\omega)$ . What are the units?





$$V_{out} = \frac{\frac{1}{j\omega C_2}}{\frac{1}{j\omega C_2} + R} V_{in} = \frac{1}{1 + j\omega RC_2} V_{in}$$


$$H(j\omega) = \frac{V_{out}(j\omega)}{V_{in}(j\omega)} = \frac{1}{1 + j\omega RC_2}$$

Units: dimensionless (V / V)

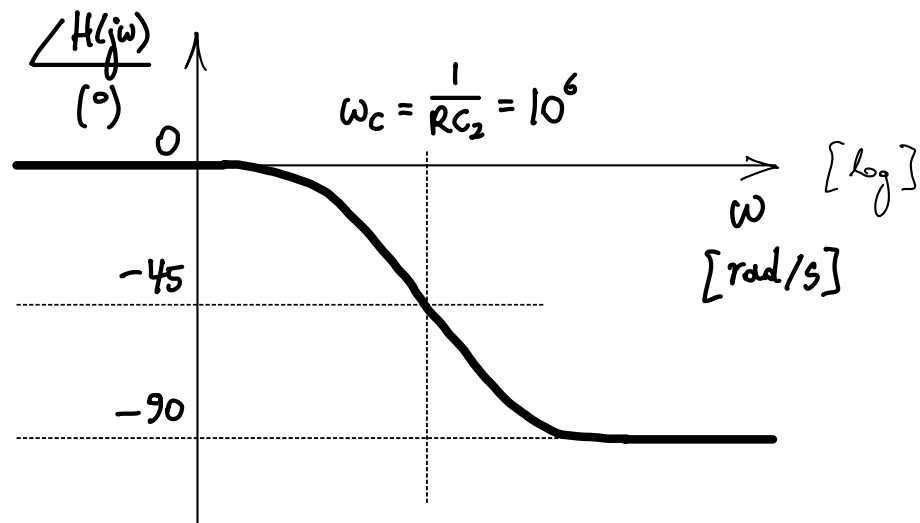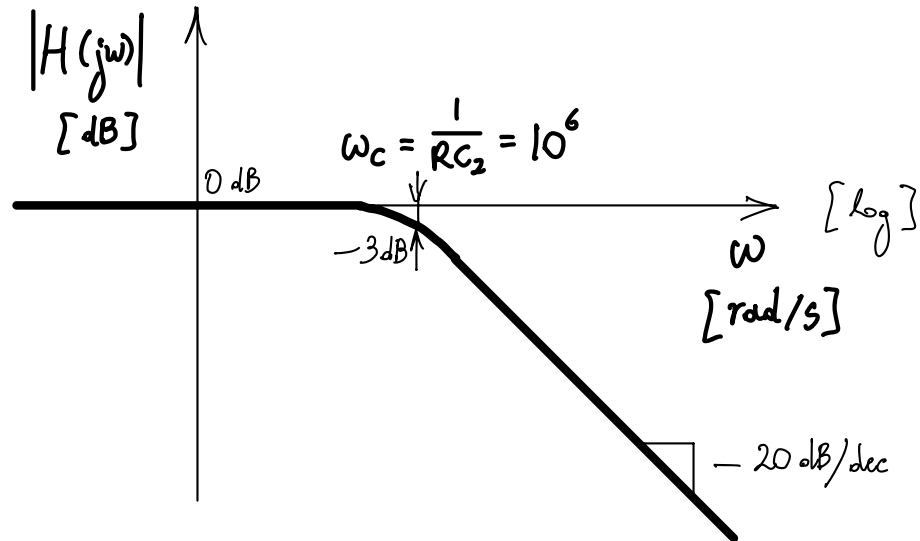- (d) [10 pts] Sketch the Bode plot of the transfer function  $H(j\omega)$  for  $C_1 = C_2 = 1 \text{ nF}$ , and  $R = 1 \text{ k}\Omega$ . Be sure to label the axes and indicate the units.



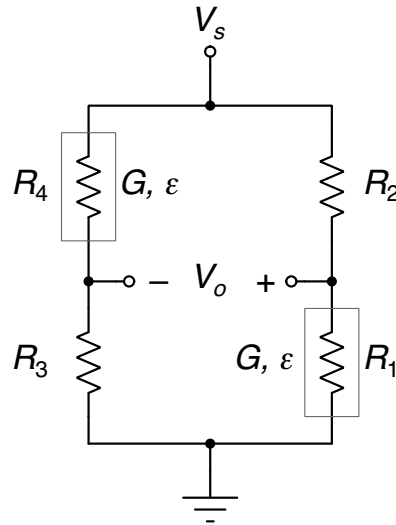3. [40 pts] Consider the stress transducer below, with constant supply voltage  $V_s = 3\text{ V}$ , and four resistors  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$  all with identical nominal resistance  $R_{nom} = 10\text{ k}\Omega$ . Resistors  $R_1$  and  $R_4$  are strain gauges with identical gauge factor  $G = 50$ , and identical Young's modulus  $E = 10\text{ kPa}$ . The transducer produces a differential output voltage  $V_o$  in response to stress  $\sigma$  applied to the two strain gauges  $R_1$  and  $R_4$ .



$$\begin{aligned} R_1 &= R_4 = R_{nom} (1 + G \epsilon) \\ R_2 &= R_3 = R_{nom} \end{aligned}$$

- (a) [10 pts] Find the output voltage  $V_o$  as a function of stress  $\sigma$ . Is the response linear, and why?

$$\begin{aligned} V_o &= \left( \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right) V_s \\ &= \left( \frac{R_{nom} \left( 1 + \frac{G}{E} \sigma \right)}{R_{nom} \left( 1 + \frac{G}{E} \sigma \right) + R_{nom}} - \frac{R_{nom}}{R_{nom} + R_{nom} \left( 1 + \frac{G}{E} \sigma \right)} \right) V_s \\ &= \frac{\cancel{R_{nom}} \frac{G}{E} \sigma}{\cancel{R_{nom}} \left( 2 + \frac{G}{E} \sigma \right)} V_s = \frac{\frac{1}{2} \frac{G}{E} V_s \sigma}{1 + \frac{1}{2} \frac{G}{E} \sigma} \leftarrow \text{Nonlinear} \end{aligned}$$

(b) [5 pts] Find the offset of the stress transducer.

$$V_{\text{off}} = 0 \quad \text{because} \quad V_o(\sigma=0) = 0$$

(c) [5 pts] Find the sensitivity of the stress transducer at zero stress.

$$S = \left. \frac{dV_o}{d\sigma} \right|_{\sigma=0} = \frac{1}{2} \frac{G}{E} V_s = \frac{1}{2} \frac{50}{10 \text{ kPa}} 3V = 7.5 \frac{V}{\text{kPa}}$$



- (d) [10 pts] Now consider that the resistors  $R_2$  and  $R_3$  have identical temperature coefficient  $\alpha$ , whereas the strain gauges  $R_1$  and  $R_4$  are temperature independent. Find the sensitivity of the transducer output voltage  $V_o$  to temperature  $T$ , at zero stress  $\sigma = 0$ . Explain what you observe.

$$R_1 = R_4 = R_{nom} \quad @ \quad \sigma = 0$$

$$R_2 = R_3 = R_{nom} (1 + \alpha \Delta T)$$

$$V_o = \left( \frac{R_1}{R_1 + R_2} - \frac{R_3}{R_3 + R_4} \right) V_s$$

$$= \left( \frac{R_{nom}}{R_{nom} + R_{nom} (1 + \alpha \Delta T)} - \frac{R_{nom} (1 + \alpha \Delta T)}{R_{nom} (1 + \alpha \Delta T) + R_{nom}} \right) V_s$$

$$= - \frac{\cancel{R_{nom}} \alpha \Delta T}{\cancel{R_{nom}} (2 + \alpha \Delta T)} V_s = - \frac{\frac{\alpha}{2} V_s \Delta T}{1 + \frac{\alpha}{2} \Delta T}$$

$$S_T = \left. \frac{\partial V_o}{\partial \Delta T} \right|_{\sigma=0} = - \frac{\alpha}{2} V_s \quad \text{for } |\Delta T| \ll \frac{2}{\alpha}$$

The offset of the stress transducer shifts with temperature.

Regardless of stress it also acts as a temperature transducer.

- (e) [10 pts] Find the worst-case absolute accuracy of digital reading of the stress using a 10-bit analog-to-digital converter that spans a 200 mV range at the output of the strain transducer.

Worst-case absolute accuracy

$$= \frac{1}{2} \text{ LSB @ input (stress)}$$

$$= \frac{1}{2} \frac{\text{LSB @ output (voltage)}}{S}$$

$$= \frac{1}{2} \frac{2^{-10} \text{ Range @ output}}{S}$$

$$= \frac{1}{2} \frac{\frac{1}{1,024} \cancel{0.2 \text{ V}}}{7.5 \cancel{\text{ V}} / \text{kPa}}$$

$$= 1.3 \cdot 10^{-5} \text{ kPa} = 0.013 \text{ Pa}$$