

BENG 186B Winter 2019


Quiz 2

Friday, February 15, 2019


Last Name, First Name: SOLUTIONS

- This quiz is closed book and closed notes. You may use a calculator for algebra and arithmetic.
- This quiz has 9 pages, including this cover sheet. Do not attach separate sheets. If you need more space, use the back of the pages.
- Circle or box your final answers and show your work on the pages provided.
- There are 4 problems. Points for each problem are given in **[brackets]**. There are 100 points total.
- You have 50 minutes to complete this quiz.

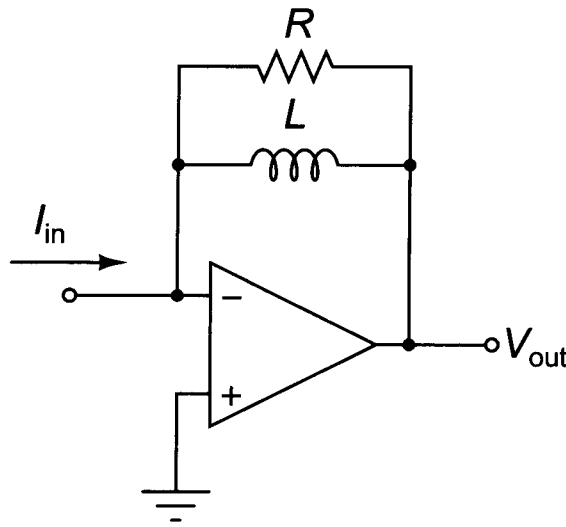1. [25 pts] Consider the current-in, voltage-out active filter circuit below:



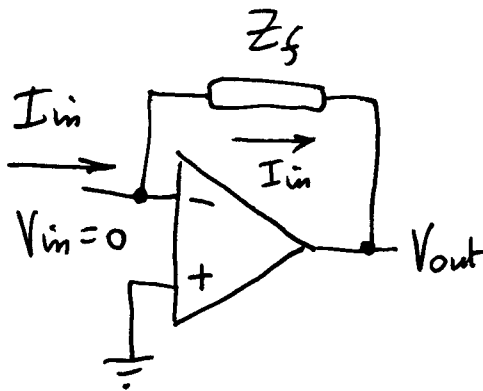(a) [15 pts] Assume the operational amplifier is ideal and unsaturated. Derive the transfer function $H(j\omega) = V_{out}(j\omega) / I_{in}(j\omega)$. What type of filter characteristic is this? What is the cutoff frequency?



$$Z_f = R \parallel j\omega L$$

$$= \frac{R \cdot j\omega L}{R + j\omega L} = \frac{j\omega L}{1 + j\omega \frac{L}{R}}$$

$$H(j\omega) = \frac{V_{out}(j\omega)}{I_{in}(j\omega)} = -Z_f(j\omega) = -\frac{j\omega L}{1 + j\omega \frac{L}{R}} = -\frac{j\omega L}{1 + \frac{j\omega}{\omega_c}}$$

\Rightarrow HIGHPASS with cut-off $\omega_c = \frac{R}{L}$

2

$$f_c = \frac{1}{2\pi} \frac{R}{L}$$

(b) [5 pts] What is the input impedance at the I_{in} node?


$$Z_{in} = 0 \quad \text{because } V_{in} = 0 \text{ independent of } I_{in}$$

(c) [5 pts] What is the output impedance at the V_{out} node?

$$Z_{out} = 0 \quad \text{because } V_{out} \text{ is independent of } I_{out}$$

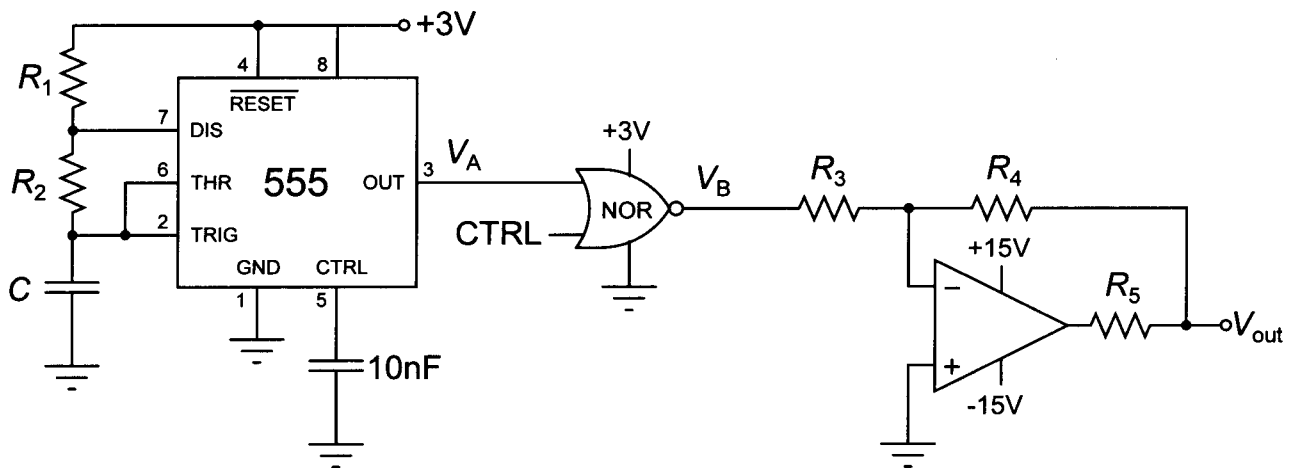2. [35 pts] A deep-brain stimulation (DBS) circuit is shown below. All active components are ideal. The 555 timer IC and the NOR logic gate operate from a +3V single supply, while the opamp operates from a +15V/-15V dual supply. The CTRL control input is logic low (0 V) by default. The values for the passive components are $R_1 = 572 \text{ k}\Omega$, $R_2 = 286 \text{ k}\Omega$, $R_3 = 100 \text{ k}\Omega$, $R_4 = 300 \text{ k}\Omega$, $R_5 = 0$, and $C = 10 \text{ nF}$. You may also find these equations useful for the 555 timer ($\ln(3) \approx 1.1$ and $\ln(2) \approx 0.7$):

$$T = \ln(3) \times RC \quad T_{lo} = \ln(2) \times R_2 C \quad T_{hi} = \ln(2) \times (R_1 + R_2)C$$



- (a) [25 pts] Sketch the waveforms for the voltages V_A , V_B and V_{out} on the diagrams on the next page. Ignore any initial transients, and assume that the circuit has been running forever such that the origin $t = 0$ on the time axis is arbitrary. Show your work below.

ASTABLE (Oscillator)

NOR

INVERTING AMPLIFIER

Amplitude: +3V

$$T_{lo} = 0.7 \cdot 286 \text{ k}\Omega \cdot 10 \text{ nF} = 2 \text{ ms}$$

$$T_{hi} = 0.7 \cdot 858 \text{ k}\Omega \cdot 10 \text{ nF} = 6 \text{ ms}$$

$$\text{Period: } 2 \text{ ms} + 6 \text{ ms} = 8 \text{ ms}$$

Gain:


$$A_V = -\frac{R_4}{R_3} = -3$$

$\Rightarrow V_A$: Square wave w/ 3V amplitude, 8ms period,
 75% duty cycle

$$V_B = \overline{V_A + \text{CTRL}} = \overline{V_A} \text{ for CTRL} = 0$$

logic inversion

$$V_{\text{out}} = -3 V_B$$

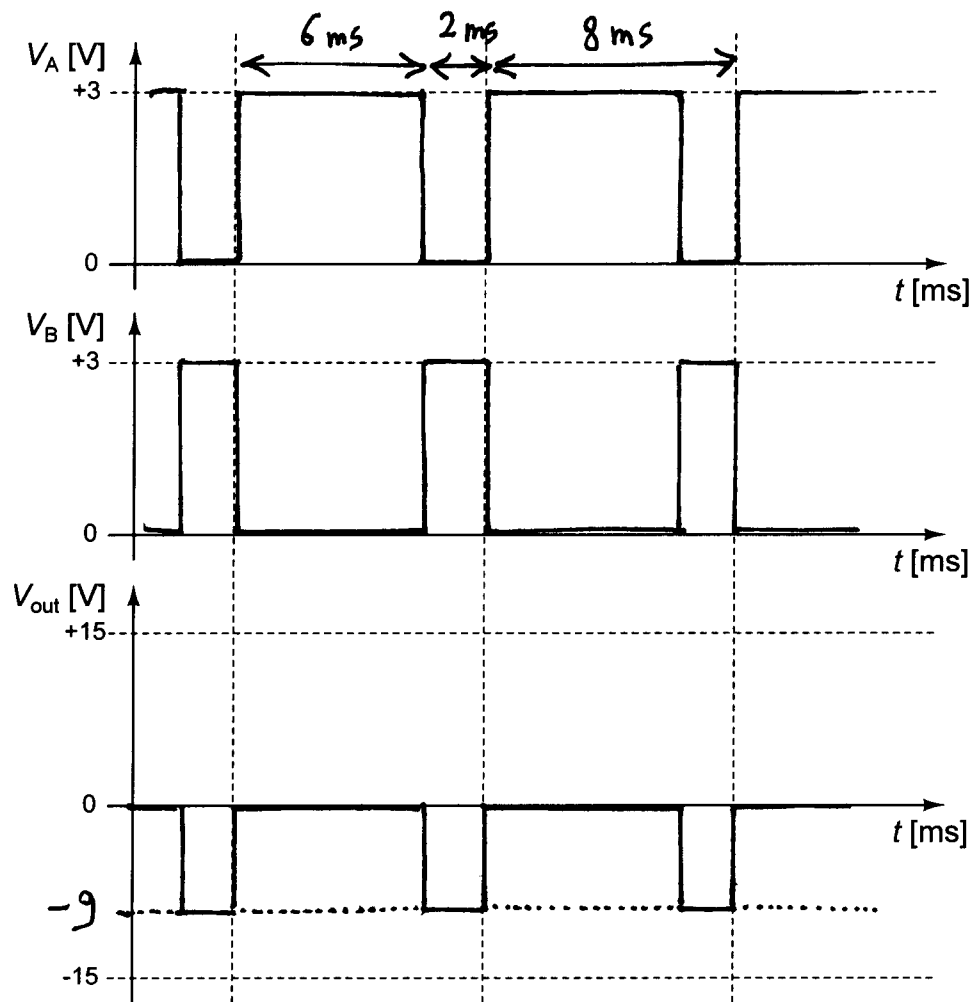

- (b) [5 pts] What purpose does the control input CTRL serve in the biomedical application? Explain.

CTRL allows to turn off the stimulator when it is not needed/wanted.

$$\begin{cases} \text{CTRL} = 1 \Rightarrow V_B = 0, \text{ and } V_{out} = 0 & (\text{OFF}) \\ \text{CTRL} = 0 \Rightarrow V_B = \bar{V}_A, \text{ and } V_{out} = -3\bar{V}_A & (\text{ON}) \end{cases}$$

- (c) [5 pts] Does the output voltage V_{out} depend on the value of the resistance R_5 ? What purpose does a large R_5 serve in the biomedical application?


No, except at larger output current.

Large R_5 serves to limit the maximum current that can be drawn from the output, protecting the patient/caregiver/instrument.

3. [20 pts] Circle the best answer (only one answer per question):

(a) [4 pts] The output V_{out} of the circuit at right (with an ideal LM311) goes high when the input V_{in} goes:

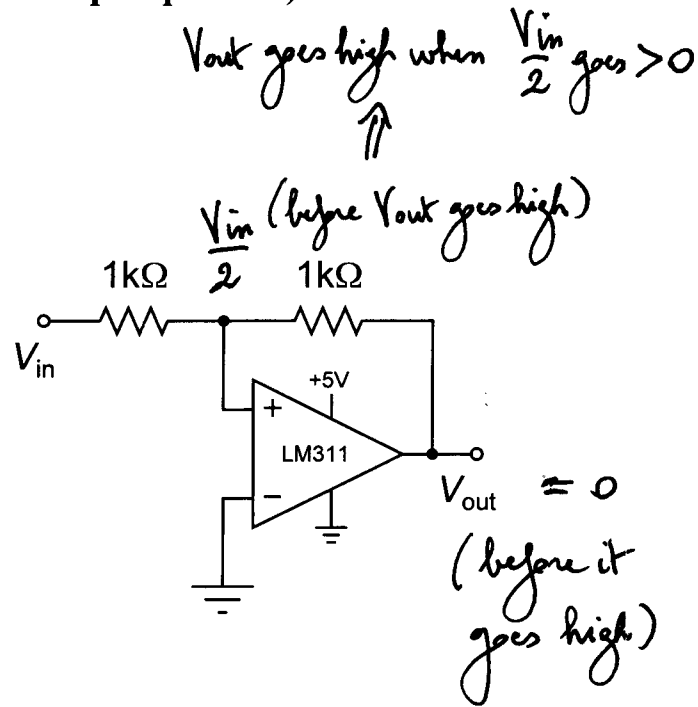- i. below 0
- ii. above 0
- iii. below +2.5V
- iv. above +2.5V
- v. below -5V




(b) [4 pts] An ideal transformer:

- i. has zero output impedance (not always; depends on input source impedance)
- ii. has infinite input impedance
- iii. converts magnetic to electrostatic energy
- iv. shares all magnetic flux between input and output coils
- v. has mutual inductance larger than either input and output inductances

(c) [4 pts] At very low current the electrode shown on the right has:

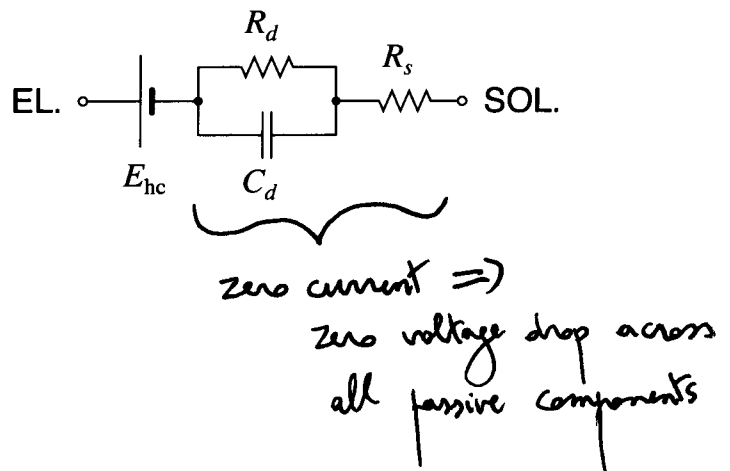- i. infinite impedance
- ii. zero impedance
- iii. voltage near the half-cell potential
- iv. zero voltage
- v. zero charge



(d) [1 pt ea.] Indicate for each statement below whether it is true or false:

- i. **TRUE** ~~FALSE~~: Nernst potentials of ion types in live cells are actively maintained by ion pumps that continuously restore concentration gradients across the membrane.
- ii. **TRUE** ~~FALSE~~: ECoG offers higher spatial and temporal resolution in resolving brain activity than EEG.
- iii. **TRUE** ~~FALSE~~: EMG activity can be observed anywhere on the body.
- iv. **TRUE** ~~FALSE~~: ERG is a measure of eye blink activity contaminating the EEG.
- v. **TRUE** ~~FALSE~~: A dipole consists of a pair of monopoles of same magnitude and opposing polarity.
- vi. **TRUE** ~~FALSE~~: The T wave of ECG indicates ventricular repolarization.
- vii. **TRUE** ~~FALSE~~: At thermal equilibrium the doublelayer charge across the membrane is zero on average.
- viii. **TRUE** ~~FALSE~~: Non-polarizable electrodes pass electrical current in either direction.

4. [20 pts] Consider two identical electrodes inserted in a Petri dish containing a biological cell culture preparation at room temperature. The cells are in a physiological saline environment of 0.15 mol/L NaCl in distilled water. Assume the cells are impermeable to K^+ and any other ion types except Na^+ and Cl^- . The GHK equation is:

$$V_m = \frac{RT}{F} \ln(10) \log_{10} \left(\frac{P_{Na}[Na^+]_o + P_K[K^+]_o + P_{Cl}[Cl^-]_i}{P_{Na}[Na^+]_i + P_K[K^+]_i + P_{Cl}[Cl^-]_o} \right)$$

and at room temperature $RT/F \ln(10) \approx 60$ mV.

- (a) [5 pts] Assume both electrodes are in the extracellular saline environment, without penetrating any cell. What voltage do you expect to measure by a voltmeter with infinite input impedance between the electrodes, and why?

Zero, since :

- 1) the two half-cell potentials are identical;
- 2) at zero current the voltage drop across the saline environment is zero.

- (b) [15 pts] Now one of the two electrodes is inserted in one of the cells in the culture. When a pharmacological agent is introduced to block all sodium channels, the voltage measured between this electrode and the other electrode remaining in the saline environment is $V_{cell} - V_{saline} = -60$ mV. What does that tell about Nernst potentials of the cell, and ion concentrations inside the cell? Explain.

$P_K = 0$: cells are impermeable to K^+

$P_{Na} = 0$; all sodium channels are blocked

$$\begin{aligned} \Rightarrow V_{cell} - V_{saline} &= 60 \text{ mV} \log_{10} \frac{[Cl^-]_{cell}}{[Cl^-]_{saline}} \\ &= E_{Cl} \\ &= -60 \text{ mV measured} \end{aligned}$$

$$\Rightarrow \begin{cases} E_{Cl} = -60 \text{ mV} \\ [Cl^-]_{cell} = \frac{1}{10} [Cl^-]_{saline} = 0.015 \frac{\text{mol}}{\text{L}} \end{cases} \text{ for } Cl^-$$

Nothing can be said for the other ion types Na^+ & K^+