

BENG 186B Principles of Bioinstrumentation

Week 4 Review

Exercises

Selections from:


2015 Homework 3

2015 Homework 4

BENG 186B Winter 2015 HW #3

Due *Thursday, February 5* at the beginning of class

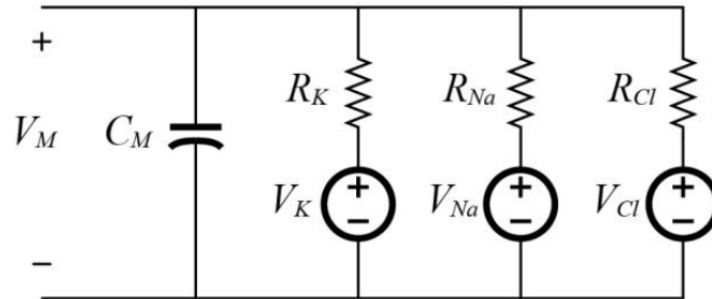1. **Nernst Potentials:** Consider the following circuit model for a cell.
 $R_K = 2.7 \text{ k}\Omega$, $R_{Na} = 30 \text{ k}\Omega$, $R_{Cl} = 3.3 \text{ k}\Omega$.




- (a) With the intracellular and extracellular concentrations given in the table below, calculate the Nernst Potential for each of the ionic species: V_K , V_{Na} , and V_{Cl} .

Ionic Species	Intracellular concentration	Extracellular concentration
K^+	397 mM	20 mM
Na^+	50 mM	437 mM
Cl^-	40 mM	556 mM

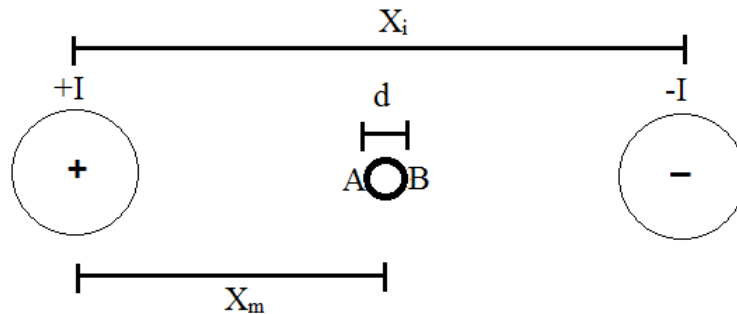- (b) Using the circuit model with Nernst potentials V_K , V_{Na} , and V_{Cl} and the resistances given above, find the membrane potential V_M at steady-state.
Hint: At DC steady-state, any capacitance reduces to an open circuit connection.
- (c) Now find the equilibrium resting potential V_M using the Goldman-Hodgkin-Katz equation. Compare the two values of the membrane potential. Which value is more reasonable for a typical resting potential of a cell?
Hint: Membrane conductance (the reciprocal of membrane resistance) for any ion type is directly proportional to membrane permeability for that ion type.
- (d) For a membrane capacitance $C_m = 1 \mu\text{F}$, find the time constant for the membrane potential V_M of the cell to recover from a transient and settle to its steady-state value.
2. **Electroporation:** Often it is necessary to insert genetic material into a cell, crossing its membrane. Electroporation is one means to open the membrane for insertion through the application of a high voltage. Here we study single cell electroporation, by injection of currents $+I$ and $-I$ through two nearby electrodes into the extracellular space, as shown in the figure below. The voltage across A and B, on both sides of the the cell, should not exceed 400 mV, otherwise the cell may die. The conductivity of the extracellular medium is $\sigma = 1 \Omega^{-1}\text{m}^{-1}$,

the inter-electrode distance is $X_i = 250 \mu\text{m}$, the cell is midway between the electrodes centered at distance $X_m = 125 \mu\text{m}$ from either electrode, and the cell diameter is $d = 20 \mu\text{m}$. Determine the maximum amplitude of the current I you can safely inject.

Hint: Express the voltage $V_A - V_B$ across the cell as a difference between two biopotentials generated by the same current dipole.



3. **Intracellular electronic recording:** In electrophysiology there are several techniques used to measure various aspects of electric activity in single cells. One such technique is the *current clamp*, which injects a current into the cell and measures the resulting membrane voltage of the cell. Based on the design specifications below design a circuit which accomplishes a current clamp for intracellular voltage recording.



- You are given a variable current source that is set to the desired current clamp value.
- The reference electrode is located in the extracellular space, and the recording electrode reaches inside the cell (through a glass pipette penetrating the cell membrane).
- The signal you are trying to measure at the recording electrode is in the range of -80 mV to 40 mV .
- Amplify the signal so an external voltmeter measures 1.2 V at 40 mV and 0 V at -80 mV . The output voltage should vary linearly with input voltage. The input impedance of your amplifier should be near-infinite.
- 60 Hz line noise present on the electrode wires should be reduced in the amplifier output.
- The frequency range of interest in the voltage signal is 100 Hz to 10 kHz .

Bonus: Design a *voltage clamp* circuit to the same above specifications for the current clamp, except the signal you are measuring is now current into the recording electrode for a fixed voltage across the electrodes, and the current signal ranges between -250 nA to $+250 \text{ nA}$, where the corresponding output voltage should range from -1 V to 1 V .

BENG 186B Winter 2015 HW #4
 Due *Thursday February 19* at the beginning of class


1. Cardiac vectors:

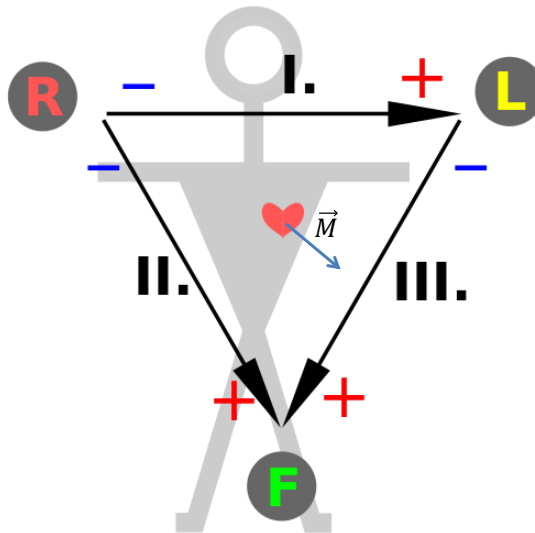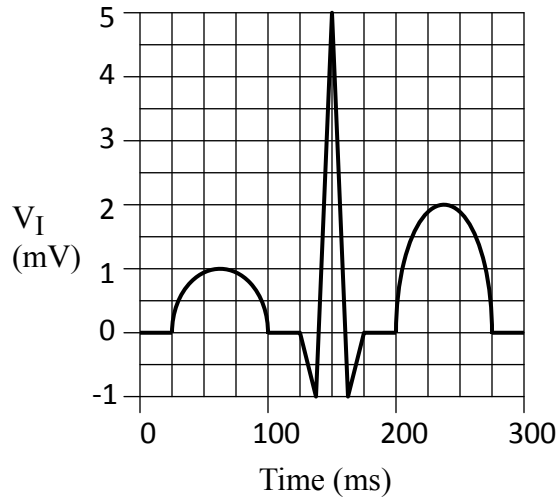- (a) Given the following ECG of Lead I and knowing that the amplitude of the R-wave in the Lead II ECG is 10 mV, determine the magnitude and direction of the cardiac vector \vec{M} , assuming it remains constant throughout the ECG. The length of each of the leads is 1 m.



- (b) Neatly sketch the ECG for Lead II and Lead III. On each of the graphs, label the axes and show the values of ECG amplitude at the P, R, and T waves.

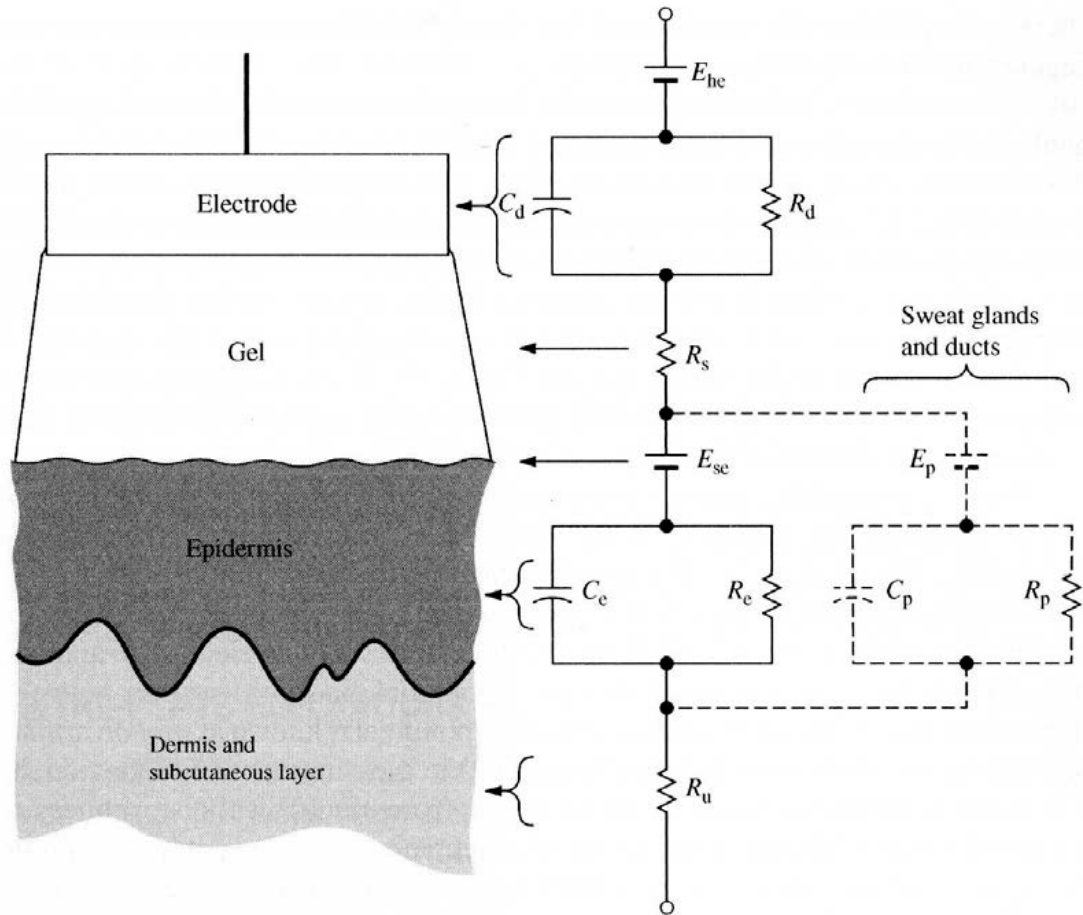
2. **Electrode model:** Consider the following skin–electrode model below:



- Find the expression for the impedance of the circuit when the subject is not sweating, that is, disregarding the sweat glands and ducts contribution.
- Find the expression for the impedance of the circuit when the subject is sweating, that is, including the sweat glands and ducts contribution.
- Using the following parameter values sketch (or plot) the magnitude of the impedance as a function of frequency, from 0.1Hz to 100Hz on a log-log scale. Make sure to properly label your plot with values and units.

$$\begin{array}{lllll}
 E_{hc} = 200 \text{ mV} & R_s = 1 \text{ k}\Omega & C_d = 1 \text{ pF} & C_e = 10 \text{ pF} & C_p = 0 \\
 E_{sc} = 430 \text{ mV} & R_u = 100 \text{ k}\Omega & R_d = 1 \text{ M}\Omega & R_e = 10 \text{ M}\Omega & R_p = \infty
 \end{array}$$

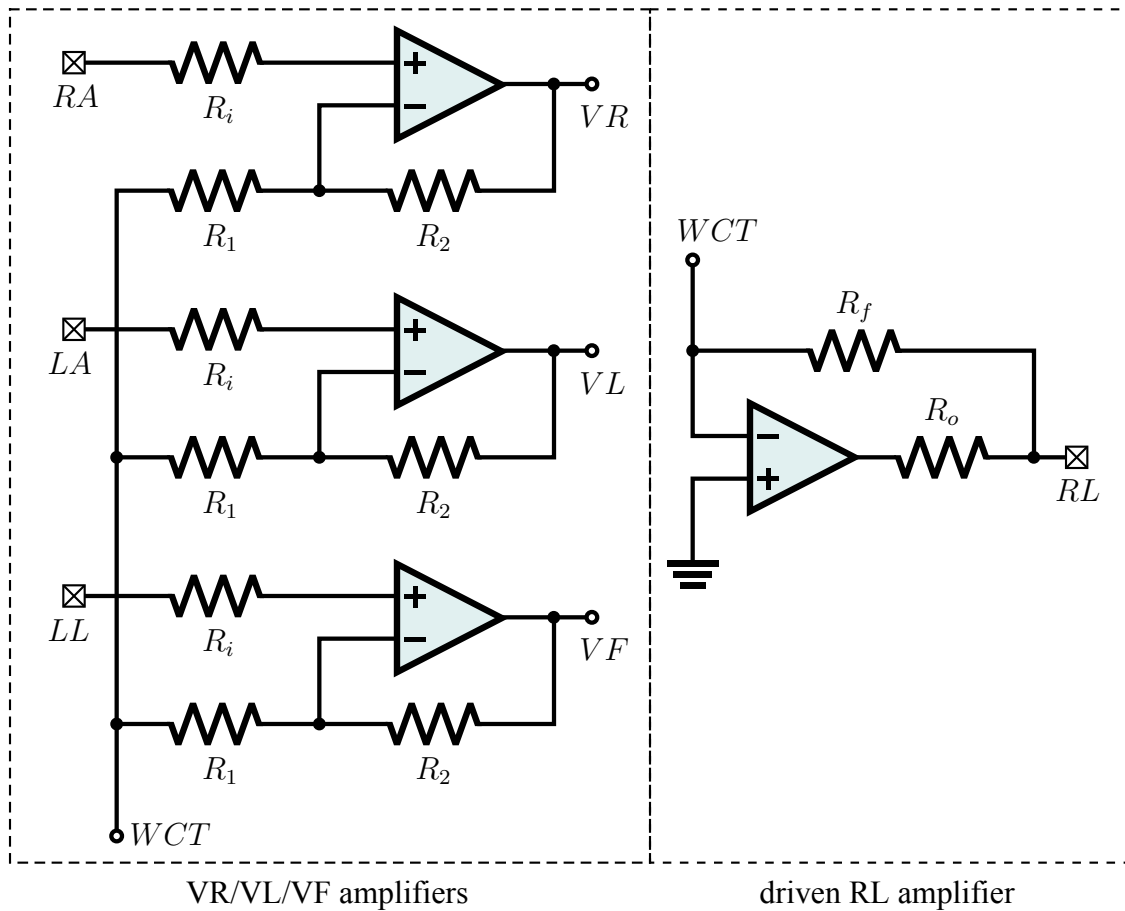3. **ECG amplifiers:** Consider the four-electrode frontal lead ECG bioamplifier system below:



- Derive the lead voltage outputs V_R , V_L , and V_F in terms of the electrode voltages R_A , L_A , and L_L , respectively. What are the voltage gains on each of these leads?
- Derive the driven right leg voltage output R_L in terms of the common mode of R_A , L_A , and L_L . What is the common mode voltage gain driving the right leg?
- Find the effective resistance from body to ground in terms of the R_L electrode impedance R_{RL} and the resistances of the circuit.
- What purpose do resistors R_i and R_o serve in this circuit?
- BONUS:** Using additional opamps and resistances, augment your circuit to produce six amplified leads I, II, III, aVR, aVL, and aVF from the V_R , V_L and V_F outputs. Express the total voltage gain of the leads in terms of the resistances.

4. **Design problem:** Your task is to design part of an internal (or implanted) automatic defibrillator (IAD) operating from a single 1.2 V battery. Your design has three parts.
- (a) The IAD has three electrodes (ground and two lead I electrodes) available for the purposes of obtaining electrocardiograms. Design an amplifier so the IAD microcontroller can observe heart activity.
 - Assume that the electrodes include protection circuitry for overvoltage protection during IAD electric shock delivery.
 - This amplifier should have a gain of at least 1000.
 - The amplifier should filter out signals above 1 kHz.
 - The amplifier should use active grounding. The ground should not pass more than $5\ \mu\text{A}$ and should reduce the common mode signal by at least a factor of 1000.
 - (b) The IAD defibrillator is configured to perform cardioversion when needed by delivering a high-energy electrical shock to the heart. It is critical that such shock never be delivered during a T wave, or ventricular tachycardia may be induced which may be fatal. Design a circuit to block the IAD from delivering any shock for a duration of 400 ms after every R wave in the ECG, spanning the T wave with sufficient timing margin. The circuit should generate a digital control signal that goes high (1.2 V) for the duration of the block.
 - (c) The IAD includes an ultrasonic transmitter to notify an external monitor whenever a shock is being delivered. Design a circuit that generates a 500 kHz 1.2 V square wave driving an ultrasonic speaker whenever the IAD cardioverter is active. The cardioverter goes active when it is driven to 1.2V by the IAD microcontroller.